

ARCOS Group

uc3m | Universidad **Carlos III** de Madrid

Lesson 4 (I) The processor

Computer Structure
Bachelor in Computer Science and Engineering



Contents


1. Computer elements
2. Processor organization
3. Control unit
4. Execution of instructions
5. Control unit design
6. Execution modes
7. Interrupts
8. Computer startup
9. Performance and parallelism

Contents


- 1) Motivation and goals
- 2) Basic functionality of the control unit
- 3) Control signals and elemental operations
- 4) Introduction of the elemental processor

- 1. Computer elements
- 2. Processor organization
- 3. Control unit
- 4. Execution of instructions
- 5. Control unit design
- 6. Execution modes
- 7. Interrupts
- 8. Computer startup
- 9. Performance and parallelism


Computer components review

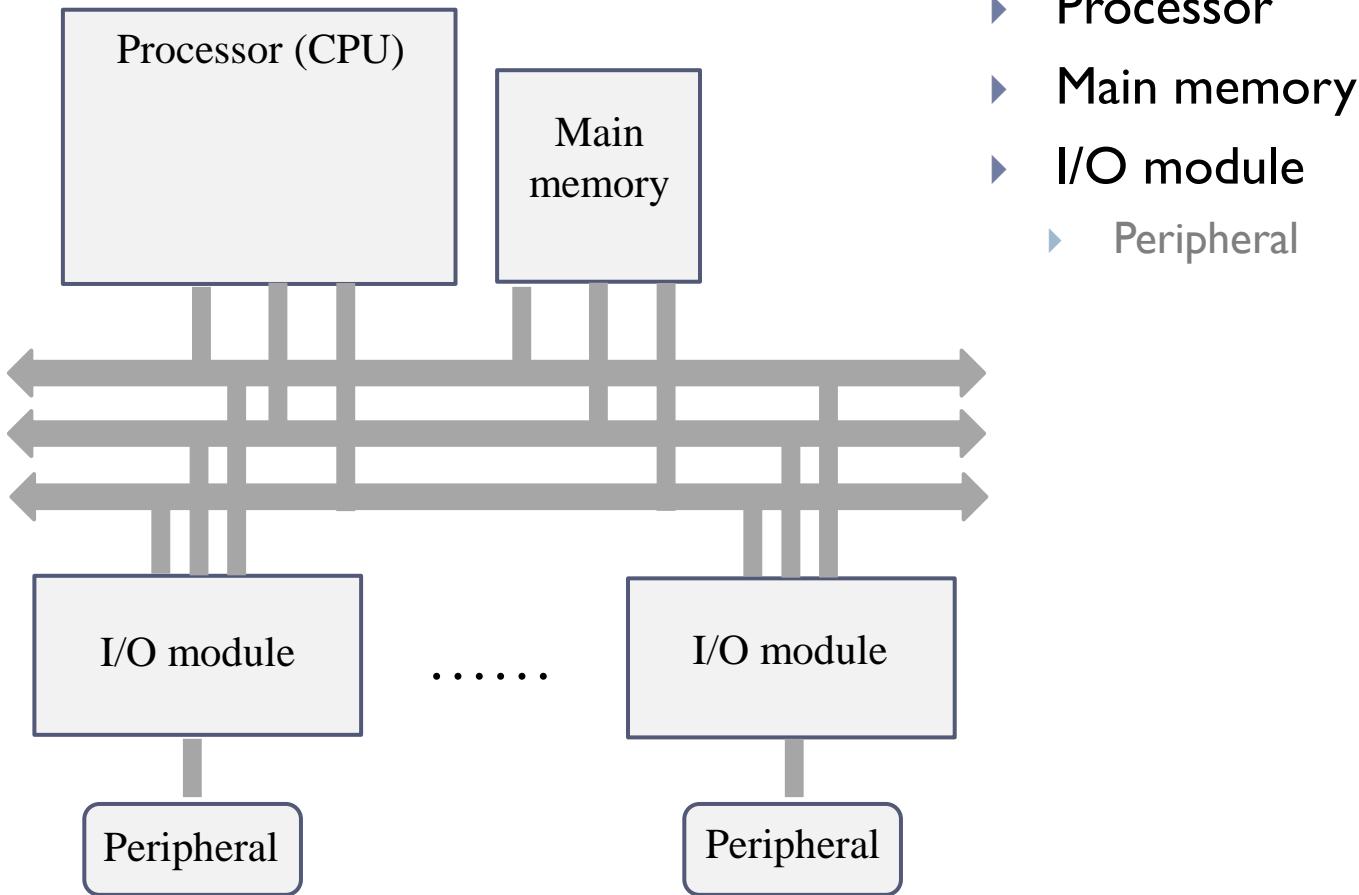

Processor components review

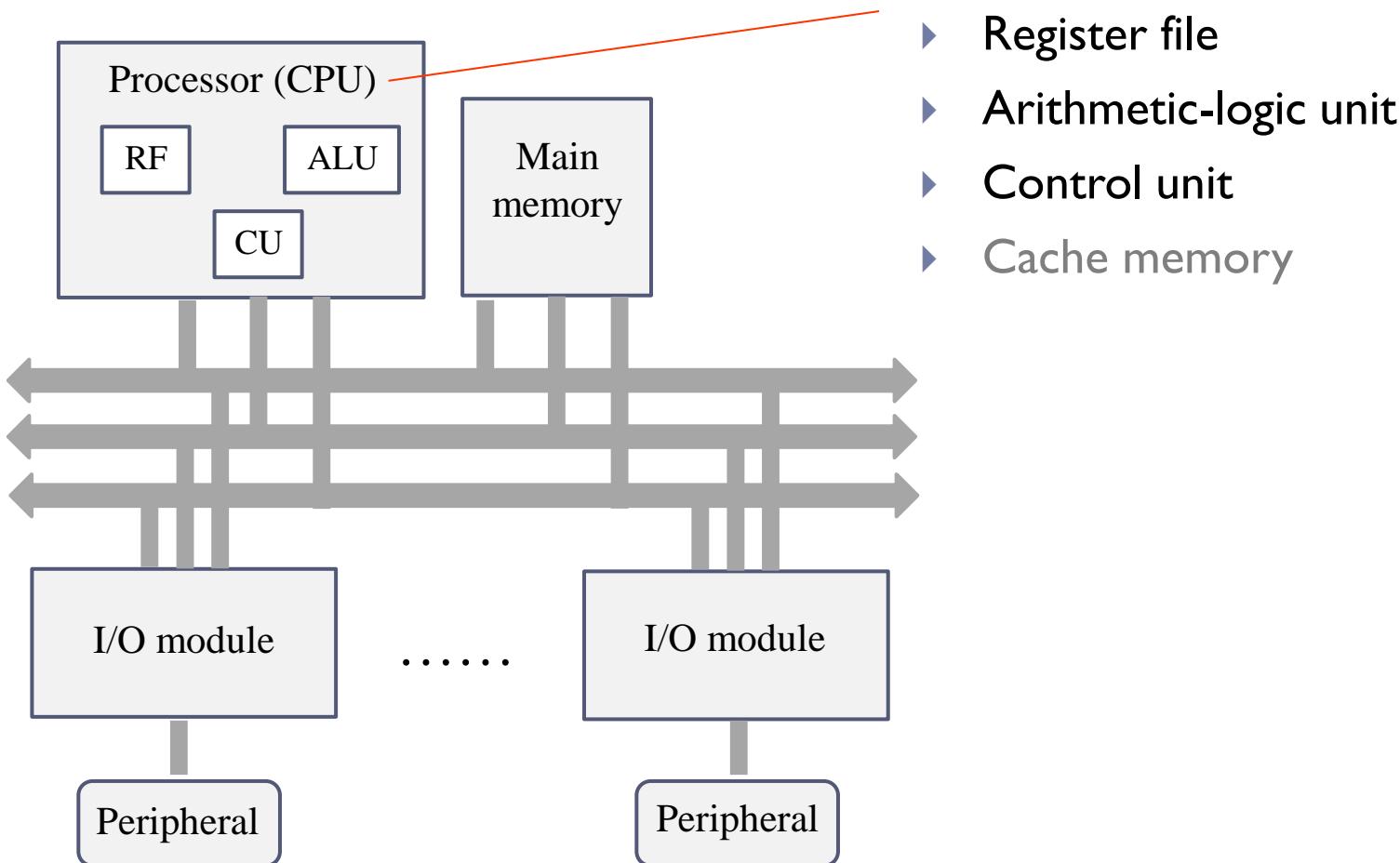


Main motivation

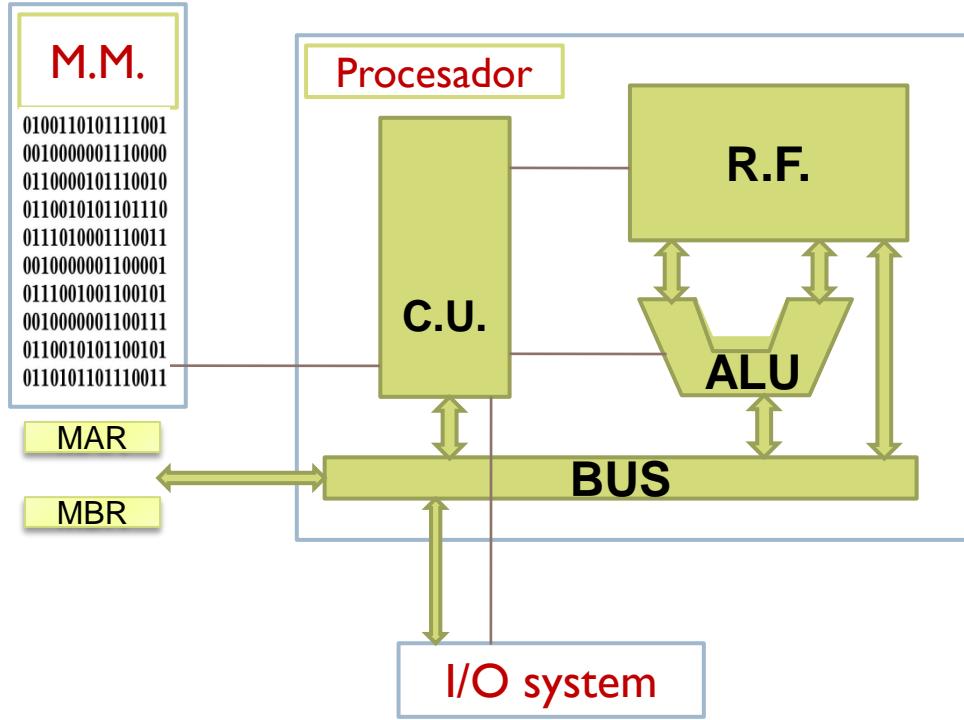

- In lesson 3, we studied **what** processor execute: assembly programming.
- In lesson 4 we are going to study **how** the instructions are executed in the computer.

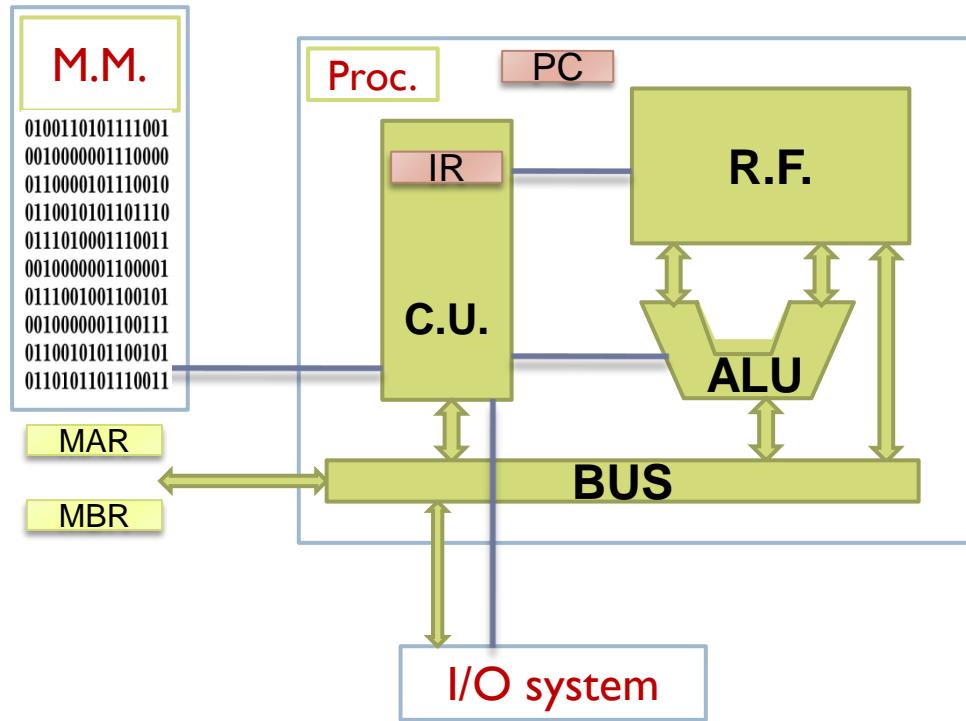How C.U. works: Execute machine instructions





- Each element of the computer has inputs, outputs and control signals.
- At each clock cycle, the Control Unit (C.U.) sends the control signals via the control bus wires.
- Control signals indicate what value to output:
 - Move from an input to an output: $S=Ex$
 - Transform an input: $S=f(E)$

Contents

- 1) Motivation and goals
 - 2) Basic functionality of the control unit
 - 3) Control signals and elemental operations
 - 4) Introduction of the elemental processor
-
- 1. Computer elements
 - 2. Processor organization
 - 3. Control unit
 - 4. Execution of instructions
 - 5. Control unit design
 - 6. Execution modes
 - 7. Interrupts
 - 8. Computer startup
 - 9. Performance and parallelism


How C.U. works...

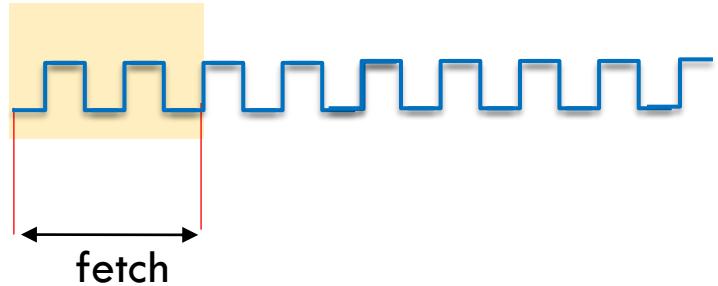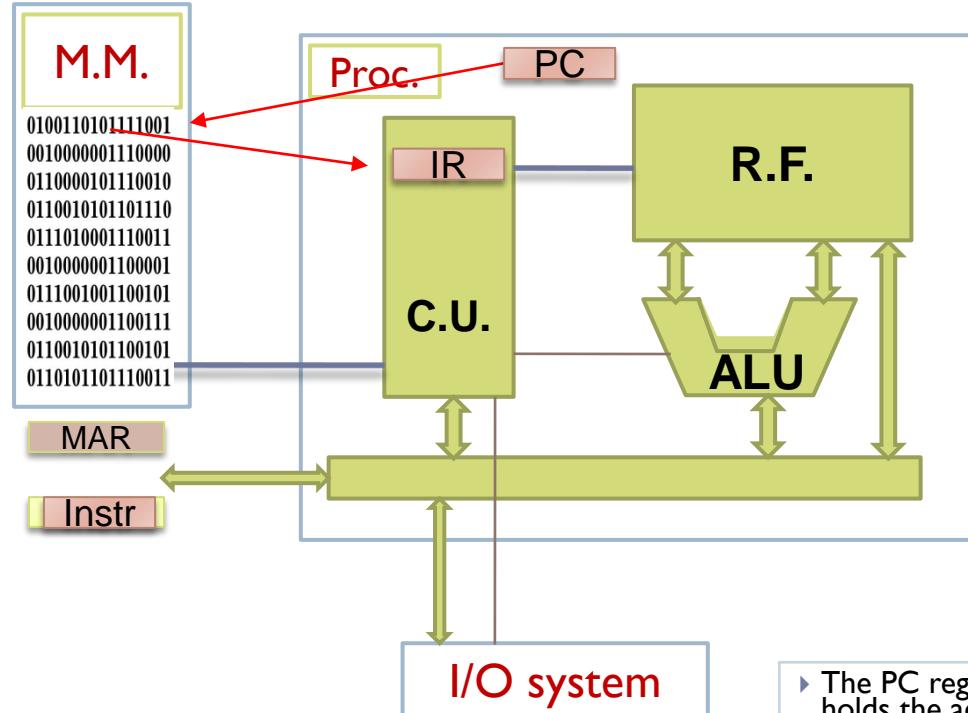



- Read from main memory the instruction pointed to by PC
- Increment PC
- Decode instruction
- Execute

- ▶ The PC register (program counter) holds the address of the next instruction to be executed.
- ▶ The RI register (instruction register) holds the instruction is currently executed.

How C.U. works...

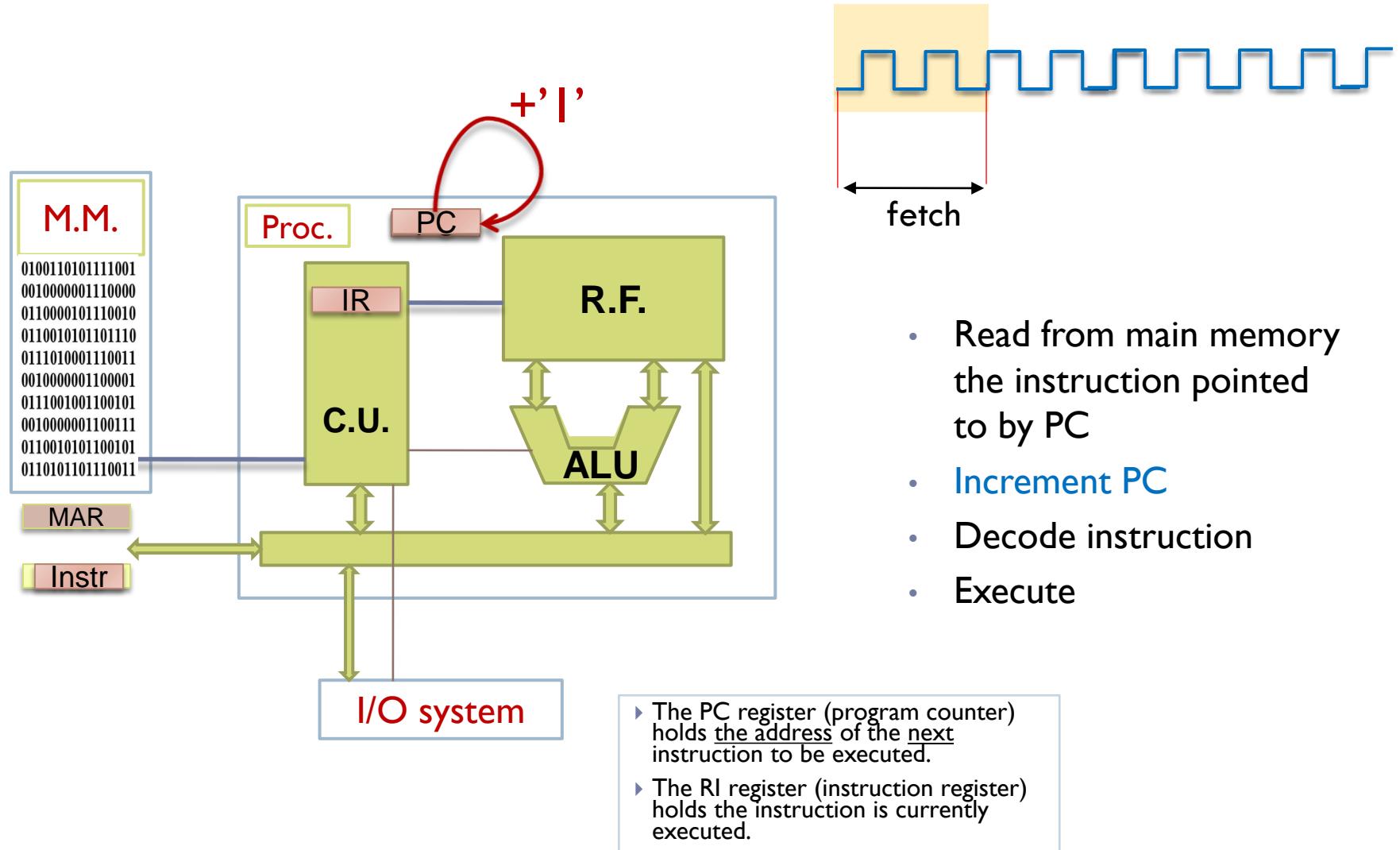



How C.U. works...

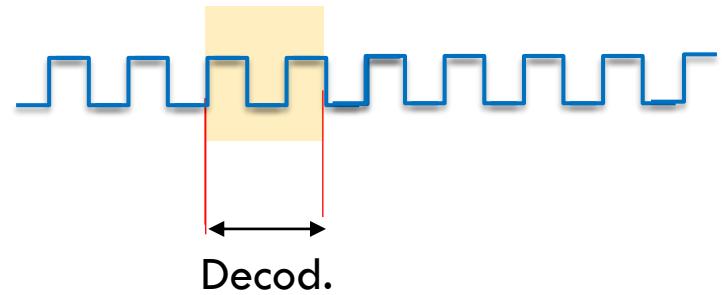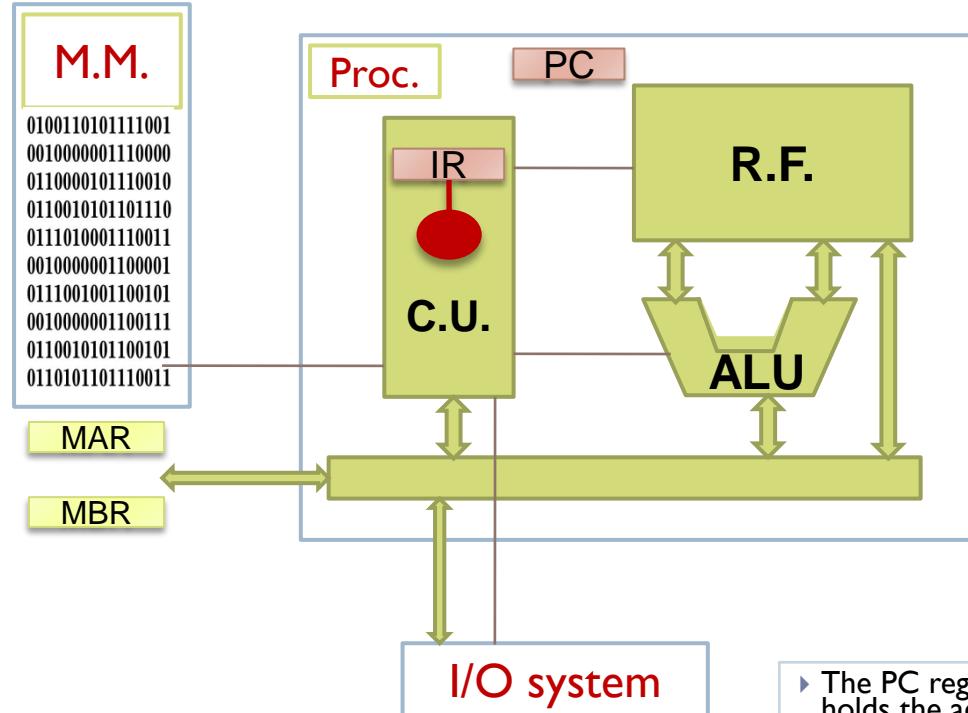

- Read from main memory the instruction pointed to by PC
- Increment PC
- **Decode instruction**
- Execute


- ▶ The PC register (program counter) holds the address of the next instruction to be executed.
- ▶ The RI register (instruction register) holds the instruction is currently executed.

How C.U. works...

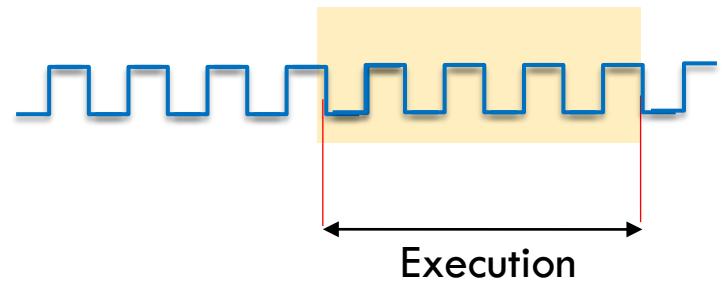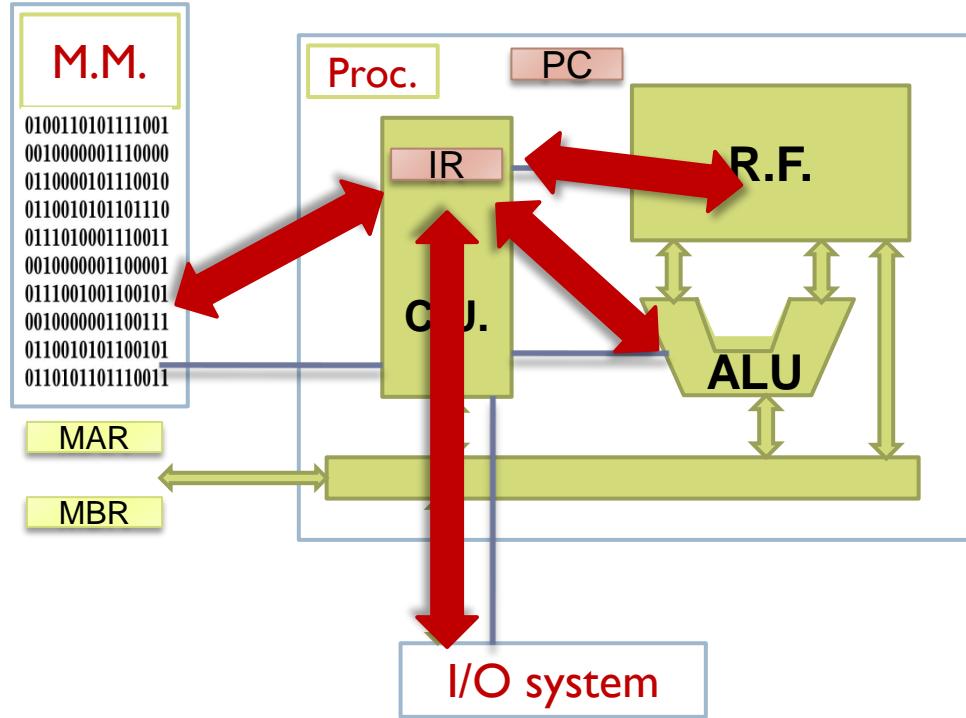

- Read from main memory the instruction pointed to by PC
- Increment PC
- Decode instruction
- Execute

Other functions of the C.U.

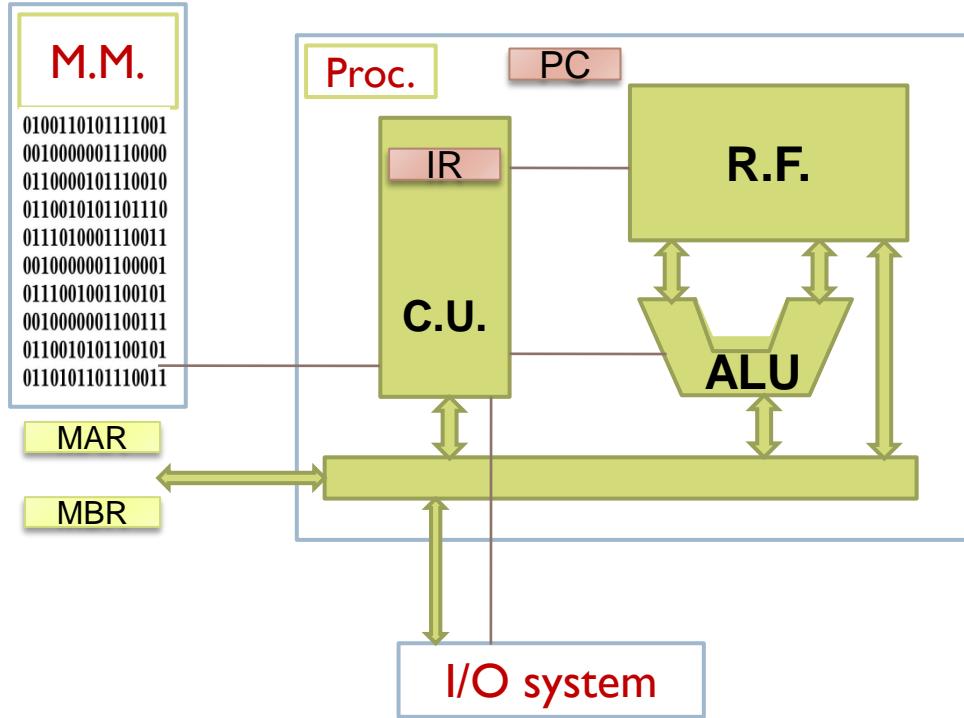


- **Resolving anomalous situations**
 - Illegal instructions
 - Illegal memory accesses
 - ...
- **Attend to interruptions**
- **Control the communication with the peripherals.**

Contents

- 1) Motivation and goals
- 2) Basic functionality of the control unit
- 3) Control signals and elemental operations
- 4) Introduction of the elemental processor

- 1. Computer elements
- 2. Processor organization
- 3. Control unit
- 4. Execution of instructions
- 5. Control unit design
- 6. Execution modes
- 7. Interrupts
- 8. Computer startup
- 9. Performance and parallelism

Register and bus

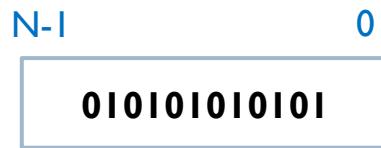



▶ Register

- ▶ Let us store a list of bits

▶ Bus

- ▶ Let us to transfer a list of bit between two elements connected though the bus

Signals: output tristate

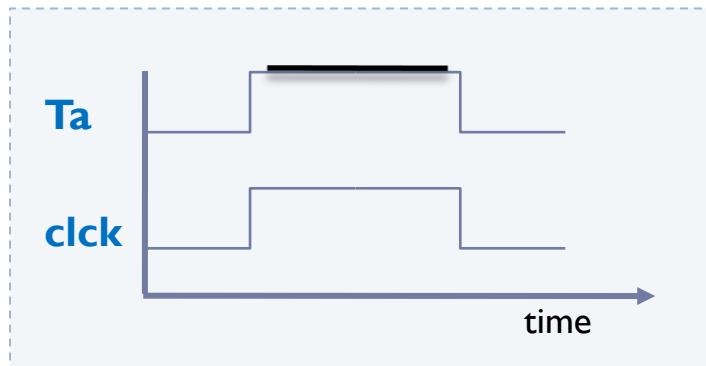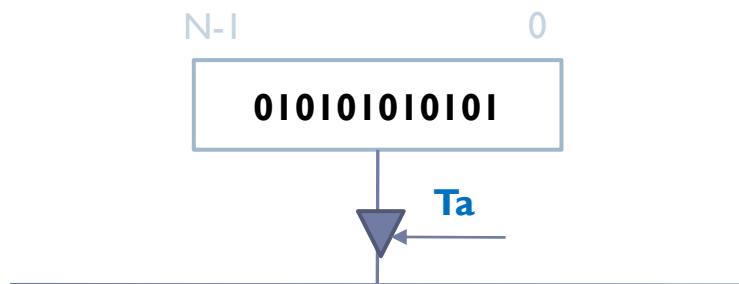



▶ Tri-state

- ▶ In the middle of the elements and the bus.
- ▶ Allows to send data to the bus.

▶ IMPORTANT

- ▶ Two or more tri-states cannot be activated on the same bus at the same time.


Signals: load in register

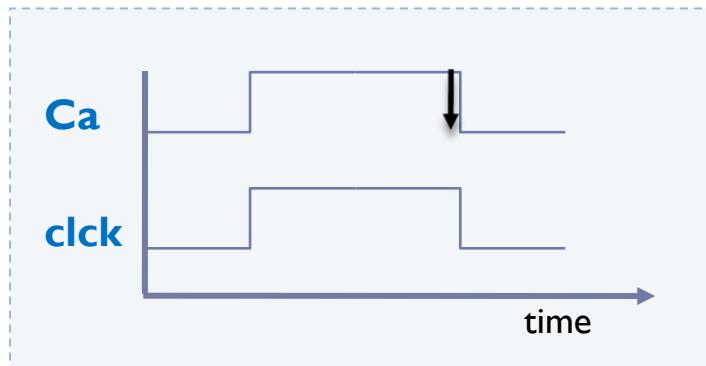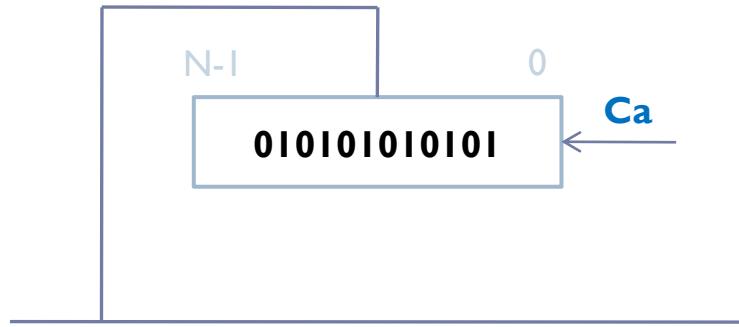


- ▶ Load in register
 - ▶ Let store the input value at the clock falling edge
 - ▶ During the clock level the register keeps the inner (old) value.
 - ▶ At the end of the clock cycle (falling edge) is when the inner value is updated

- ▶ **IMPORTANT**
 - ▶ Therefore, in the following cycle, the new value will be seen at the output


Sequence of signals

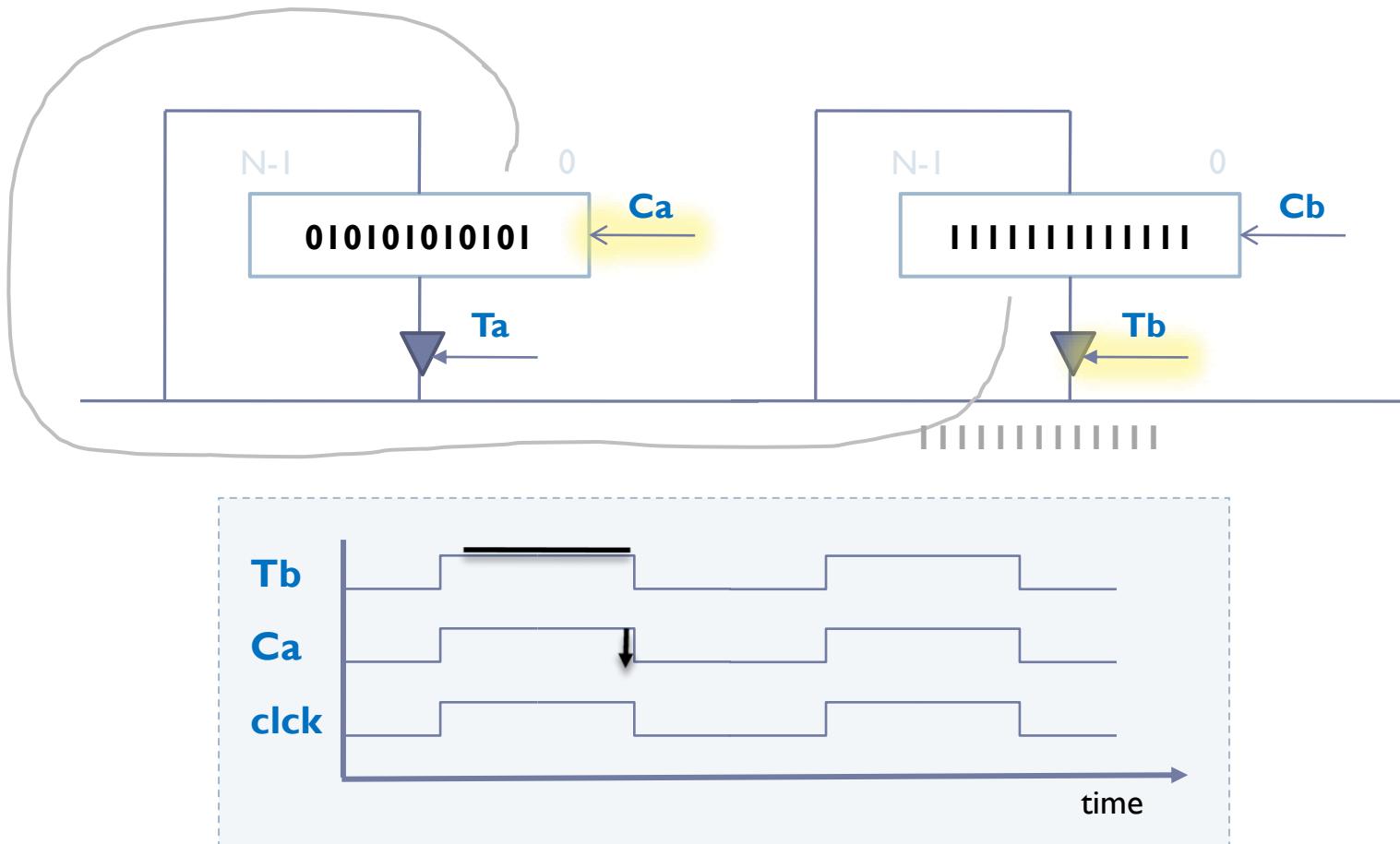

Sequence of signals

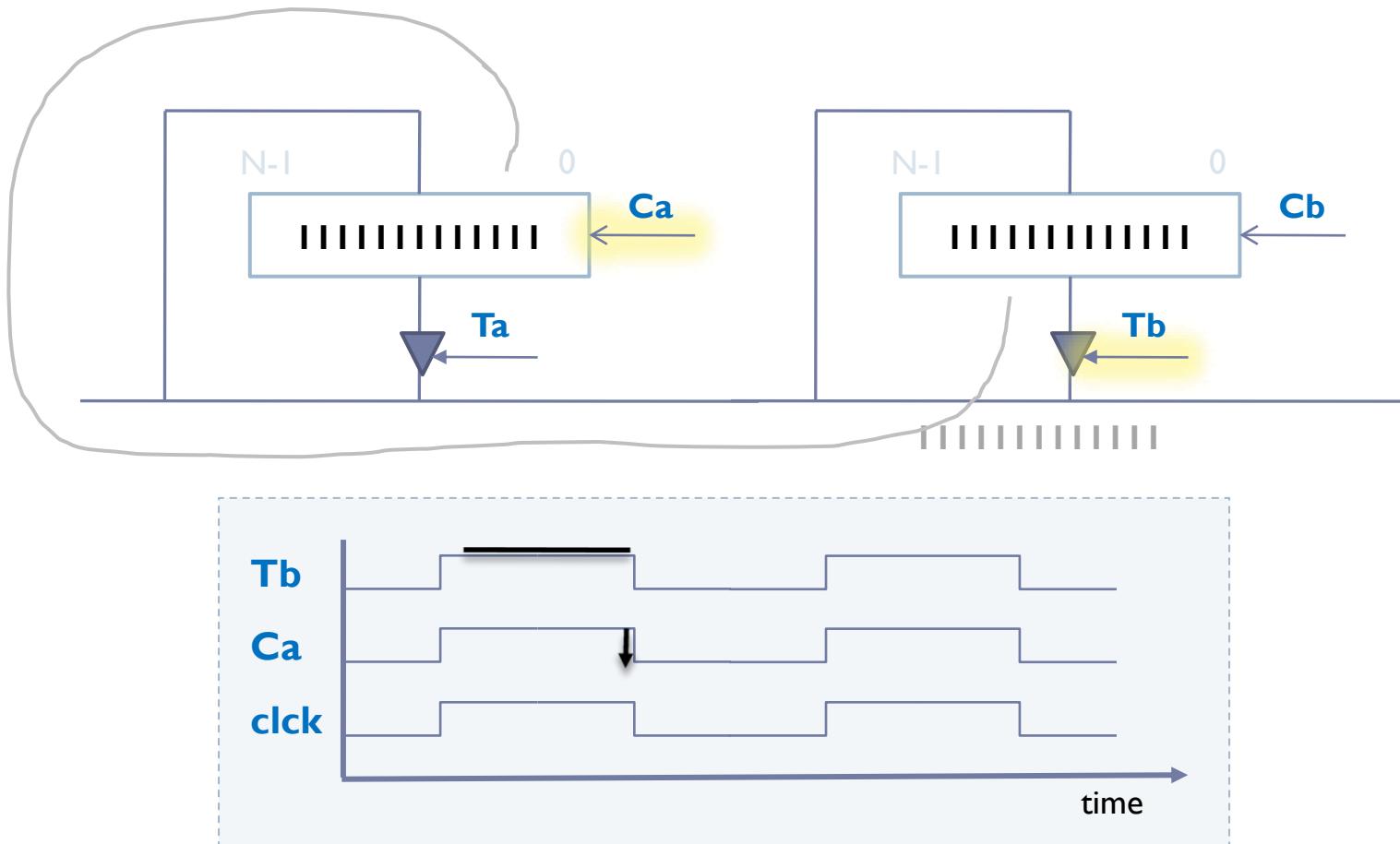

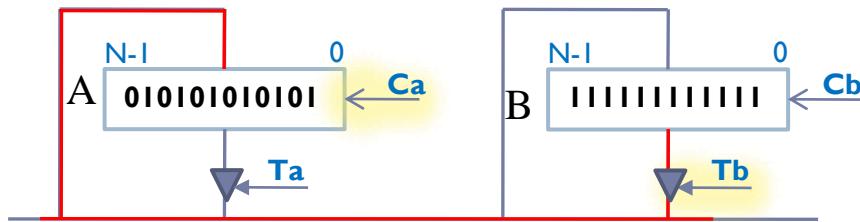
Example of *transfer* elemental operation



- ▶ **Elementary transfer operation:**

- ▶ Source storage element
- ▶ Target storage element
- ▶ A path is established



xx: $A \leftarrow B$ [Tb, Ca]

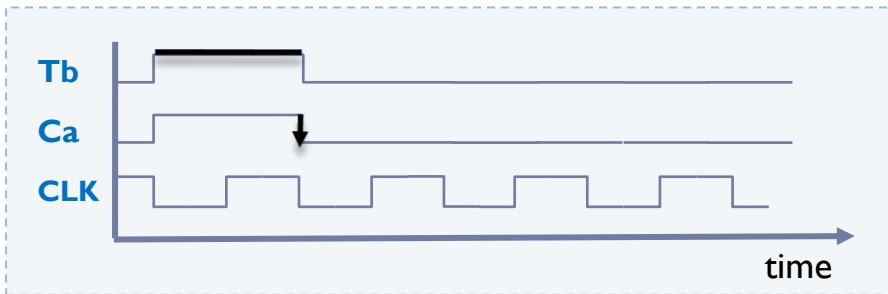


- ▶ **IMPORTANT**

- ▶ Establish the path between origin and destination in the same cycle
- ▶ In the same cycle NOT:
 - ▶ Traverse a register
 - ▶ carry two values to a bus at the same time.

Sequence of signals

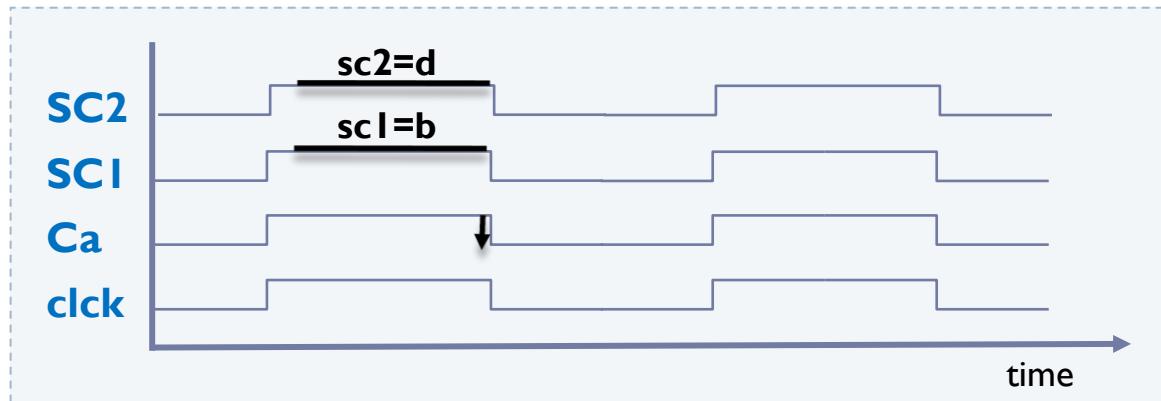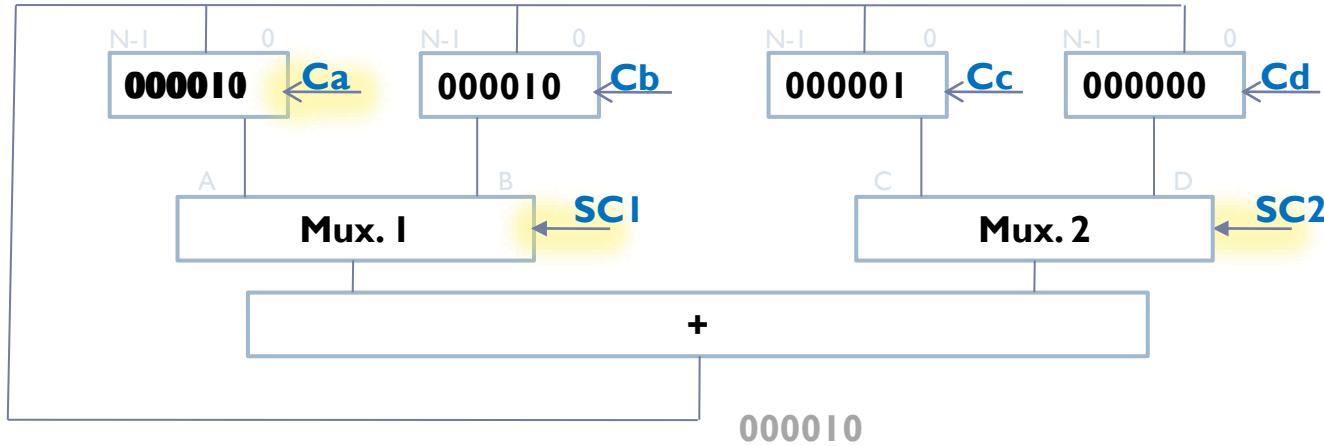


Example of process elemental operation

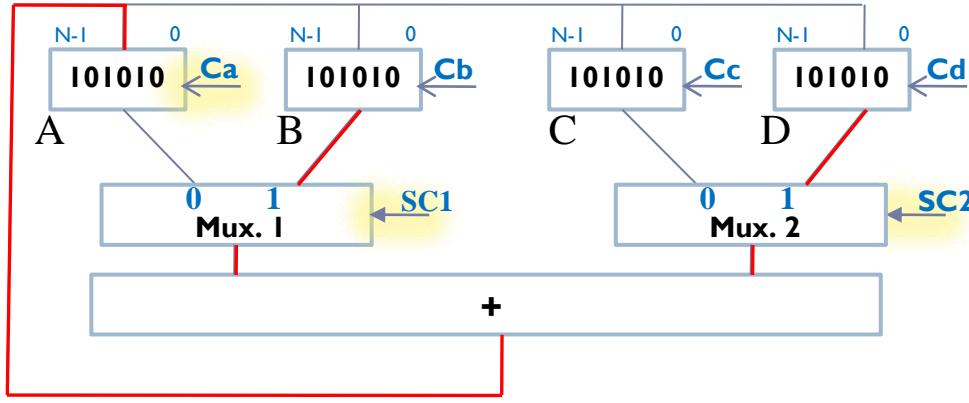

- ▶ **Elementary processing operation:**
 - ▶ Source element(s)
 - ▶ Target element
 - ▶ Transformation operation on the path

yy: $A \leftarrow B+D$ [SC1=b,SC2=d, Ca]

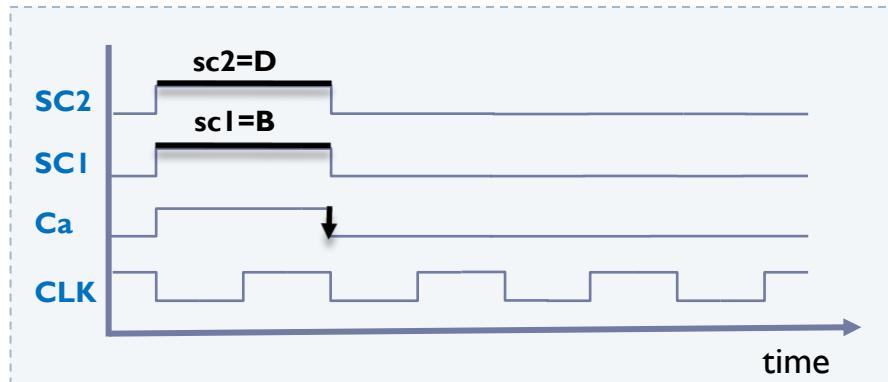


- ▶ **IMPORTANT**
 - ▶ Establish the path between origin and destination in the same cycle
 - ▶ In the same cycle NOT:
 - ▶ Traverse a register
 - ▶ carry two values to a bus at the same time.

RT Language and Elementary Operations

- ▶ RT Language:
 - ▶ Register transfer level language.
 - ▶ It specifies what happens in the computer by elementary operations.
- ▶ Elementary operations:
 - ▶ Transfer operations
 - ▶ $\text{MAR} \leftarrow \text{PC}$
 - ▶ Processing operations
 - ▶ $\text{RI} \leftarrow \text{R2} + \text{RT2}$




$\text{Reg} \leftarrow \text{Reg}$

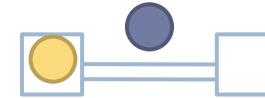

$\text{Reg} \leftarrow \varphi(\text{Reg}, \text{Reg})$

Review all components...

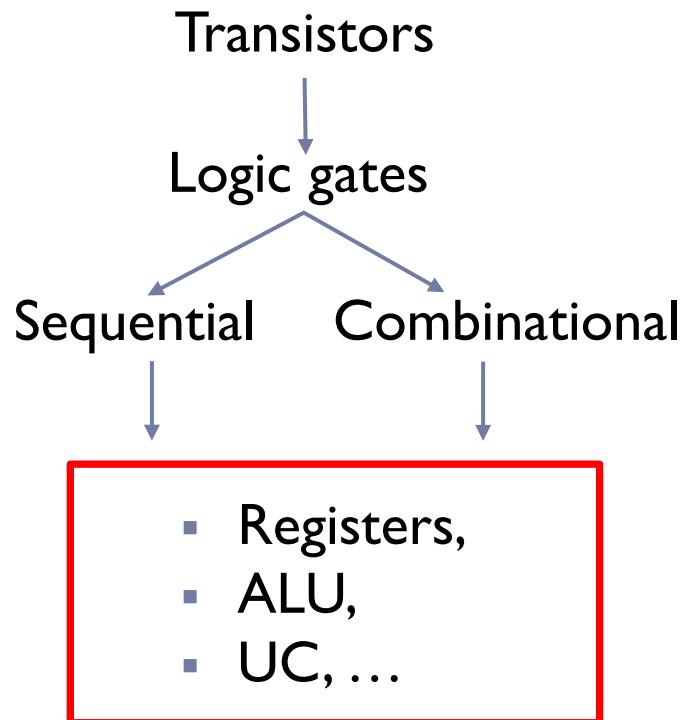- ▶ Binary system based on 0 y 1
- ▶ Building blocks:





Review all components...


Registers

- ▶ Element storing n bits at a time

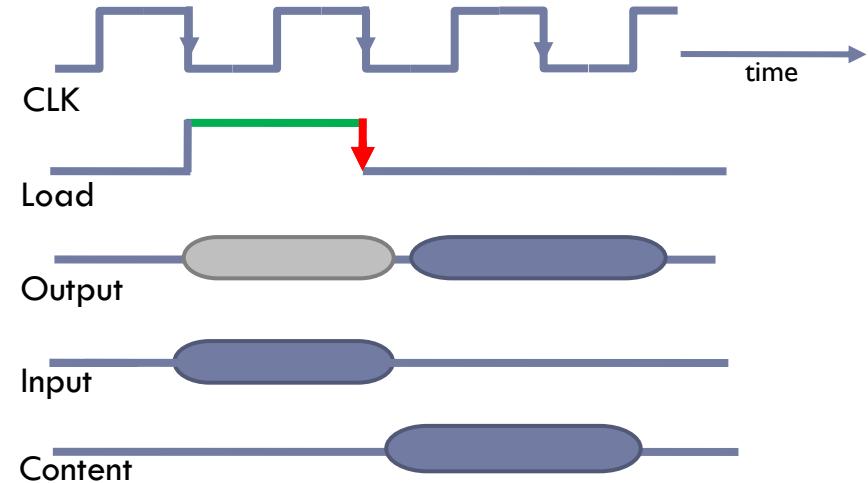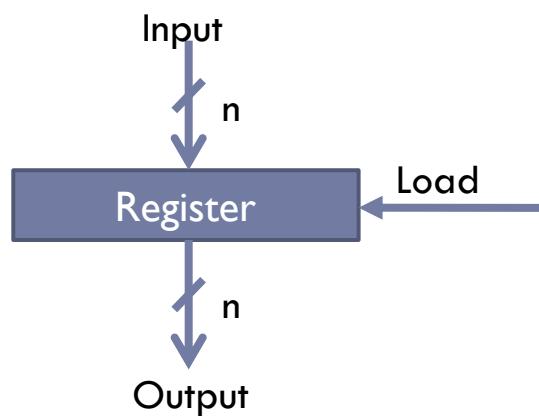- ▶ Output:
 - ▶ During **the level**, the output is the value stored in the register.
- ▶ Input:
 - ▶ Possible new value to be stored
- ▶ Control:
 - ▶ Load: in the **falling edge** the possible new value is stored
 - ▶ Reset: there may be a signal to set the register to zero



Control Unit (UC)

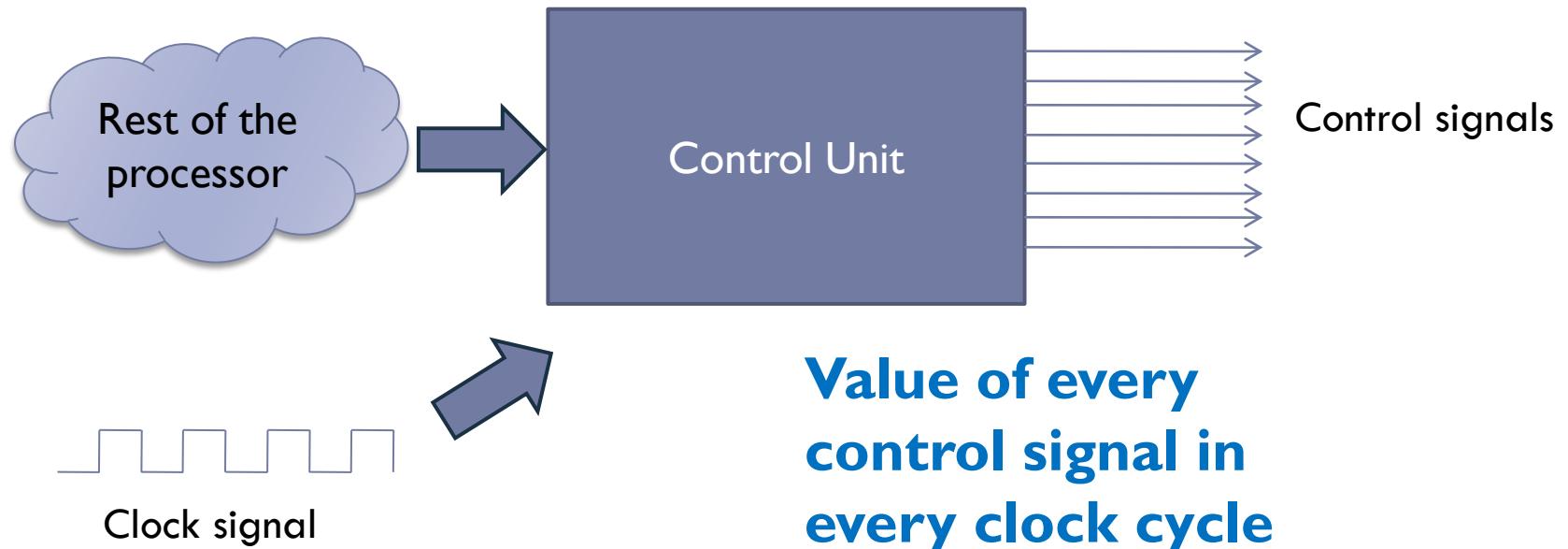


Contents

- 1) Motivation and goals
- 2) Basic functionality of the control unit
- 3) Control signals and elemental operations
- 4) Introduction of the elemental processor

- 1. Computer elements
- 2. Processor organization
- 3. Control unit
- 4. Execution of instructions
- 5. Control unit design
- 6. Execution modes
- 7. Interrupts
- 8. Computer startup
- 9. Performance and parallelism

Structure of an elementary computer and WepSIM Simulator

- ▶ Elemental Processor (E.P.):

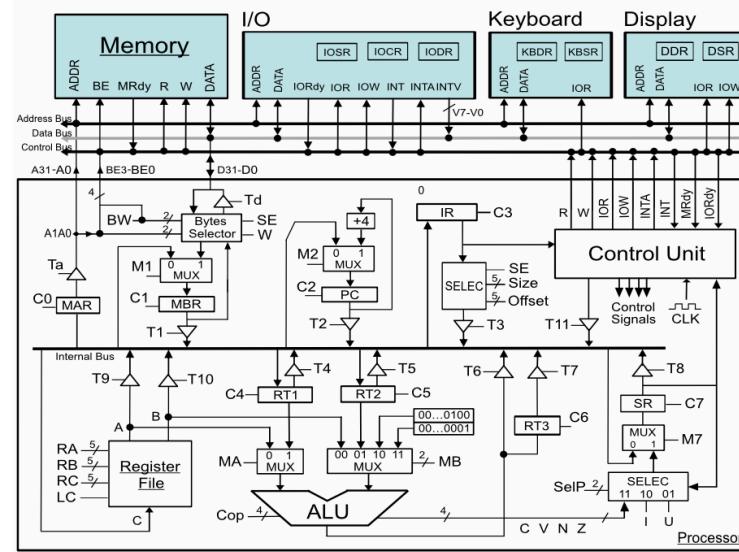


- ▶ WepSIM simulates the E.P.:
 - ▶ <https://wepsim.github.io/wepsim/>


Main features of the elemental processor

- ▶ 32 bits computer
- ▶ Main memory:
 - ▶ Addressed by bytes
 - ▶ A clock cycle for reading and writing operations
- ▶ Different types of registers available:
 - ▶ Register file of 32 registers visible to programmers (R0...R31)
 - ▶ Similar to MIPS: R0 = 0 and SP = R29
 - ▶ Registers not visible to programmers (RT1, RT2 and RT3)
 - ▶ Possible use for intermediate calculations within an instruction
 - ▶ Control registers (PC, IR, MAR, MBR) and state register (SR)
 - ▶ MAR, MBR, PC, SR, IR


Structure of an elementary computer

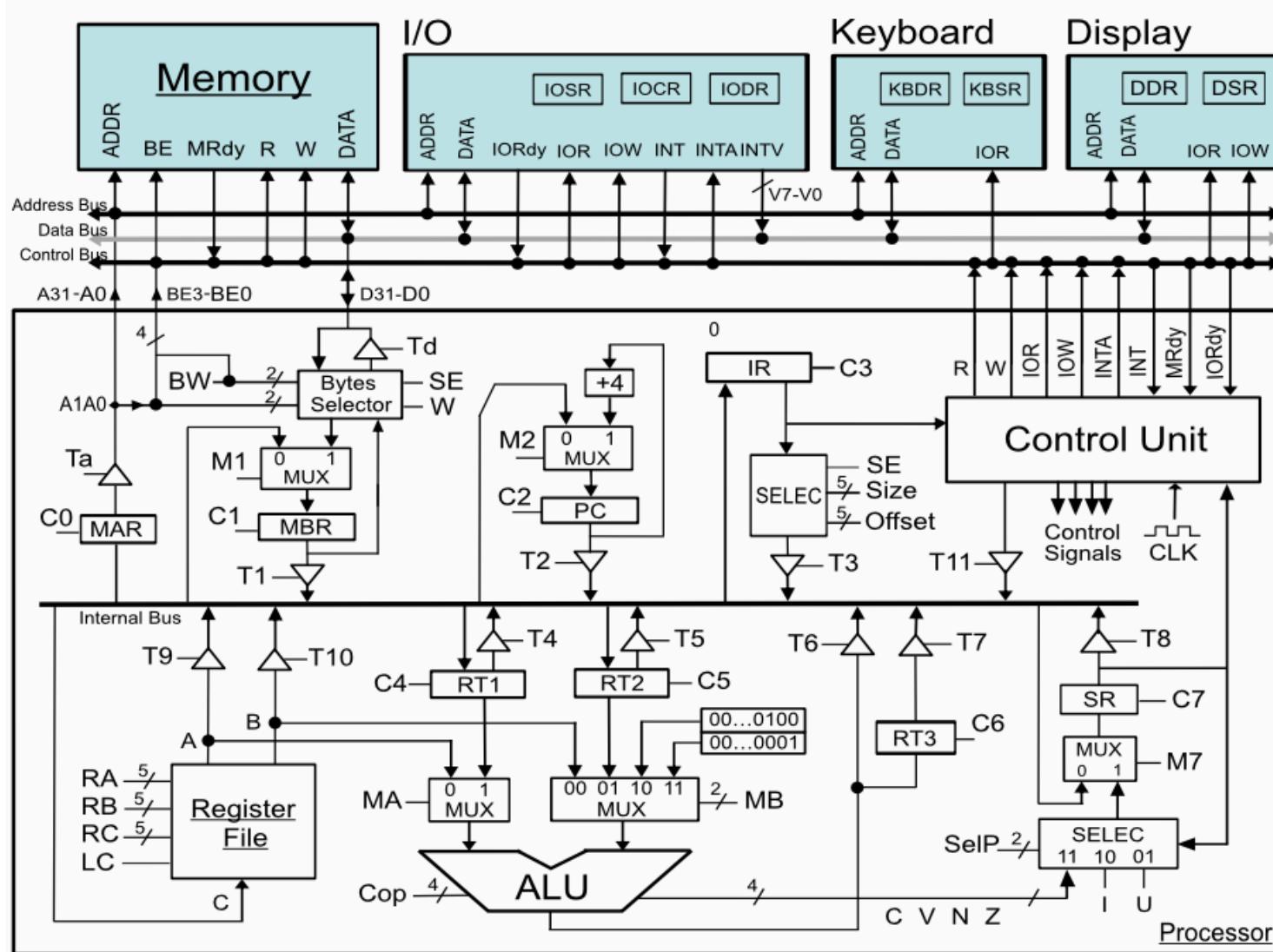

Control signals

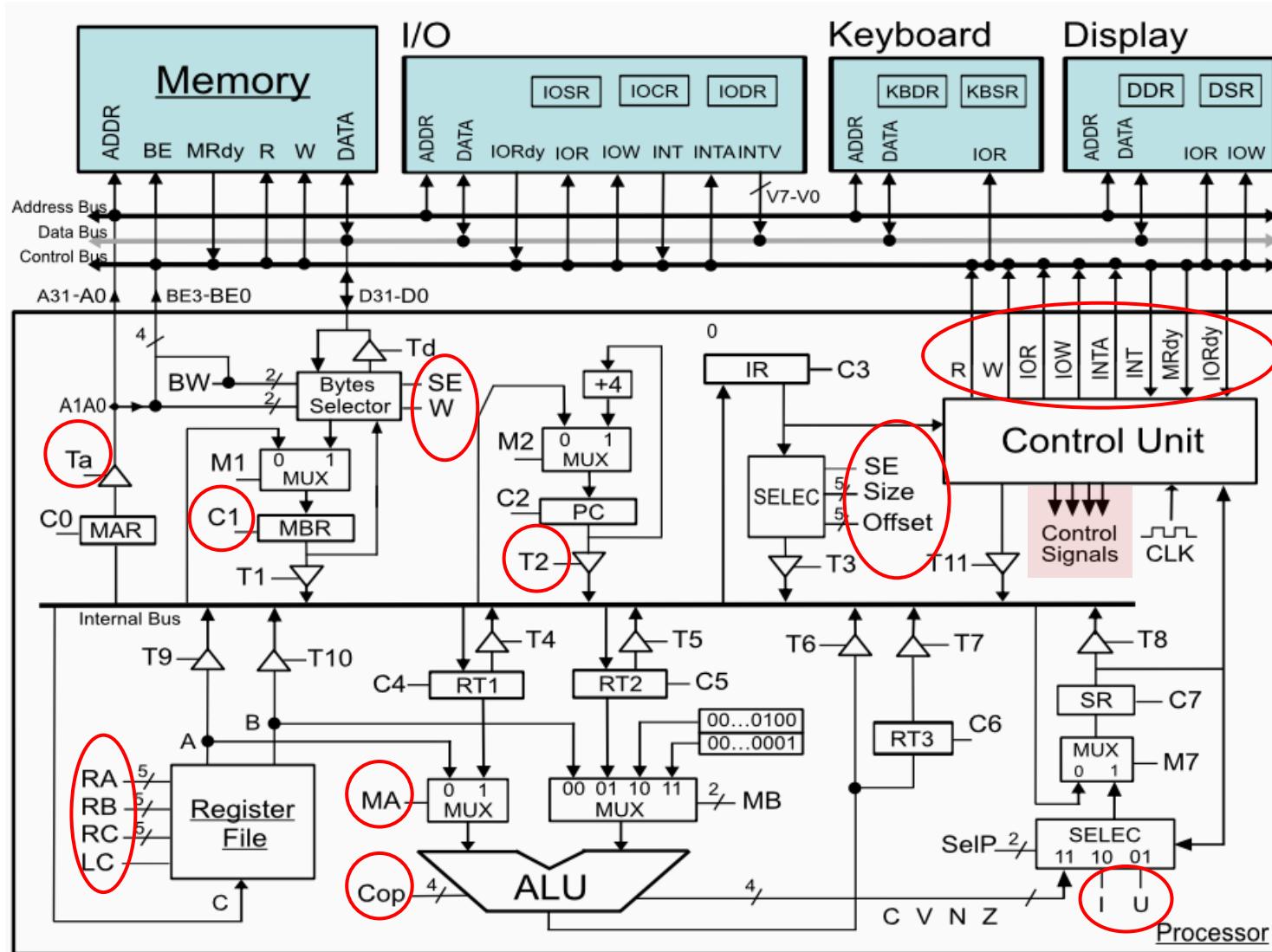


Control signals

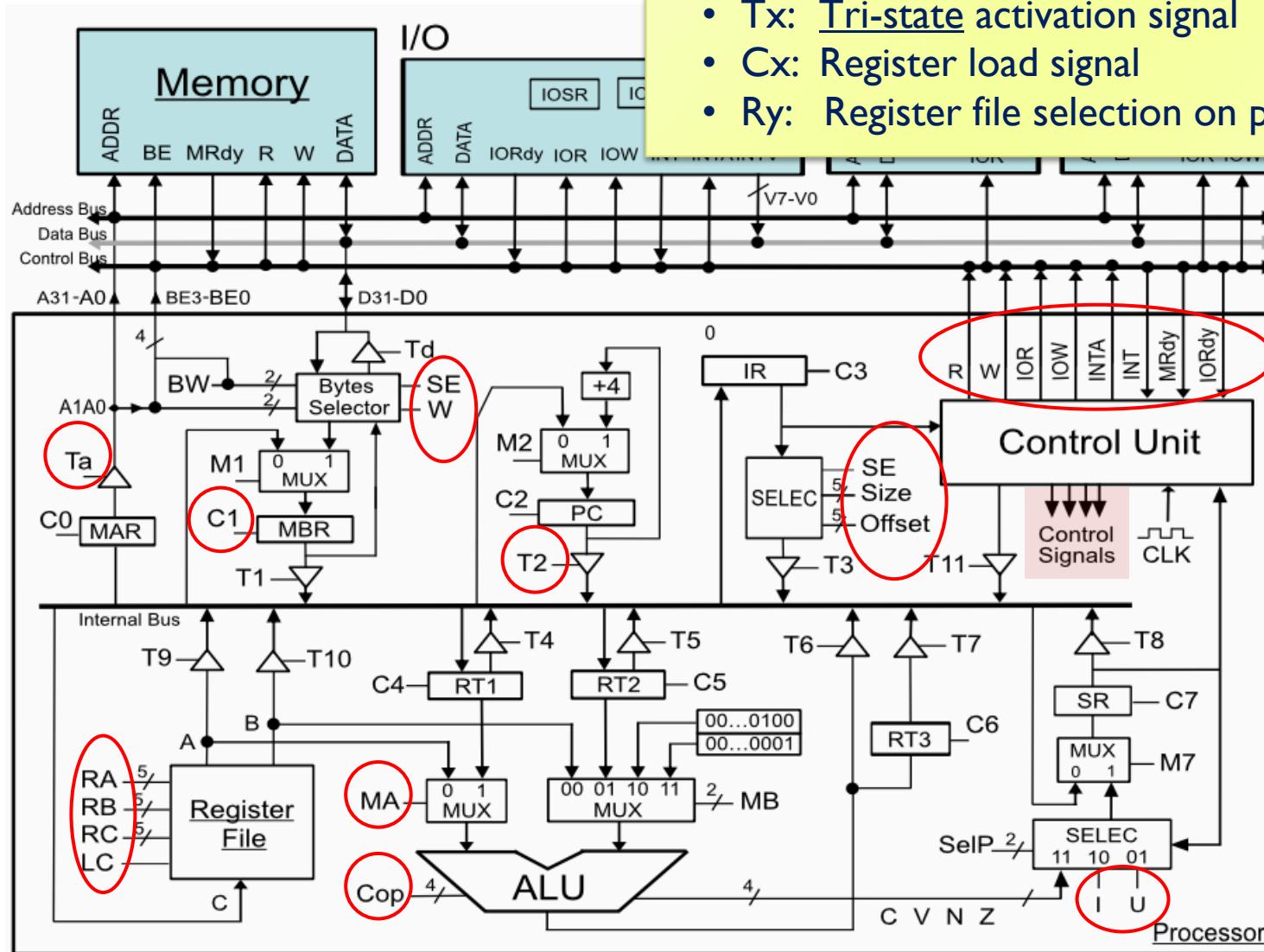


General nomenclature:

- M_x: Selection in multiplexor
- Tx: Tri-state activation signal
- C_x: Register load signal
- Ry: Register file selection on point y

Elemental Processor: control signals



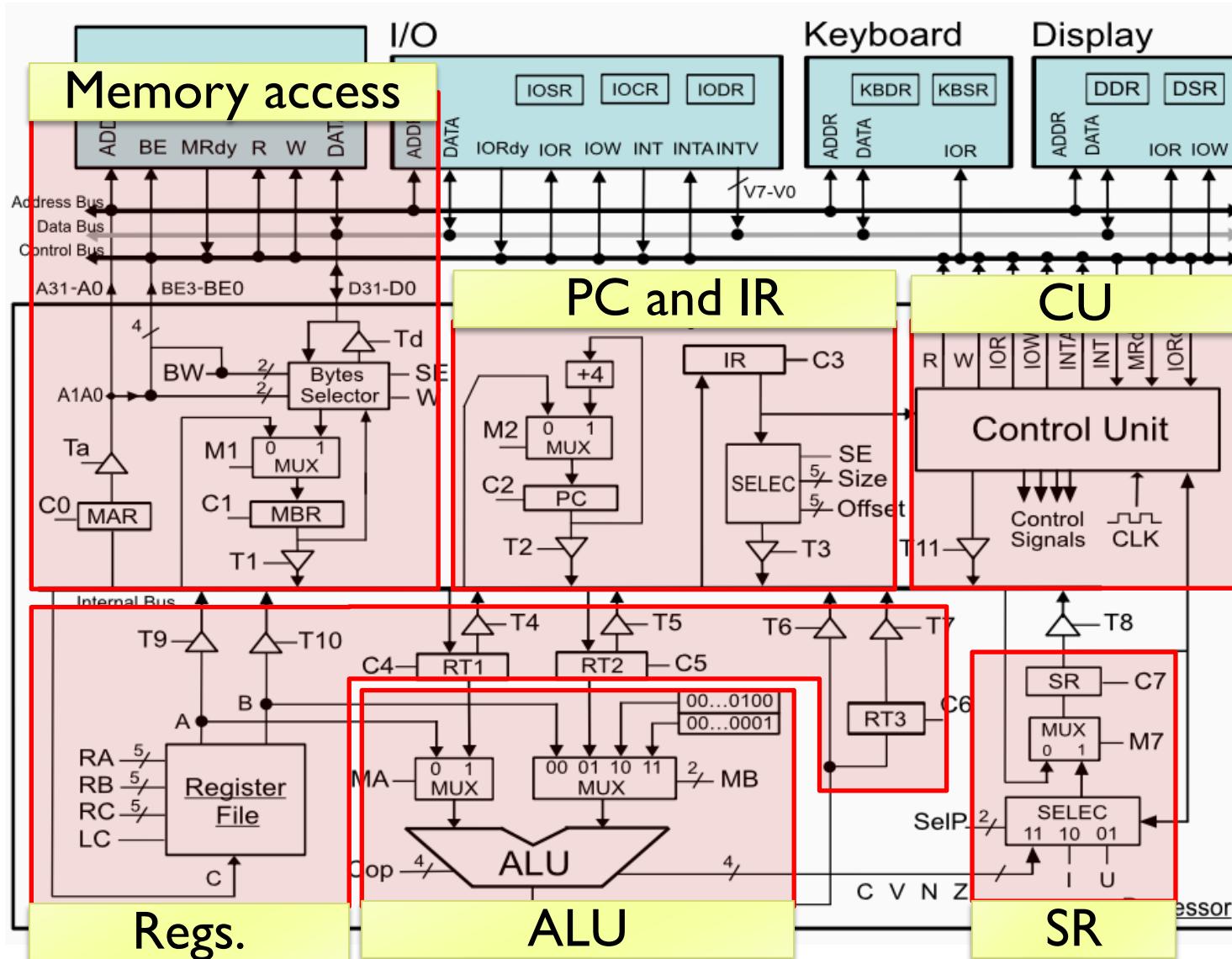


Elemental Processor: registers

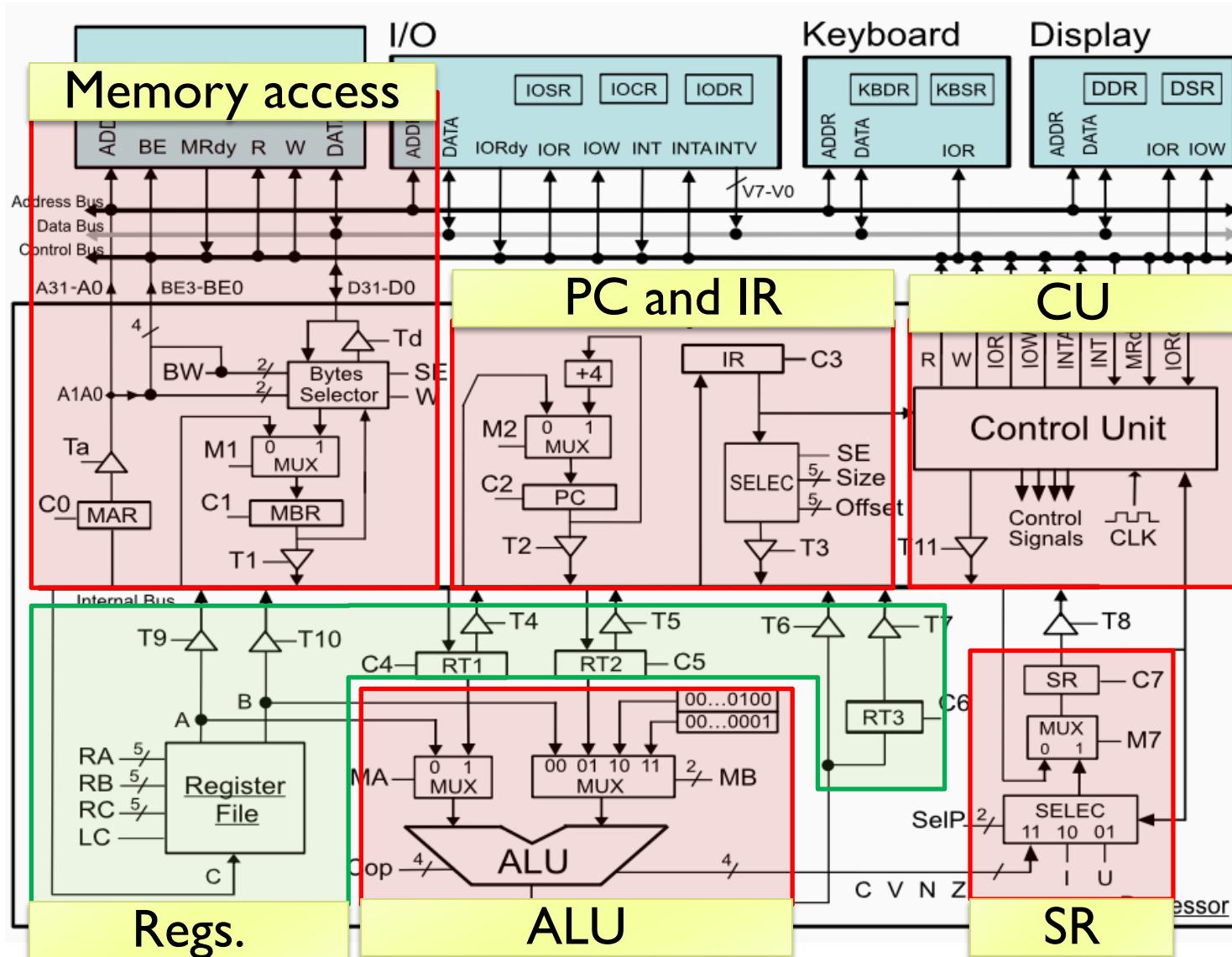


Registers

- ▶ Registers visible to programmers
 - ▶ Register file's registers (~MIPS: \$t0, \$t1, etc.)
- ▶ Control and status registers:
 - ▶ PC: program counter
 - ▶ IR: instruction register
 - ▶ SP: stack pointer (in the register file)
 - ▶ MAR: memory address register
 - ▶ MBR: memory data register
 - ▶ SR: status register
- ▶ Registers not visible to the user:
 - ▶ RT1, RT2 and RT3 (internal temporal reg.)

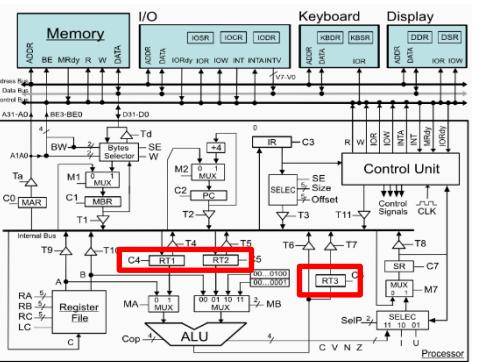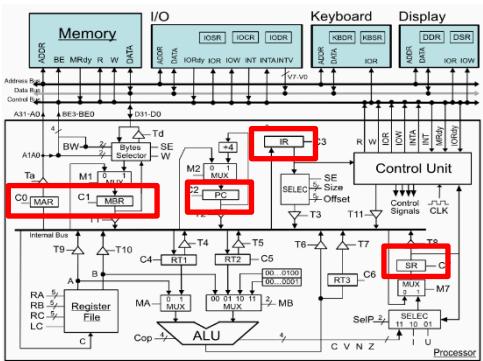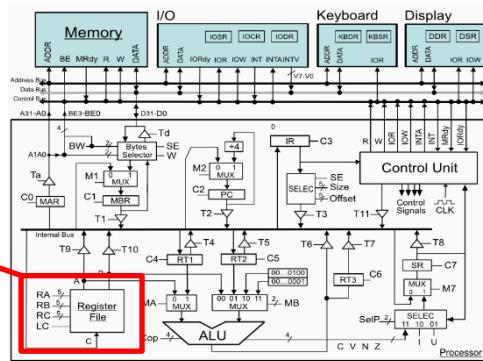

Structure of an elementary computer

Registers

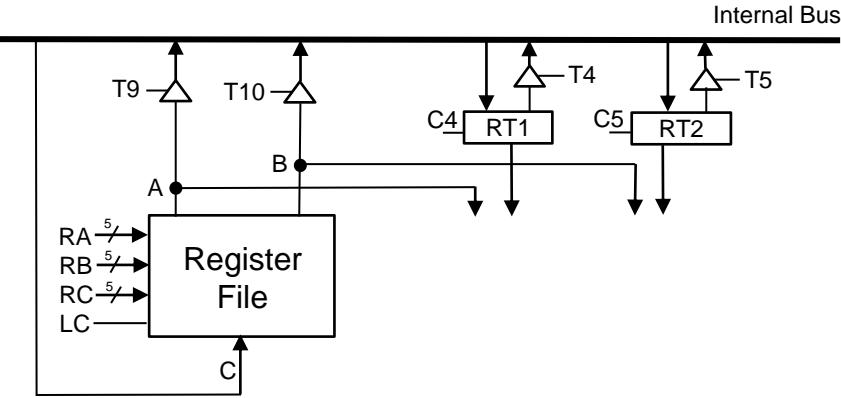

Nomenclature:

- Ry: Register file selection
- Tx: Tri-state activation signal
- Cx: Register load signal


▶ Register file

- ▶ RA – register output by A
- ▶ RB – register output by B
- ▶ RC – input C to the RC register
- ▶ LC – activates writing for RC
- ▶ T9 - copy A to the internal bus
- ▶ T10 - copy B to the internal bus

▶ RT1 and RT2


- ▶ C4 - from the internal bus to RT1
- ▶ T4 - RT1 output to internal bus
- ▶ C5 - from the internal bus to RT2
- ▶ T5 - RT2 output to internal bus

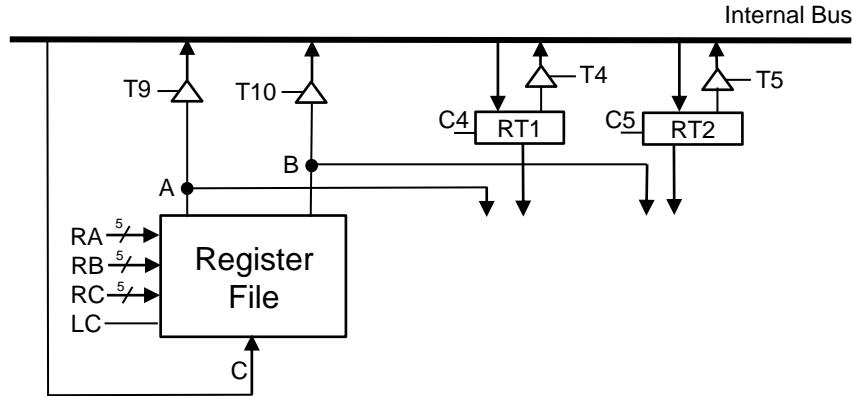Example elemental operations in registers



▶ **SWAP RI R2**

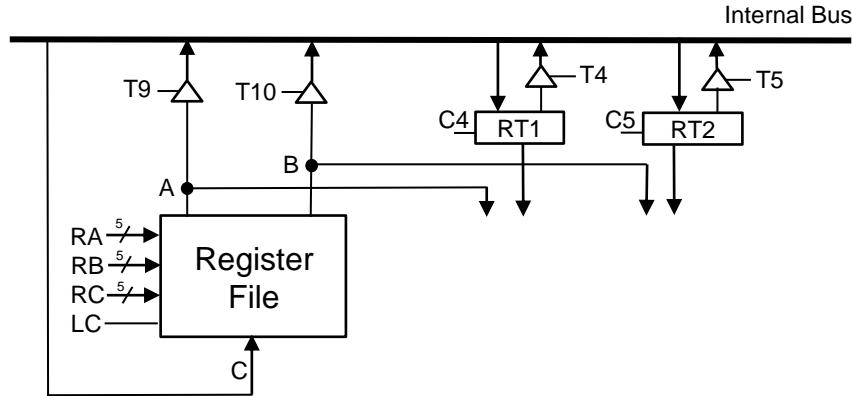
Example elemental operations in registers



▶ **SWAP RI R2**


Elemental Op.	Signals

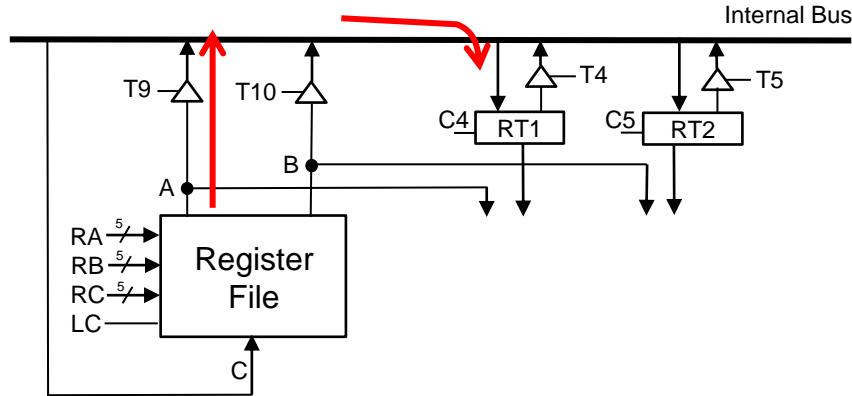Example elemental operations in registers




▶ SWAP RI R2

Elemental Op.	Signals
RT1 ← R1	RA=00001, T9, C4

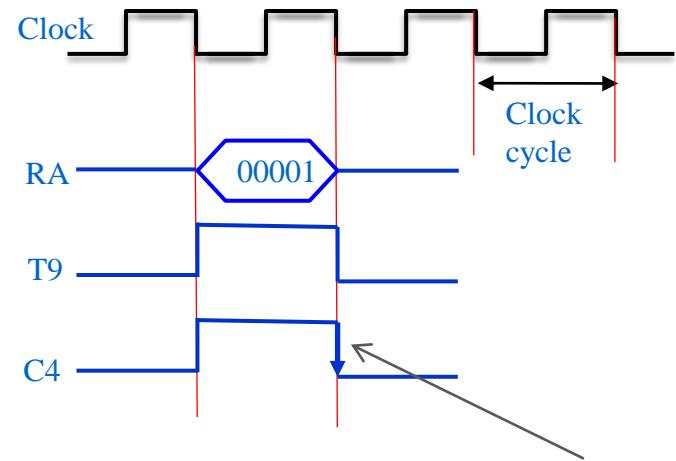

The data is loaded on RT1 on the falling edge.
It will be available on RT1 during the **next** cycle.

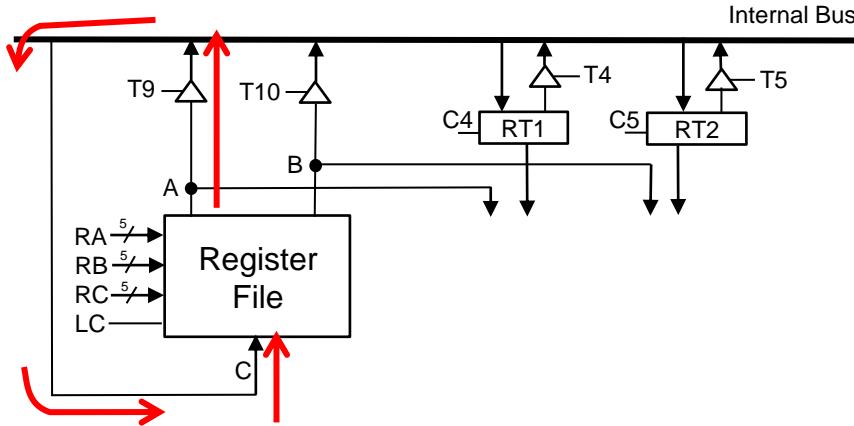
Example elemental operations in registers



▶ SWAP R1 R2


Elemental Op.	Signals
$RT1 \leftarrow R1$	$RA=00001$, T9, C4
$R1 \leftarrow R2$	$RA=2$ (00010), T9, RC=1, LC

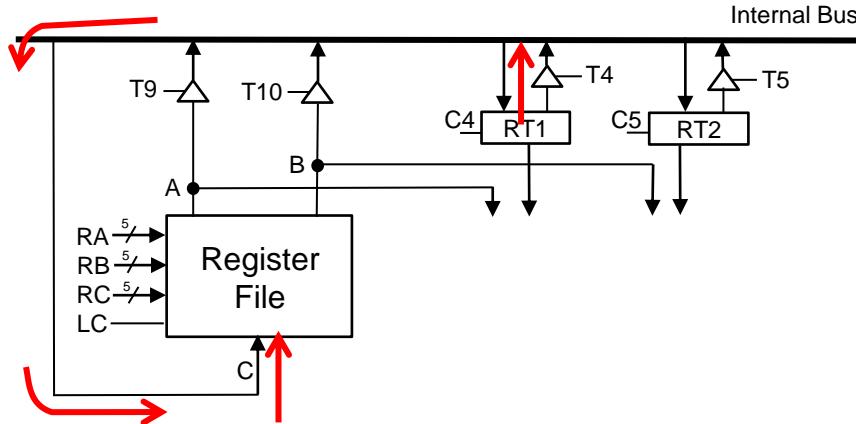Example elemental operations in registers




▶ SWAP RI R2

Elemental Op.	Signals
$RT1 \leftarrow R1$	$RA=00001$, T9, C4
$R1 \leftarrow R2$	$RA=2$ (00010), T9, RC=1, LC
$R2 \leftarrow RT1$	T4, RC=2 (00010), LC

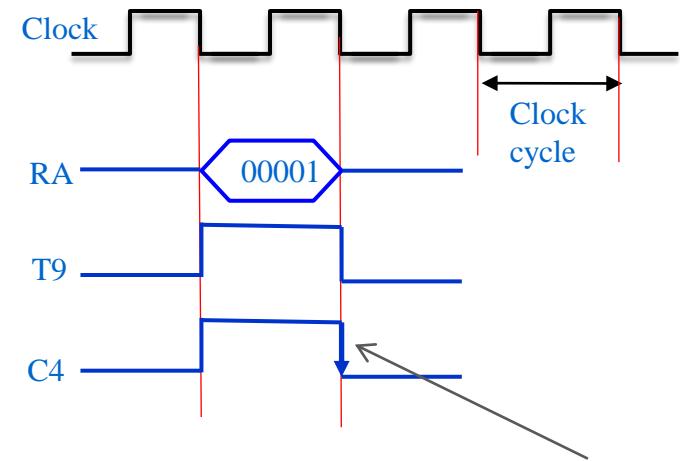


The data is loaded on RT1 on the falling edge.
It will be available on RT1 during the next cycle.

ALU: Arithmetic Logic Unit

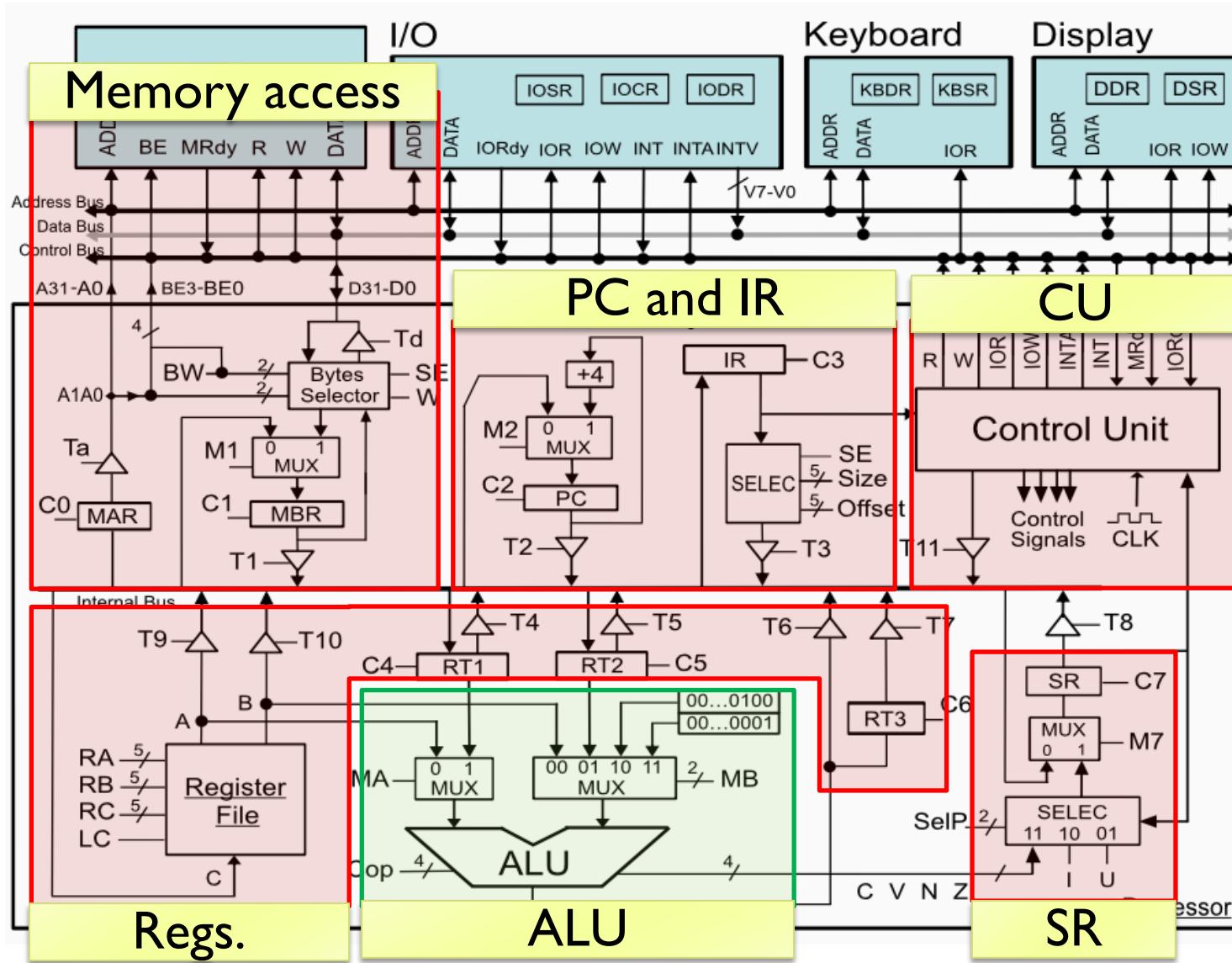

Control Signals

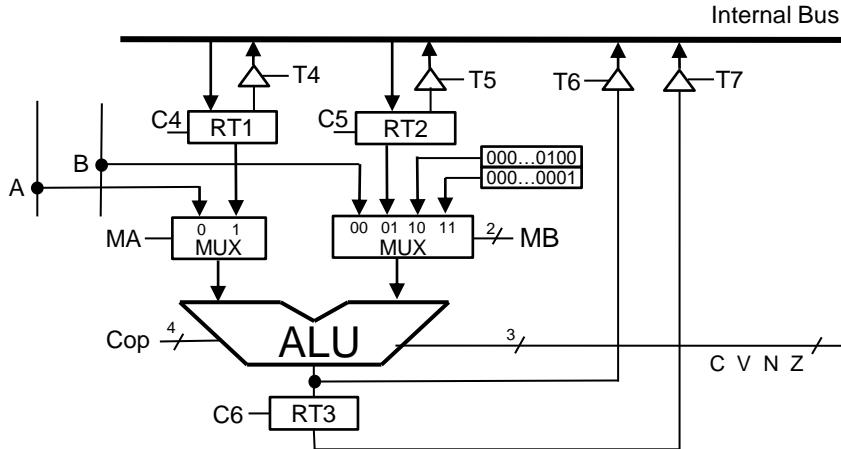


▶ ALU


- ▶ MA - selection of operand A
- ▶ MB - selection of operand B
- ▶ Cop - operation code

Cop (Cop ₃ -Cop ₀)	Operation
0000	NOP
0001	A and B
0010	A or B
0011	not (A)
0100	A xor B
0101	Shift Right Logical (A) B= number of bits to shift
0110	Shift Right Arithmetic (A) B= number of bits to shift
0111	Shift left (A) B= number of bits to shift
1000	Rotate Right (A) B= number of bits to rotate
1001	Rotate Left (A) B= number of bits to rotate
1010	A + B
1011	A - B
1100	A * B (with overflow)
1101	A / B (integer division)
1110	A % B (integer division)
1111	LUI (A)

Control Signals

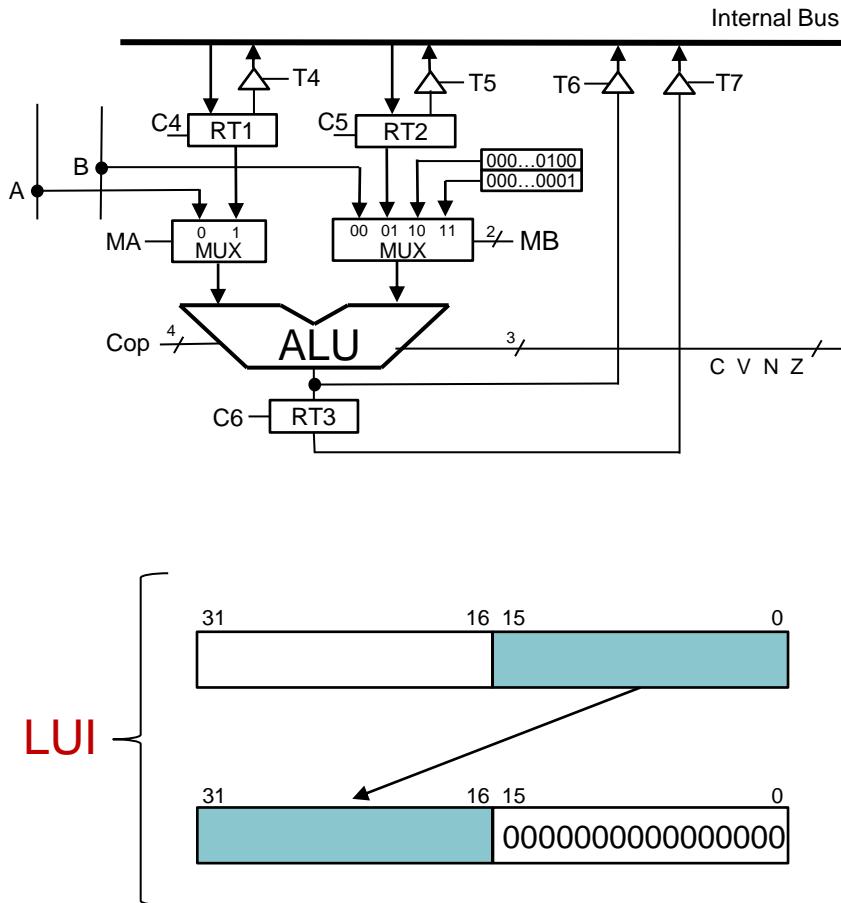


LUI

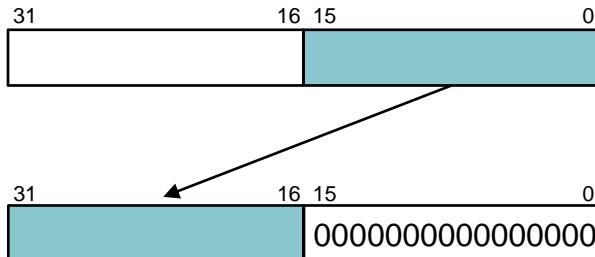

Cop (Cop ₃ -Cop ₀)	Operation
0000	NOP
0001	A and B
0010	A or B
0011	not (A)
0100	A xor B
0101	Shift Right Logical (A) B= number of bits to shift
0110	Shift Right Arithmetic (A) B= number of bits to shift
0111	Shift left (A) B= number of bits to shift
1000	Rotate Right (A) B= number of bits to rotate
1001	Rotate Left (A) B= number of bits to rotate
1010	A + B
1011	A - B
1100	A * B (with overflow)
1101	A / B (integer division)
1110	A % B (integer division)
1111	LUI (A)


Control Signals

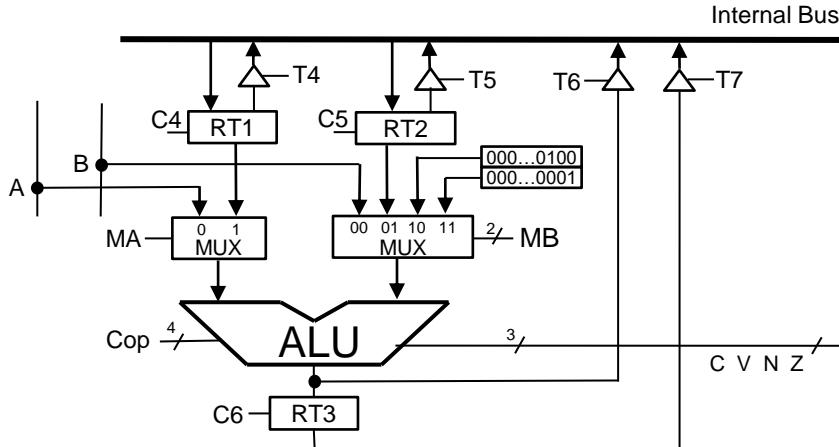

Result	C	V	N	Z
Positive result (0 is considered +)	0	0	0	0
Result == 0	0	0	0	1
Negative result	0	0	1	0
Overflow	0	1	0	0
Division by zero	0	1	0	1
Carrying at bit 32	1	0	0	0

Cop (Cop ₃ -Cop ₀)	Operation
0000	NOP
0001	A and B
0010	A or B
0011	not (A)
0100	A xor B
0101	Shift Right Logical (A) B= number of bits to shift
0110	Shift Right Arithmetic (A) B= number of bits to shift
0111	Shift left (A) B= number of bits to shift
1000	Rotate Right (A) B= number of bits to rotate
1001	Rotate Left (A) B= number of bits to rotate
1010	A + B
1011	A - B
1100	A * B (with overflow)
1101	A / B (integer division)
1110	A % B (integer division)
1111	LUI (A)


Example elemental operations in ALU

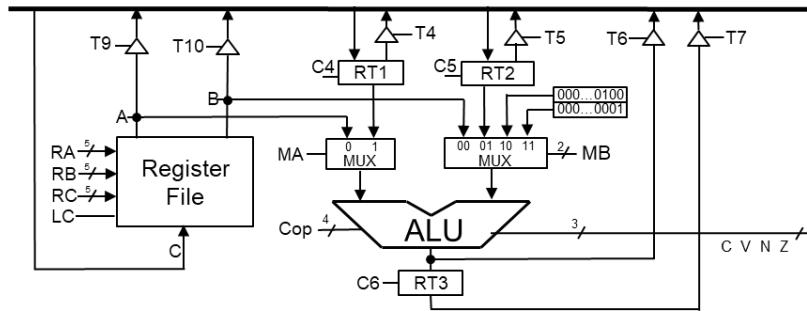

▶ ADD R3 RI R2

Elem. Op.	Signals


Example elemental operations in ALU

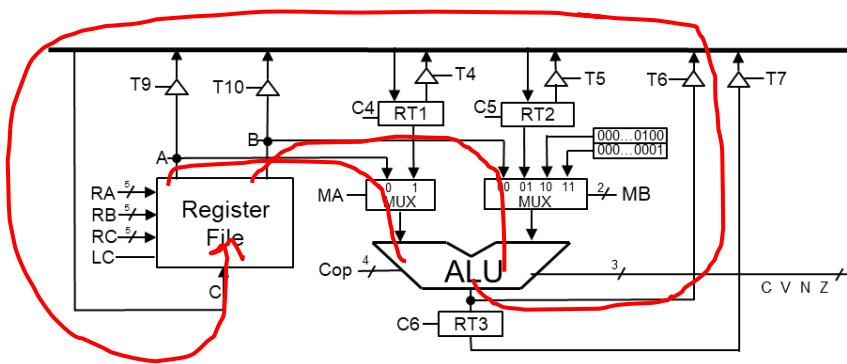

▶ ADD R3 RI R2

Elem. Op.	Signals


Example elemental operations in ALU

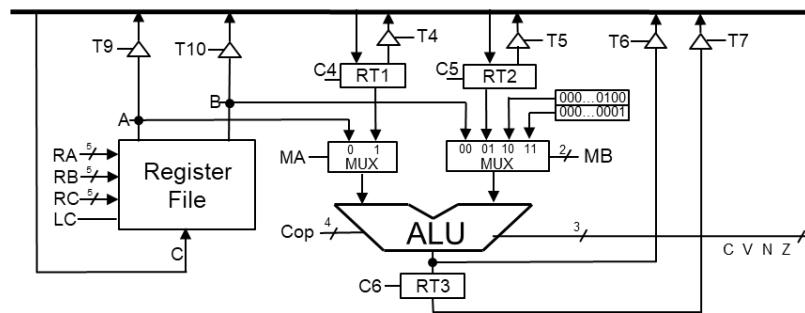

▶ **ADD R3 RI R2**


Elem. Op.	Signals
$R3 \leftarrow R1 + R2$	RA=R1, RB=R2, Cop=+, T6, RC=R3, LC=1

Example elemental operations in ALU

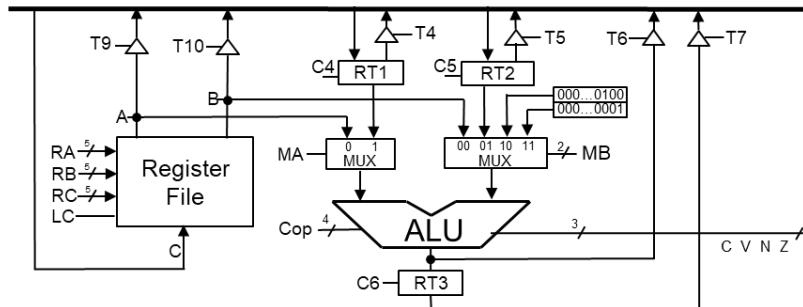

▶ ADD R3 RI R2


Elem. Op.	Signals
$R3 \leftarrow R1 + R2$	RA=R1, RB=R2, Cop=+, T6, RC=R3, LC=1

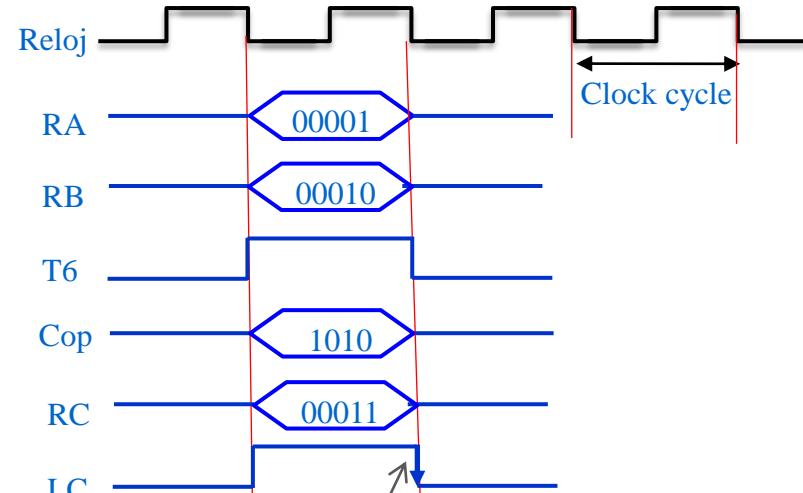

Rest of signals at 0.
The load is performed on R3 on the falling edge.
The data is available in register R3 for the next cycle.

Example

elemental operations in ALU

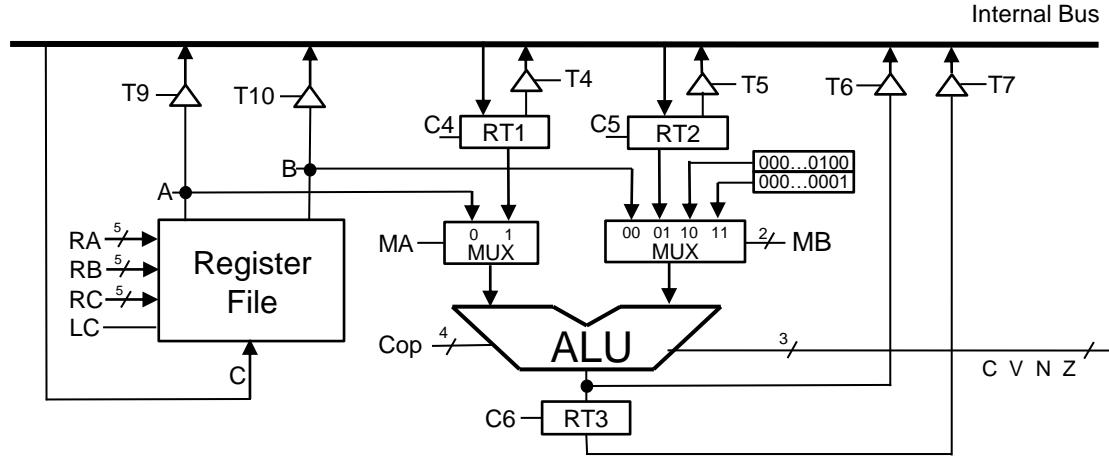


▶ **SWAP RI R2**

▶ **SWAP RI, R2 without R_{tmp}**

Elem. Op.	Signals
RT1 ← R1	RA=1, T9, C4
R1 ← R2	RA=2, T9, RC=1, LC
R2 ← RT1	T4, RC=2, LC

Example

elemental operations in ALU

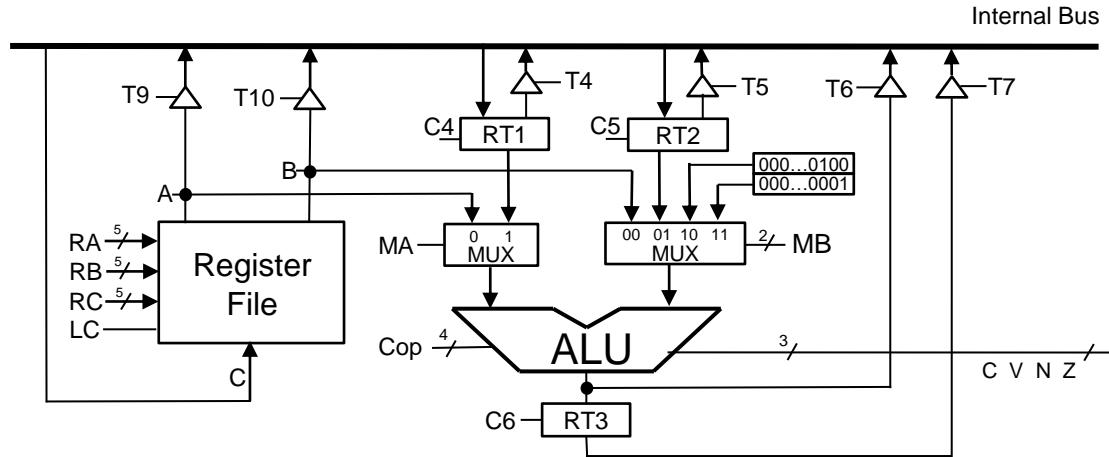

▶ **SWAP RI R2**


Elem. Op.	Signals
$RT1 \leftarrow R1$	$RA=1, T9, C4$
$R1 \leftarrow R2$	$RA=2, T9, RC=1, LC$
$R2 \leftarrow RT1$	$T4, RC=2, LC$

▶ **SWAP RI, R2 without R_{tmp}**

Elem. Op.
$R1 \leftarrow R1 \wedge R2$
$R2 \leftarrow (R1 \wedge R2) \wedge R2$
$R1 \leftarrow (R1 \wedge R2) \wedge R1$

Example

elemental operations in ALU

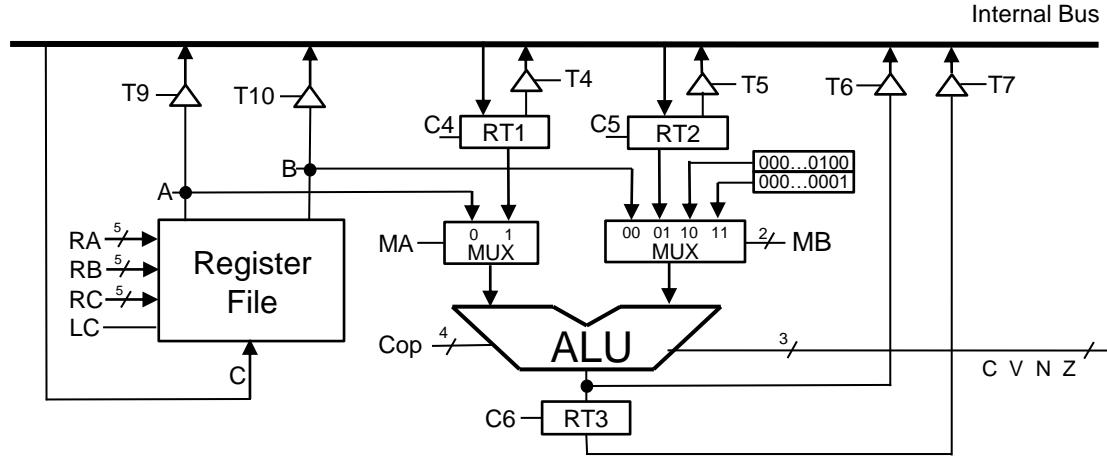

▶ **SWAP RI R2**


Elem. Op.	Signals
$RT1 \leftarrow R1$	$RA=1, T9, C4$
$R1 \leftarrow R2$	$RA=2, T9, RC=1, LC$
$R2 \leftarrow RT1$	$T4, RC=2, LC$

▶ **SWAP RI, R2 without R_{tmp}**

Elem. Op.	Signals
$R1 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=1, LC$
$R2 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=2, LC$
$R1 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=1, LC$

Example

elemental operations in ALU

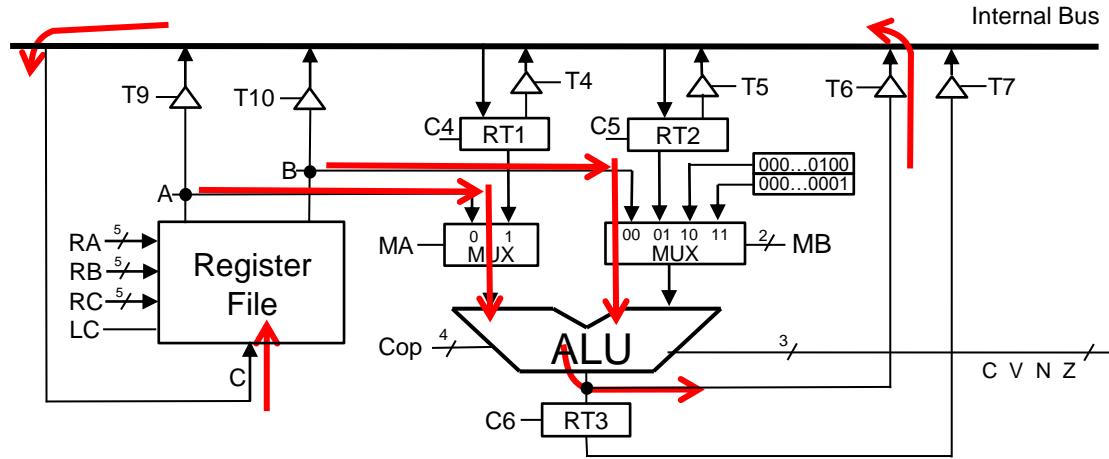

▶ **SWAP RI R2**


Elem. Op.	Signals
$RT1 \leftarrow R1$	RA=1, T9, C4
$R1 \leftarrow R2$	RA=2, T9, RC=1, LC
$R2 \leftarrow RT1$	T4, RC=2, LC

▶ **SWAP RI, R2 without R_{tmp}**

Elem. Op.	Signals
$R1 \leftarrow R1 \wedge R2$	RA=1, RB=2, Cop= \wedge , T6, RC=1, LC
$R2 \leftarrow R1 \wedge R2$	RA=1, RB=2, Cop= \wedge , T6, RC=2, LC
$R1 \leftarrow R1 \wedge R2$	RA=1, RB=2, Cop= \wedge , T6, RC=1, LC

Example

elemental operations in ALU

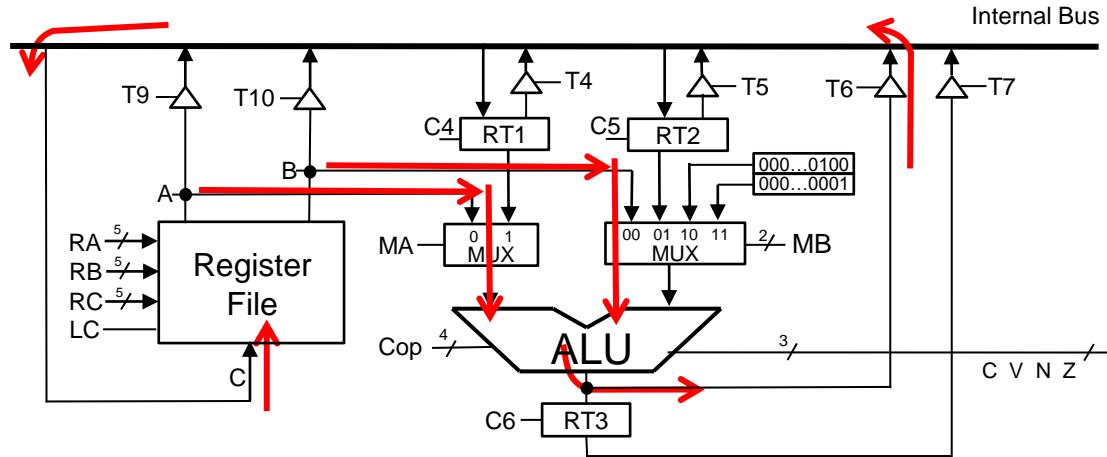

▶ **SWAP RI R2**


Elem. Op.	Signals
$RT1 \leftarrow R1$	$RA=1, T9, C4$
$R1 \leftarrow R2$	$RA=2, T9, RC=1, LC$
$R2 \leftarrow RT1$	$T4, RC=2, LC$

▶ **SWAP RI, R2 without R_{tmp}**

Elem. Op.	Signals
$R1 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=1, LC$
$R2 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=2, LC$
$R1 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=1, LC$

Example

elemental operations in ALU

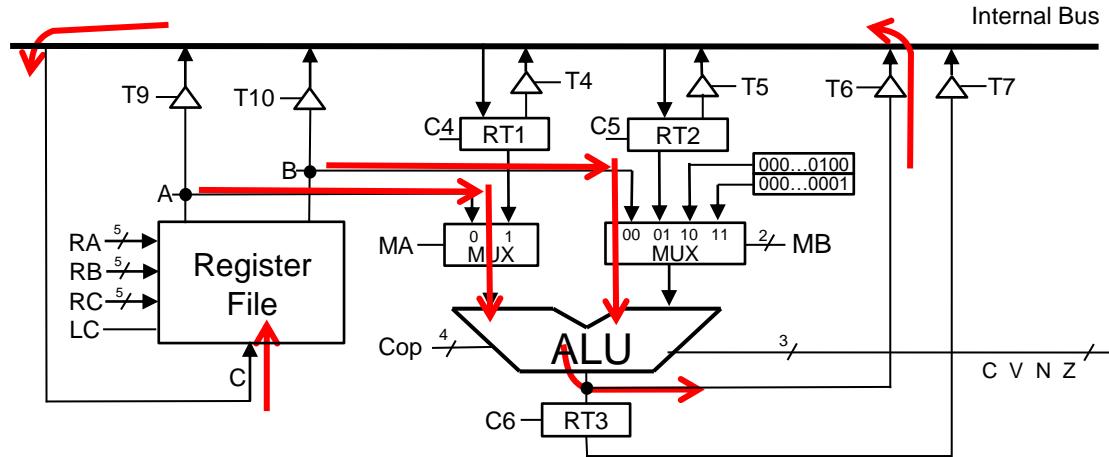


▶ **SWAP RI R2**

Elem. Op.	Signals
$RT1 \leftarrow R1$	$RA=1, T9, C4$
$R1 \leftarrow R2$	$RA=2, T9, RC=1, LC$
$R2 \leftarrow RT1$	$T4, RC=2, LC$

▶ **SWAP RI, R2 without R_{tmp}**


Elem. Op.	Signals
$R1 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=1, LC$
$R2 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=2, LC$
$R1 \leftarrow R1 \wedge R2$	$RA=1, RB=2, Cop=\wedge, T6, RC=1, LC$

Elemental Processor: memory access

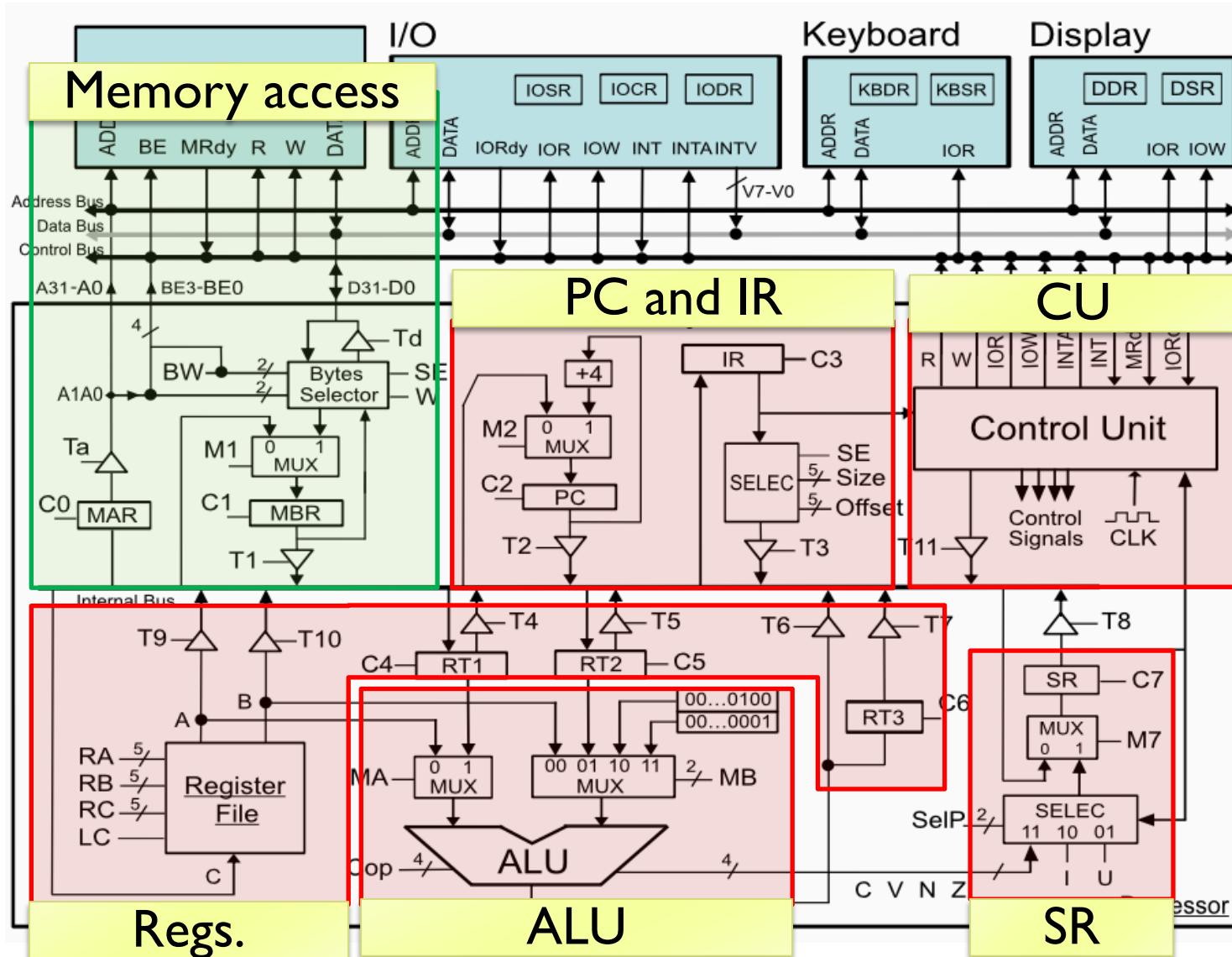

Control Signals

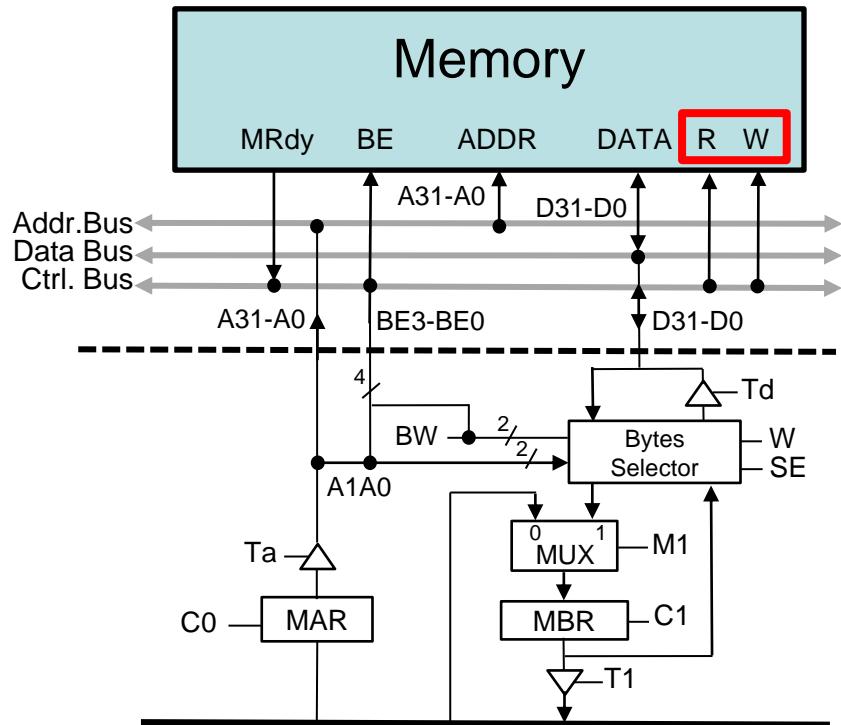
- ▶ **Main Memory**
 - ▶ R – Read
 - ▶ W – Write



Nomenclature:

- MAR -> Address register
- MBR -> Data register

Control Signals

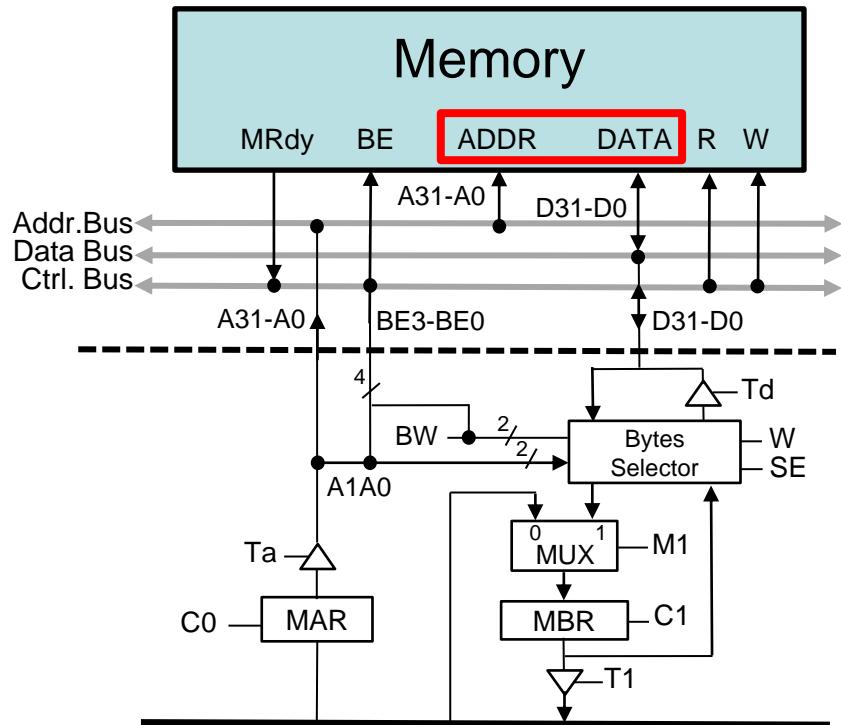


Main Memory

- ▶ R – Read
- ▶ W – Write
- ▶ DATA – data from/to memory
- ▶ ADDR – address

Nomenclature:

- MAR -> Address register
- MBR -> Data register

Control Signals

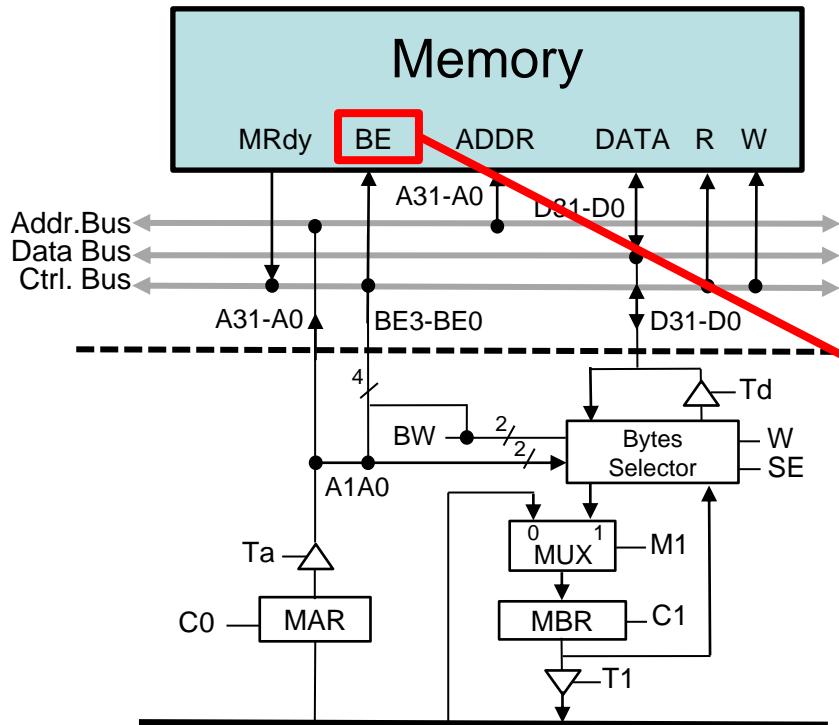

Nomenclature:

- MAR -> Address register
- MBR -> Data register

Main Memory

- ▶ R – Read
- ▶ W – Write
- ▶ DATA – data from/to memory
- ▶ ADDR – address
- ▶ $BE3-BE0 = A1A0 + BW$
 - ▶ Access size (byte, word, half word)

BW: byte selector


It selects which bytes are stored in MBR while reading and copy to the bus on writes.

- ▶ **BW=0:** access to **byte**
- ▶ **BW=01:** access to **half word**
- ▶ **BW=11:** **word** access

SE: sign extension

- ▶ **0:** does **not extend the sign** in smaller accesses of a word
- ▶ **1:** **extends the sign** in smaller word accesses

Control Signals

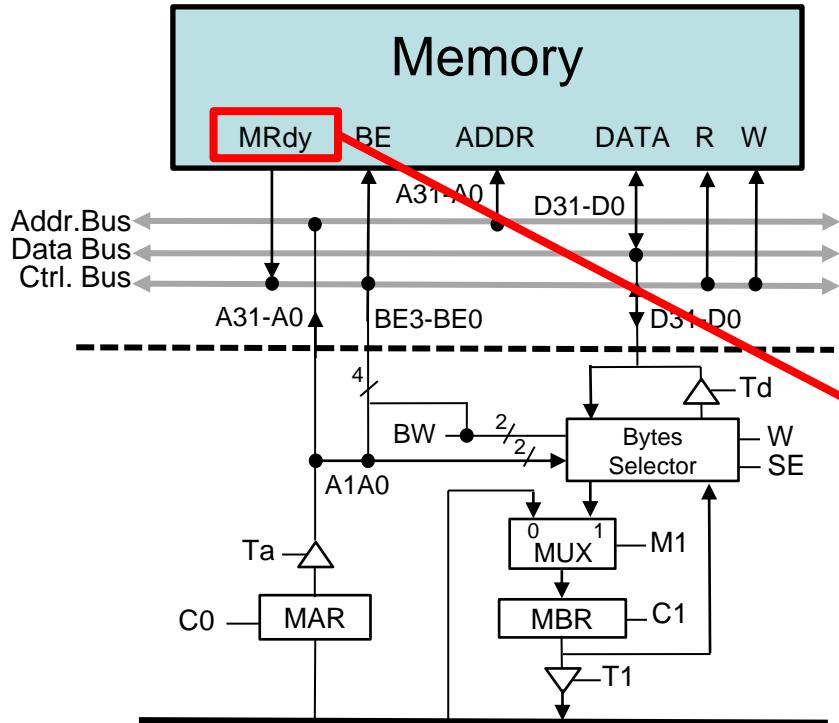

Nomenclature:

- MAR -> Address register
- MBR -> Data register

Main Memory

- ▶ R – Read
- ▶ W – Write
- ▶ DATA – data from/to memory
- ▶ ADDR – address
- ▶ $BE_3 - BE_0 = A1A0 + BW$
 - ▶ Access size (byte, word, half word)
- ▶ MRdy – operation ended
 - ▶ [only in asynchronous]


Synchronous:

- ▶ Memory requires a certain number of cycles for all operations.

Asynchronous:

- ▶ Non fixed number of clock cycles for memory operations.
- ▶ The memory indicates when the operation ends

Control Signals

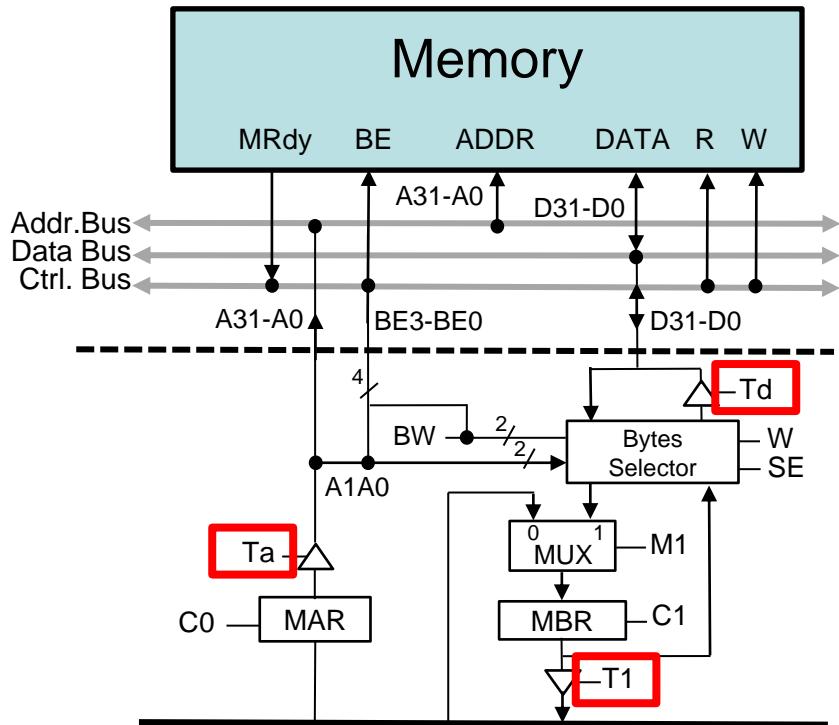

Main Memory

- ▶ R – Read
- ▶ W – Write
- ▶ DATA – data from/to memory
- ▶ ADDR – address
- ▶ $BE3-BE0 = A1A0 + BW$
 - ▶ Access size (byte, word, half word)
- ▶ MRdy – operation ended
 - [only in asynchronous]


MAR & MBR

- ▶ Ta – output of MAR to the address bus
- ▶ Td – MBR output to data bus
- ▶ TI – MBR output to internal bus

Nomenclature:

- MAR -> Address register
- MBR -> Data register

Control Signals

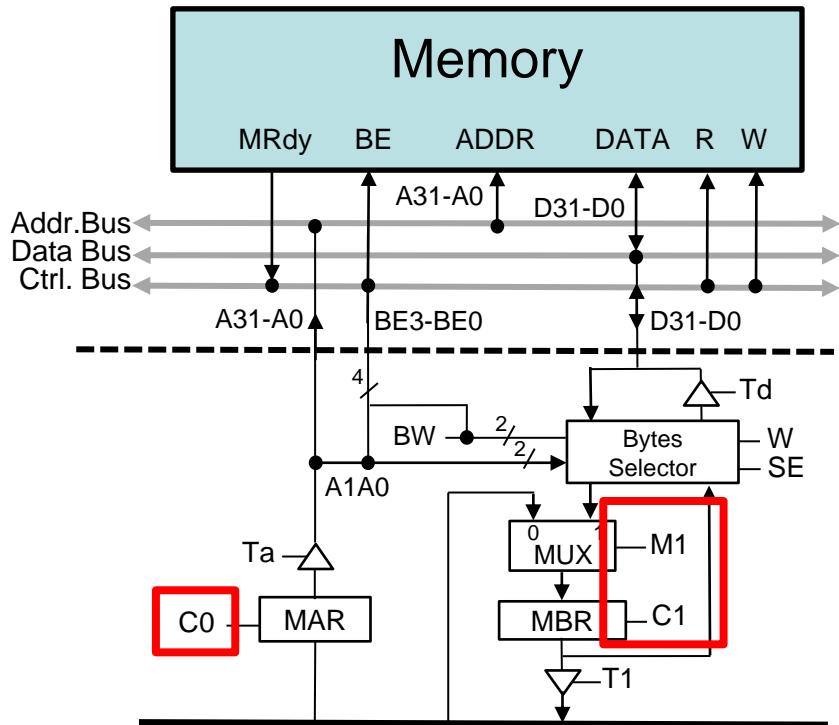

Nomenclature:

- MAR -> Address register
- MBR -> Data register

Main Memory


- ▶ R – Read
- ▶ W – Write
- ▶ DATA – data from/to memory
- ▶ ADDR – address
- ▶ $BE3-BE0 = A1A0 + BW$
 - ▶ Access size (byte, word, half word)
- ▶ MRdy – operation ended
 - ▶ [only in asynchronous]

MAR & MBR

- ▶ Ta – output of MAR to the address bus
- ▶ Td – MBR output to data bus
- ▶ TI – MBR output to internal bus
- ▶ M1 – selection for MBR: memory or internal bus
- ▶ CI – from data bus to MBR
- ▶ C0 – from internal bus to MAR

Control Signals

summary

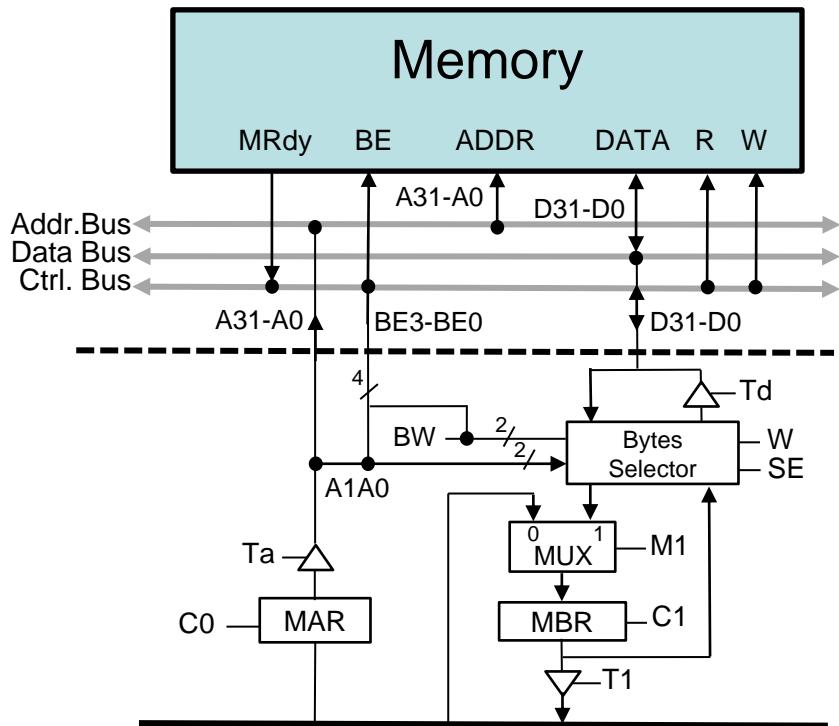

Nomenclature:

- MAR -> Address register
- MBR -> Data register

Main Memory


- ▶ R – Read
- ▶ W – Write
- ▶ DATA – data from/to memory
- ▶ ADDR – address
- ▶ $BE3-BE0 = A1A0 + BW$
 - ▶ Access size (byte, word, half word)
- ▶ MRdy – operation ended
 - ▶ [only in asynchronous]

MAR & MBR

- ▶ Ta – output of MAR to the address bus
- ▶ Td – MBR output to data bus
- ▶ TI – MBR output to internal bus
- ▶ MI – selection for MBR:
 - ▶ memory or internal bus
- ▶ CI – from data bus to MBR
- ▶ C0 – from internal bus to MAR

Example elemental operations in main memory


▶ Reading a word

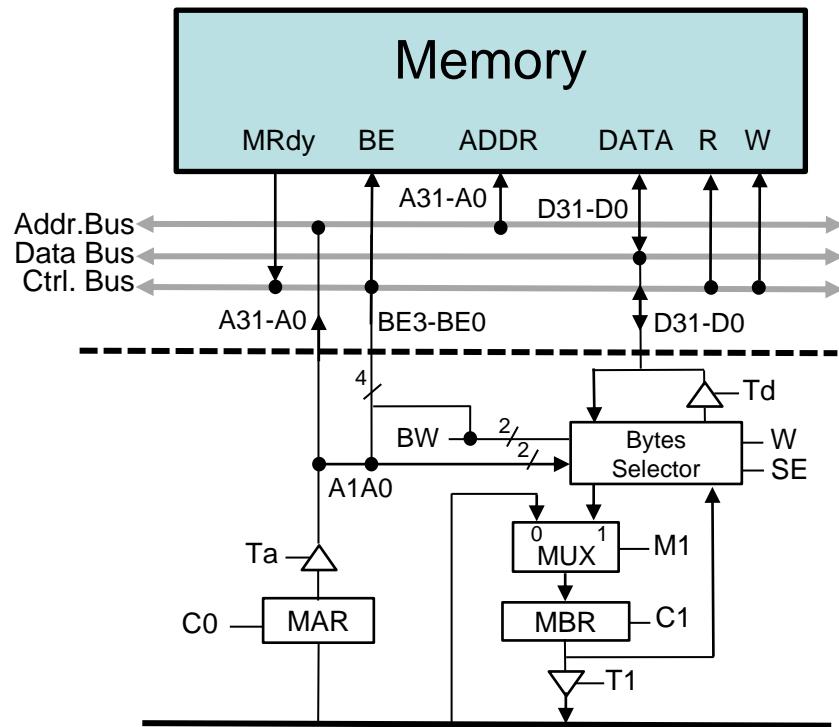

Example

access to 1 cycle synchronous main memory

▶ Read

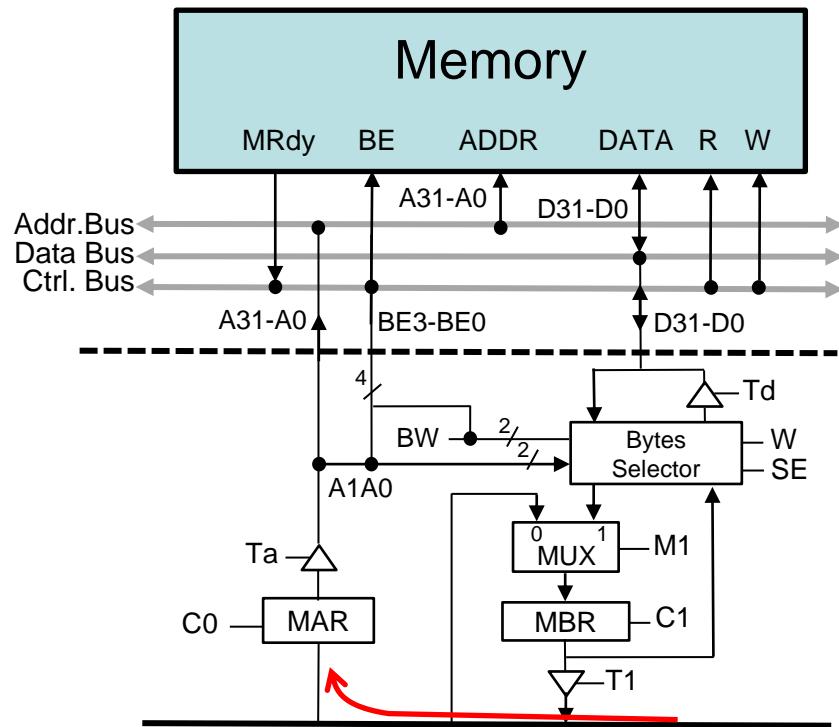


Elem. Op.	Signals
MAR ← <address>	..., C0

Example

access to 1 cycle synchronous main memory


▶ Read

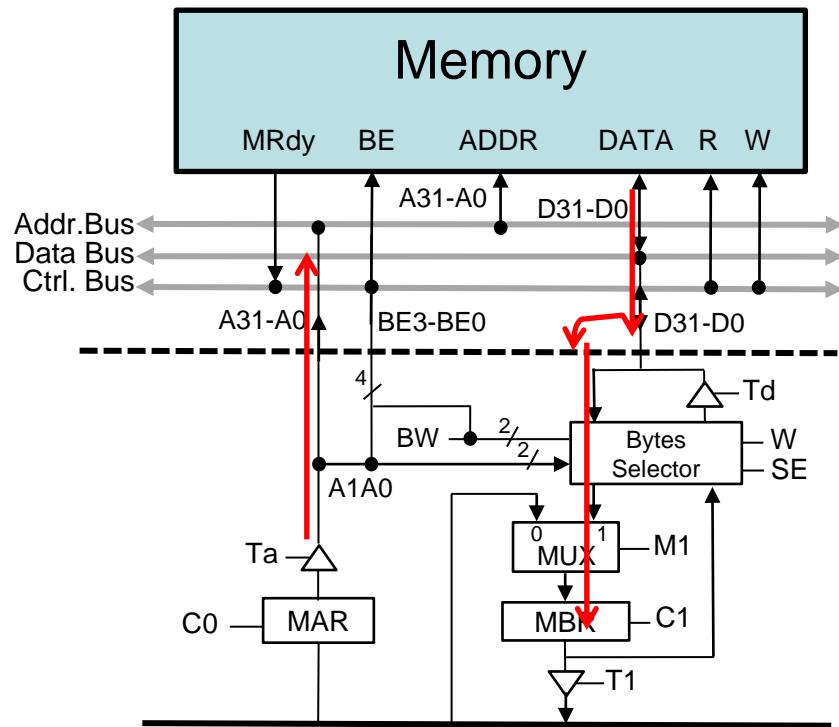

Elem. Op.	Signals
MAR ← <address>	..., C0
MBR ← MP[MAR]	Ta, R, M1, C1, BW=11

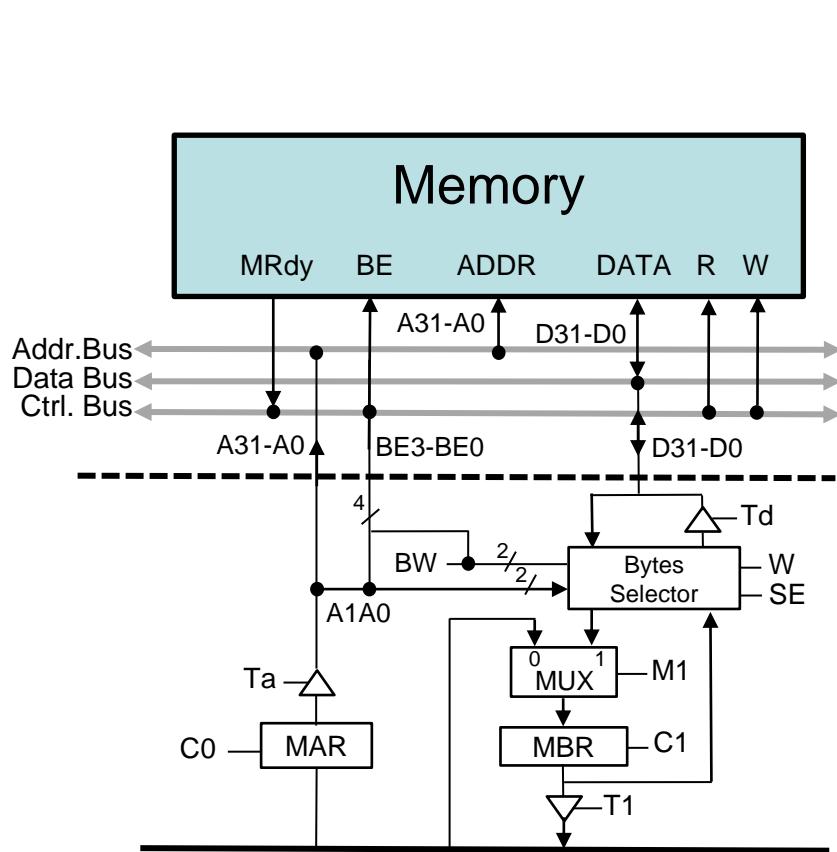Example

access to 1 cycle synchronous main memory




▶ Read

Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow MP[MAR]	Ta, R, M1, C1, BW=11

▶ Writing a word

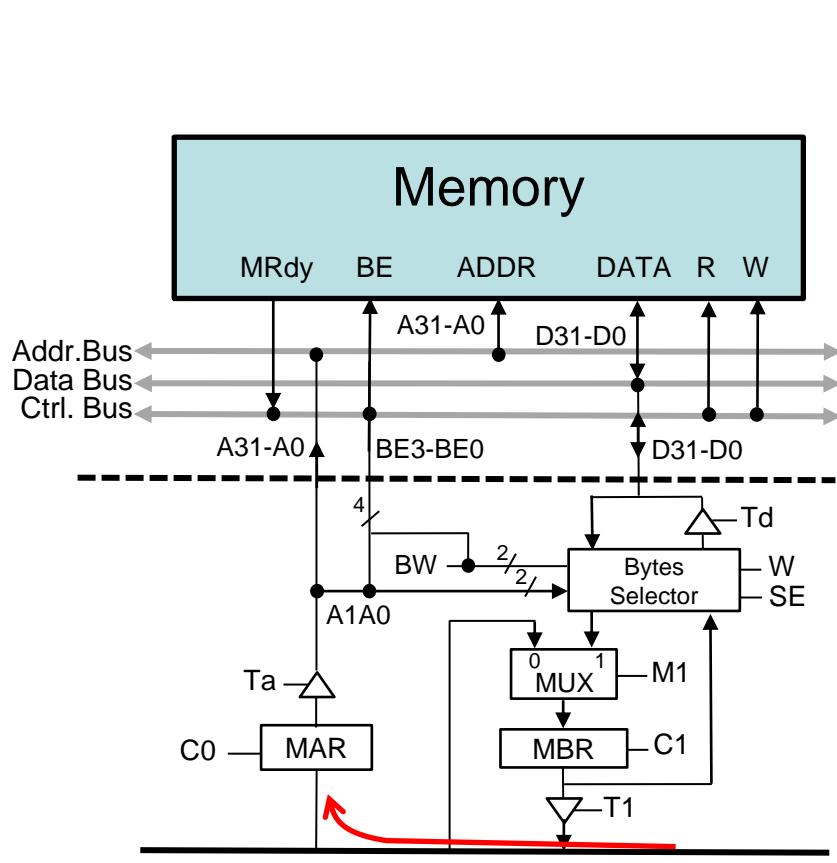Example

access to 1 cycle synchronous main memory



▶ Read


Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow MP[MAR]	Ta, R, M1, C1, BW=11

▶ Write

Elem. Op.	Signals
MAR \leftarrow <address>	..., C0

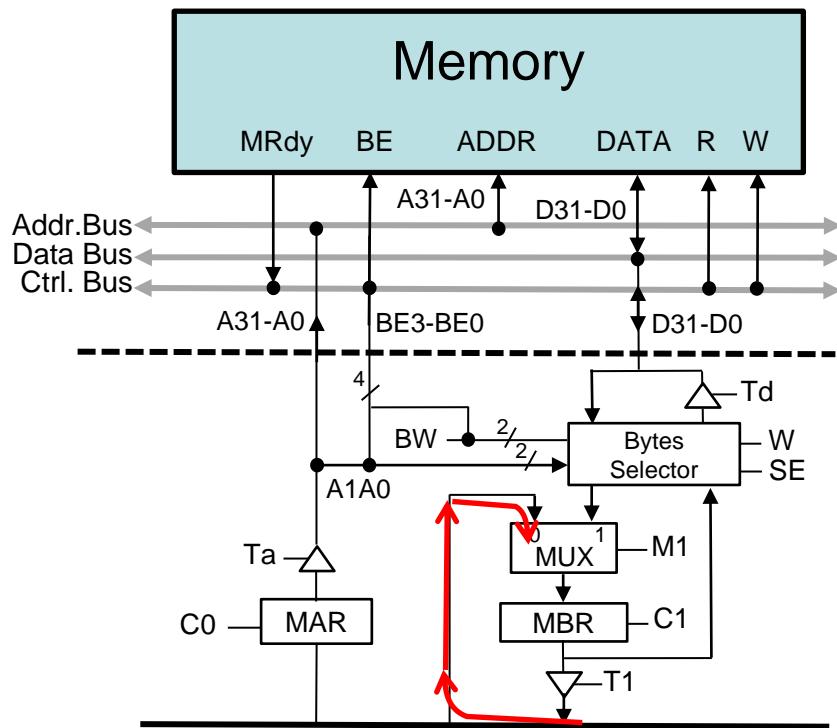Example

access to 1 cycle synchronous main memory



▶ Read


Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow MP[MAR]	Ta, R, M1, C1, BW=11

▶ Write

Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow <data>	..., C1

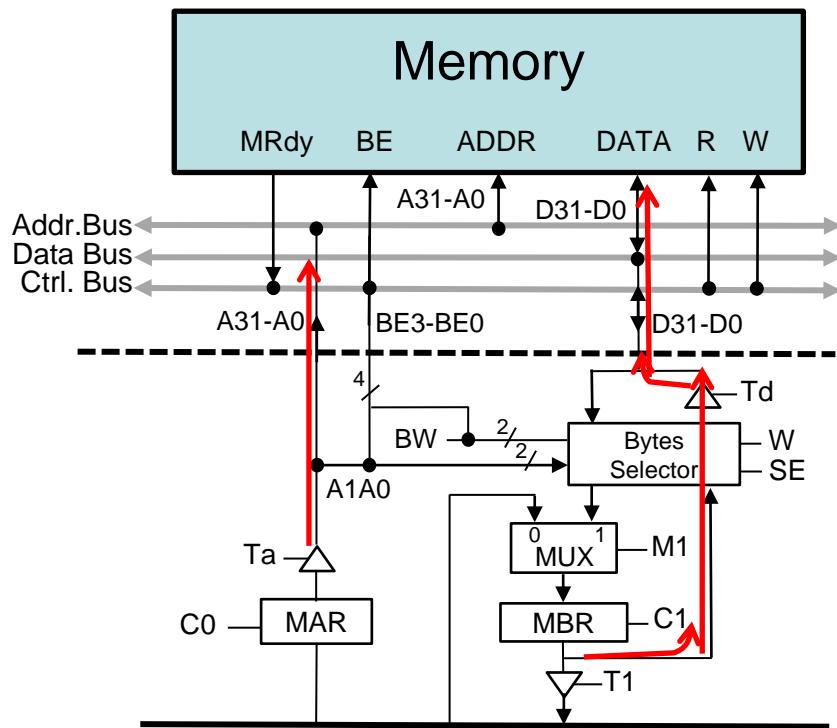Example

access to 1 cycle synchronous main memory



▶ Read


Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow MP[MAR]	Ta, R, M1, C1, BW=11

▶ Write

Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow <data>	..., C1
Writing cycle	Ta, Td, W, BW=11

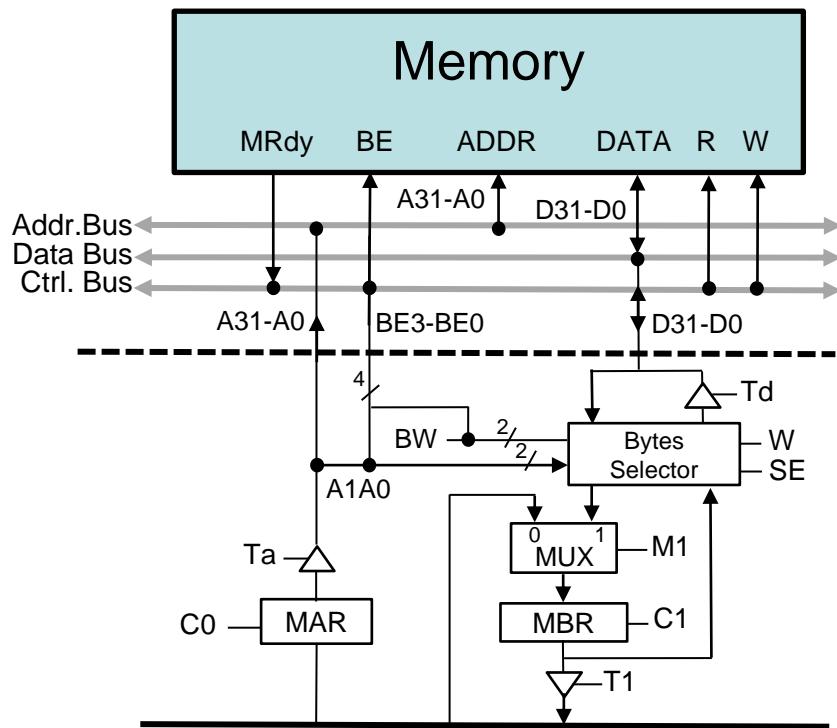Example

access to 1 cycle synchronous main memory



▶ Read

Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow MP[MAR]	Ta, R, M1, C1, BW=11


▶ Write

Elem. Op.	Signals
MAR \leftarrow <address>	..., C0
MBR \leftarrow <data>	..., C1
Writing cycle	Ta, Td, W, BW=11

Example

access to 2 cycle synchronous main memory

▶ Reading a word

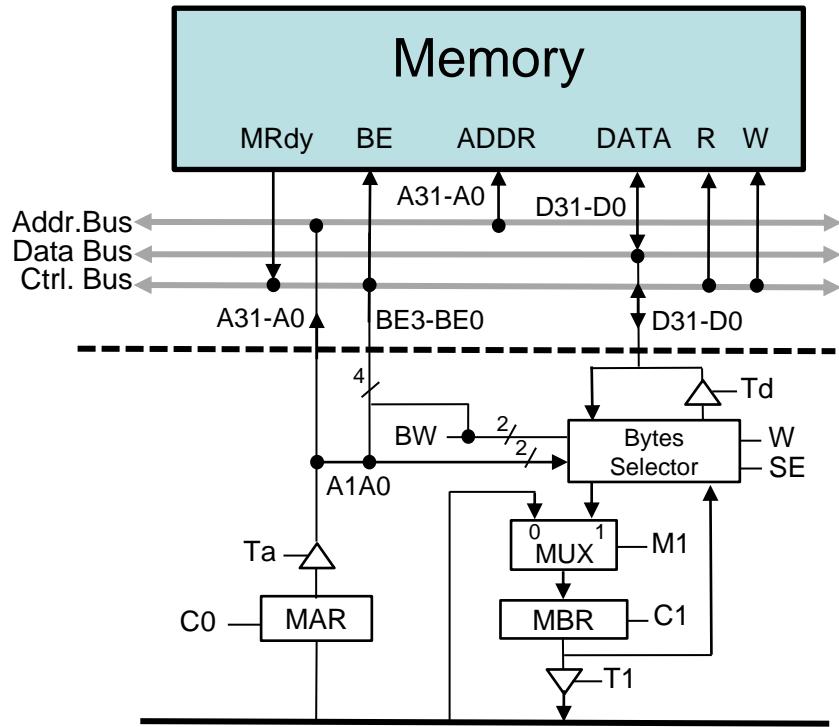

Elem. Op.	Signals
MAR ← <address>	..., C0
Reading cycle	Ta, R,
Reading cycle, MBR ← MP[MAR]	Ta, R, M1, C1, BW=11


BE (Byte-Enable) signals for reading

Bytes in memory				Byte-Enable				Output to bus			
D31-D24	D23-D16	D15-D8	D7-D0	BE3	BE2	BE1	BE0	D31-D24	D23-D16	D15-D8	D7-D0
Byte 3	Byte 2	Byte 1	Byte 0	0	0	0	0	---	---	---	Byte 0
Byte 3	Byte 2	Byte 1	Byte 0	0	0	0	1	---	---	Byte 1	---
Byte 3	Byte 2	Byte 1	Byte 0	0	0	1	0	--	Byte 2	---	---
Byte 3	Byte 2	Byte 1	Byte 0	0	0	1	1	Byte 3	---	---	---
Byte 3	Byte 2	Byte 1	Byte 0	0	1	0	X	---	---	Byte 1	Byte 0
Byte 3	Byte 2	Byte 1	Byte 0	0	1	1	X	Byte 3	Byte 2	---	---
Byte 3	Byte 2	Byte 1	Byte 0	1	1	X	X	Byte 3	Byte 2	Byte 1	Byte 0

BE (Byte-Enable) signals for writing

Data in bus				Byte-Enable				Bytes written in memory			
D31-D24	D23-D16	D15-D8	D7-D0	BE3	BE2	BE1	BE0	D31-D24	D23-D16	D15-D8	D7-D0
Byte 3	Byte 2	Byte 1	Byte 0	0	0	0	0	---	---	---	Byte 0
Byte 3	Byte 2	Byte 1	Byte 0	0	0	0	1	---	---	Byte 1	---
Byte 3	Byte 2	Byte 1	Byte 0	0	0	1	0	--	Byte 2	---	---
Byte 3	Byte 2	Byte 1	Byte 0	0	0	1	1	Byte 3	---	---	---
Byte 3	Byte 2	Byte 1	Byte 0	0	1	0	X	---	---	Byte 1	Byte 0
Byte 3	Byte 2	Byte 1	Byte 0	0	1	1	X	Byte 3	Byte 2	---	---
Byte 3	Byte 2	Byte 1	Byte 0	1	1	X	X	Byte 3	Byte 2	Byte 1	Byte 0

Memory Access size

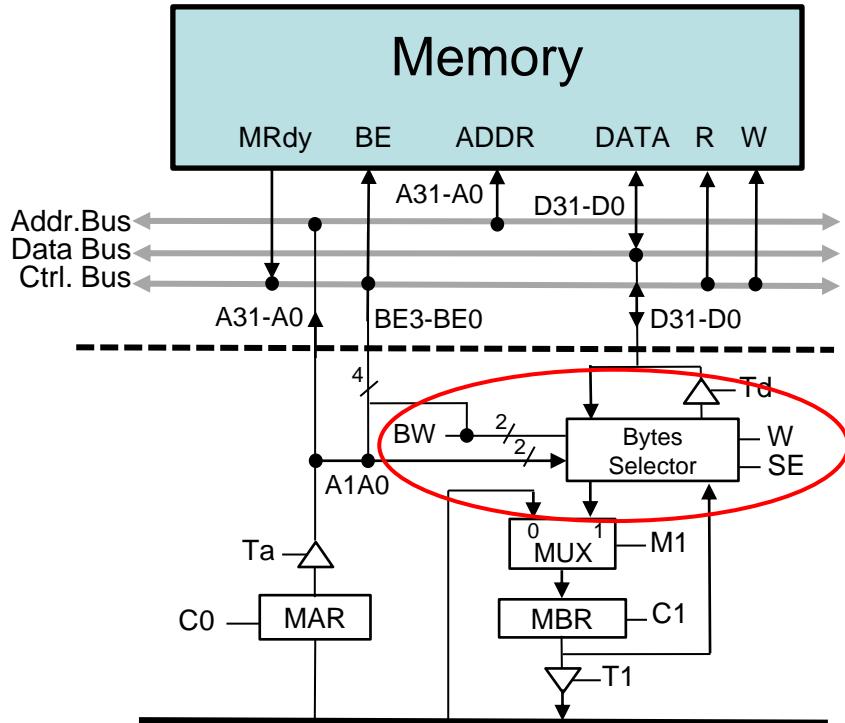


Nomenclature:

- MAR -> Addresss register
- MBR -> Data register

- ▶ Byte Selector: selects which bytes are stored in MBR while reading and copy to the bus on writes.
 - ▶ **BW=0**: access to **byte**
 - ▶ **BW=01**: access to **half word**
 - ▶ **BW=11**: **word** access
- ▶ SE: sign extension
 - ▶ **0**: does **not extend the sign** in smaller accesses of a word
 - ▶ **1**: **extends the sign** in smaller word accesses


Elemental Processor: PC and IR

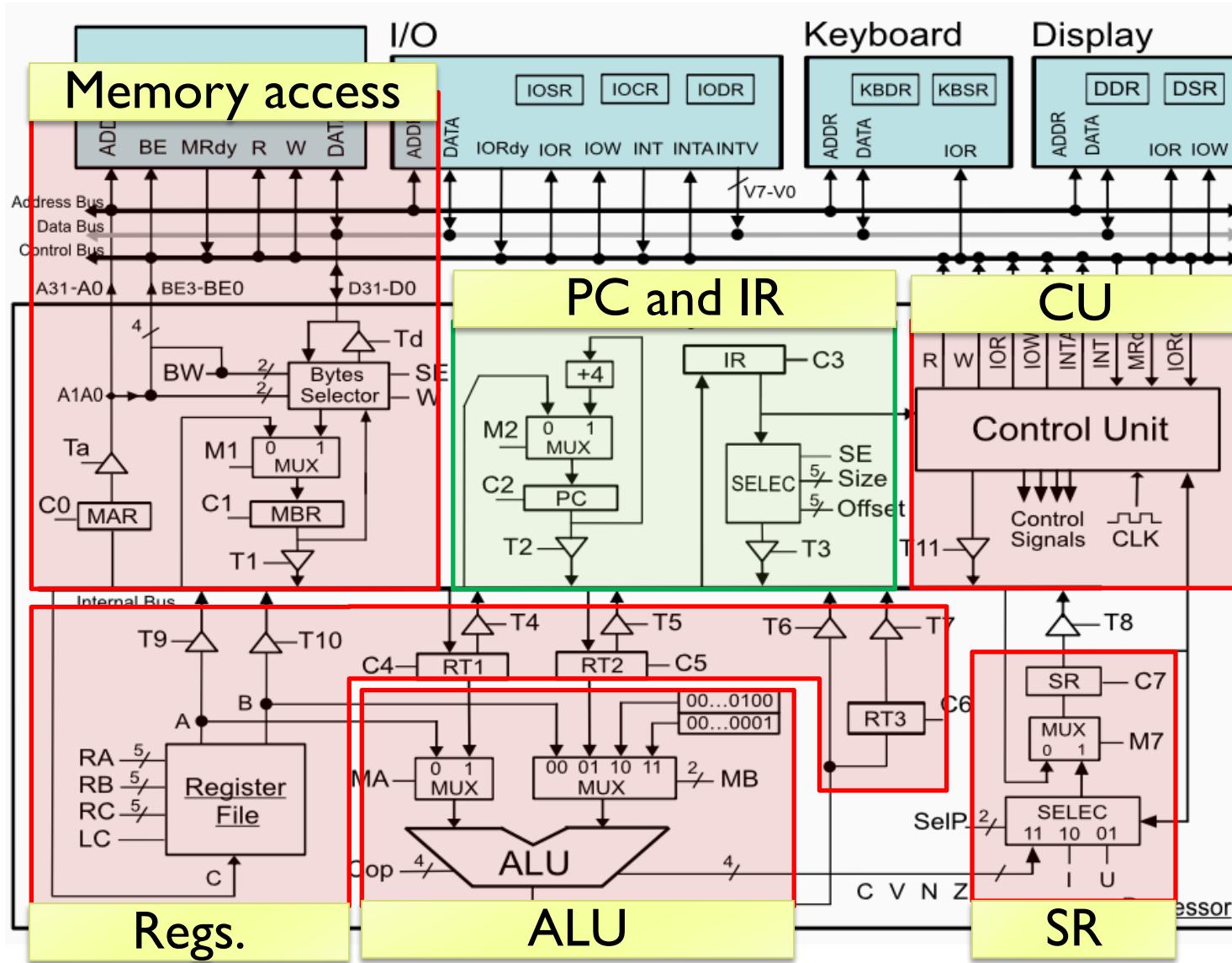


PC: Program Counter

▶ PC

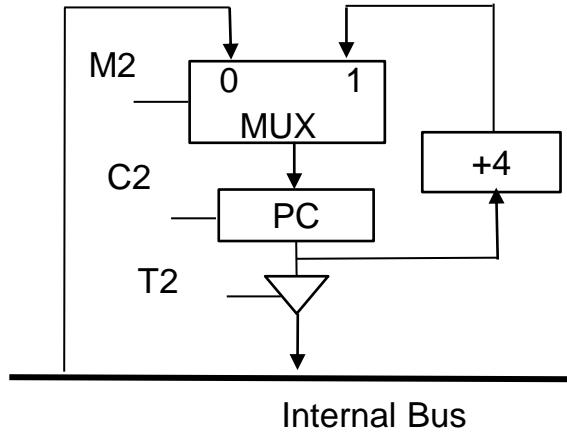- ▶ C2 – load value into PC
- ▶ T2 – from PC to internal bus



PC Mux: IB/PC+4

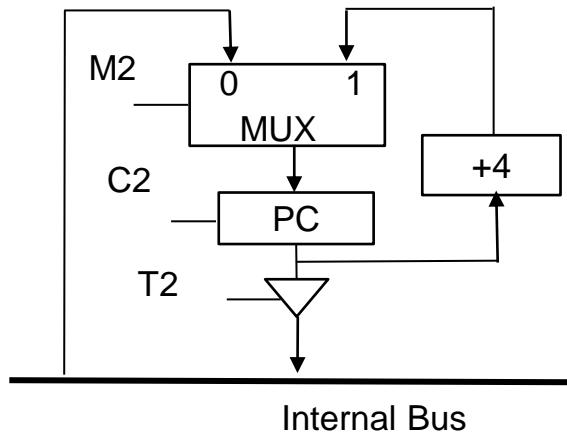


▶ PC

- ▶ C2 – load value into PC
- ▶ T2 – from PC to internal bus

- ▶ C2, M2
 - ▶ $PC \leftarrow PC + 4$
- ▶ C2, M2=0
 - ▶ $PC \leftarrow <\text{internal bus}>$



IR: Instruction register

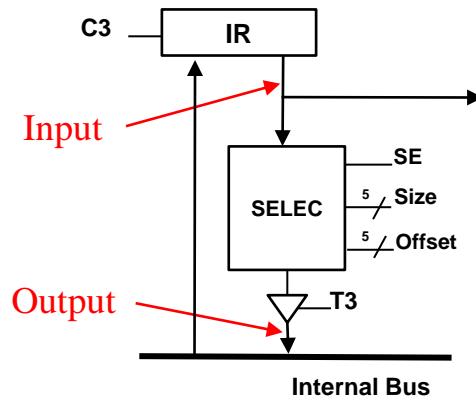


► IR:

- ▶ C3 - from internal bus to IR
- ▶ SELEC: IR content to the bus
 - Offset: displacement
 - Start bit (less significant)
 - Size: Size
 - Number of bits
 - SE: sign extension

SELEC: selector circuit

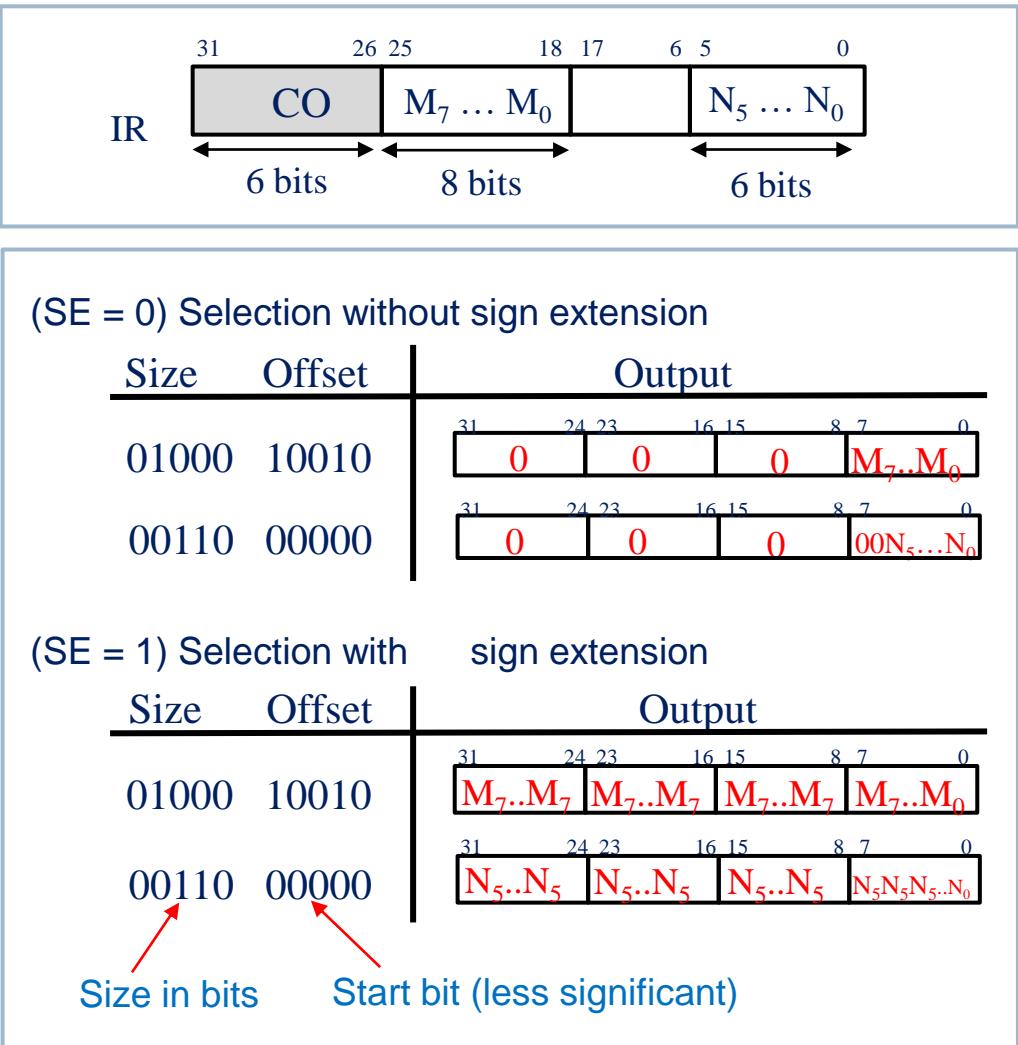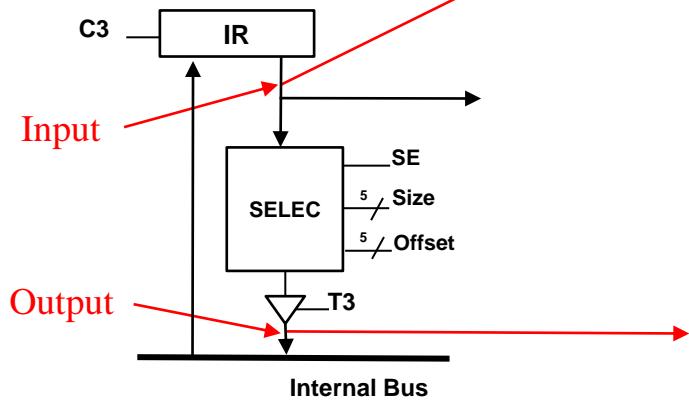

Execution of j addr

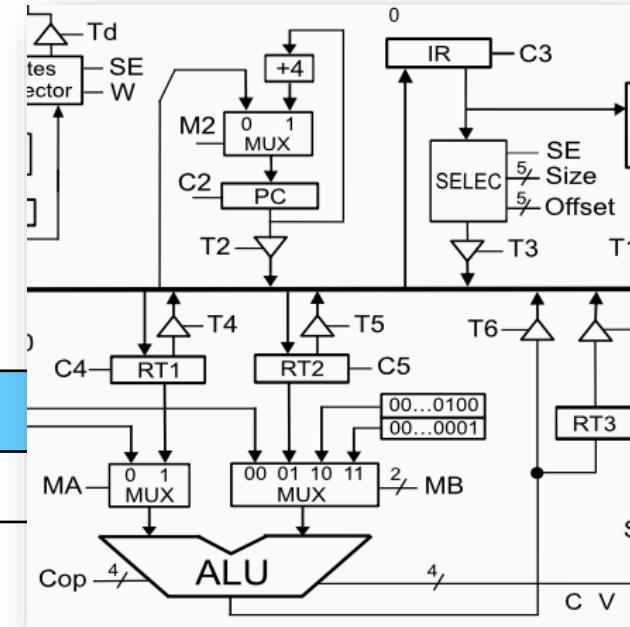

Cycle	Elem. Op.	Control Signals


Execution of j addr

TIP

General phases:

- A. Fetch + Decode
- B. Fetch operands
- C. Execution
- D. Store results

Cycle	Elem. Op.	Control Signals

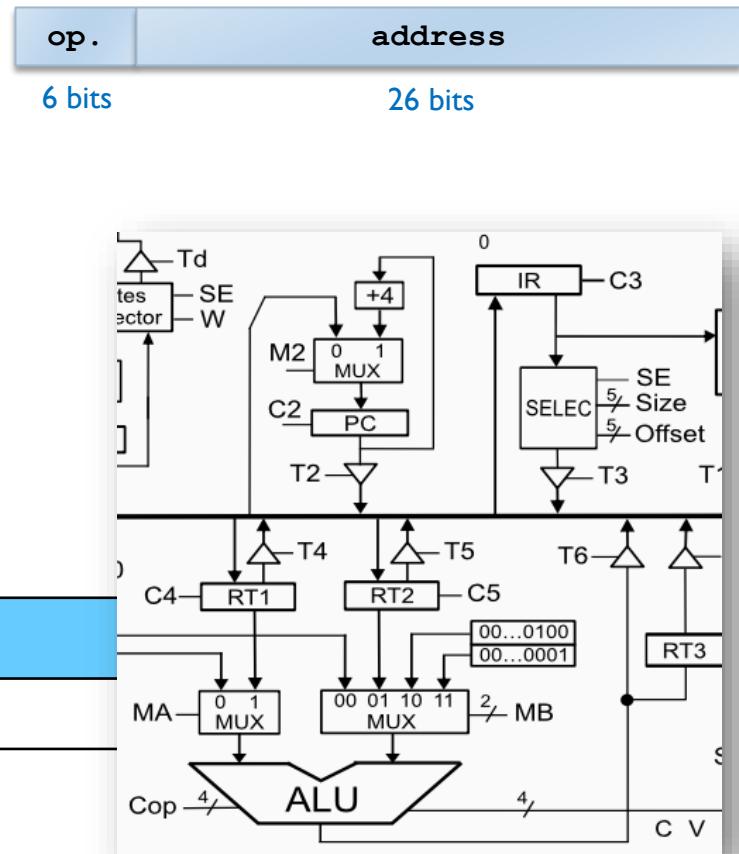


Execution of j addr

TIP


Not possible in the same clock cycle:

1. To passthrough a register (~~C4, MA=1~~)
2. To send several values to a bus (~~T4, T5~~)
3. To set a datapath if the circuitry does not enable it (~~IDB \rightarrow RT3~~)

Cycle	Elem. Op.	Control Signals

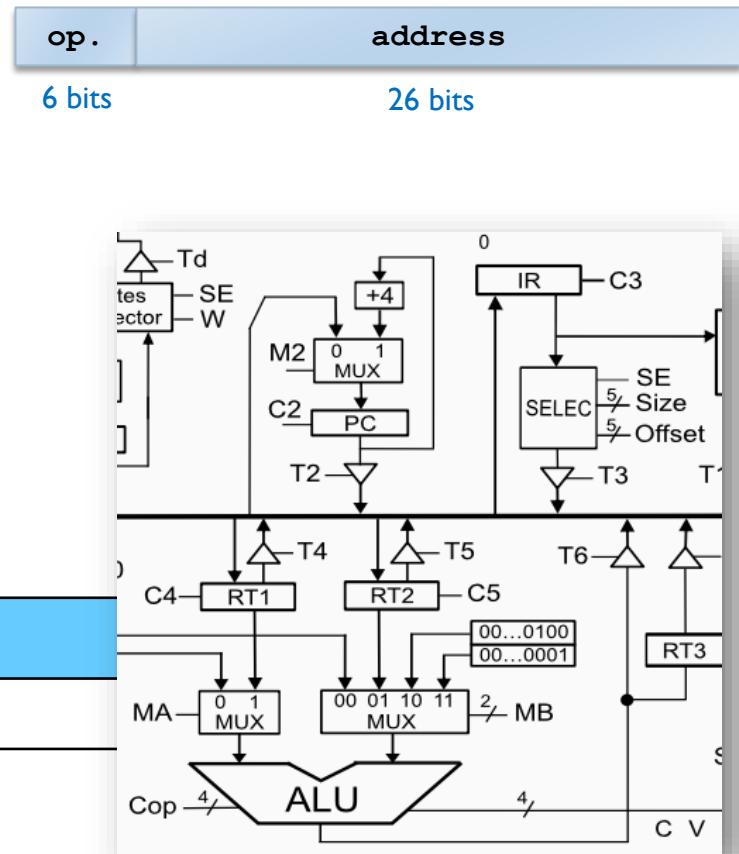


Execution of j addr

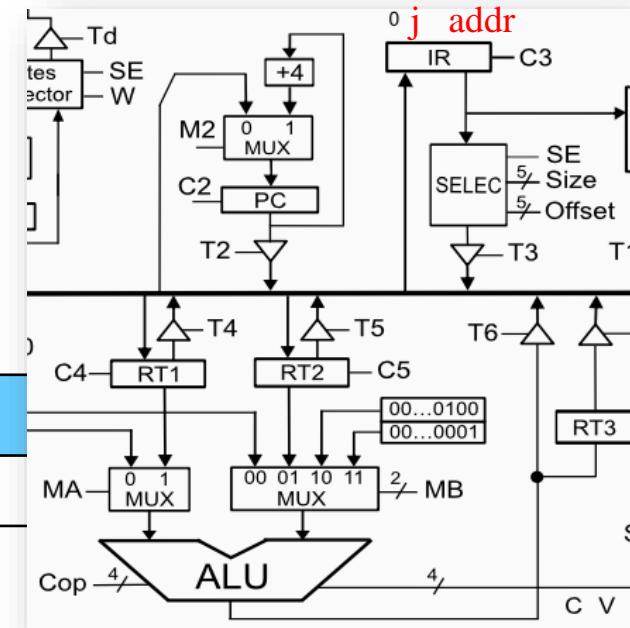

Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, MI Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4	Decoding	A0, B=0, C=0

Execution of j addr

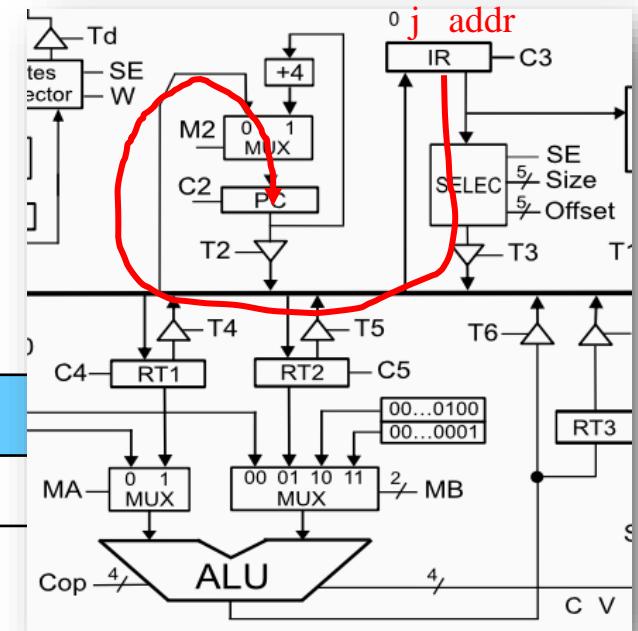


Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, MI Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4	Decoding	A0, B=0, C=0
C5	$\text{PC} \leftarrow \text{RI}(\text{dir})$	Size = 11010 (26), Offset = 00000, SE=0, C2, T3
C6	Salto a fetch	A0, B=1, C=0


Execution of b offset



Cycle	Elem. Op.	Control Signals

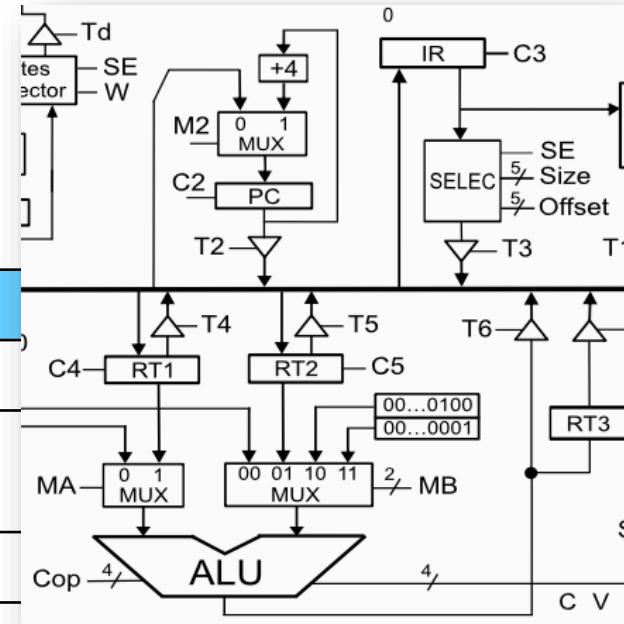

Execution of b offset

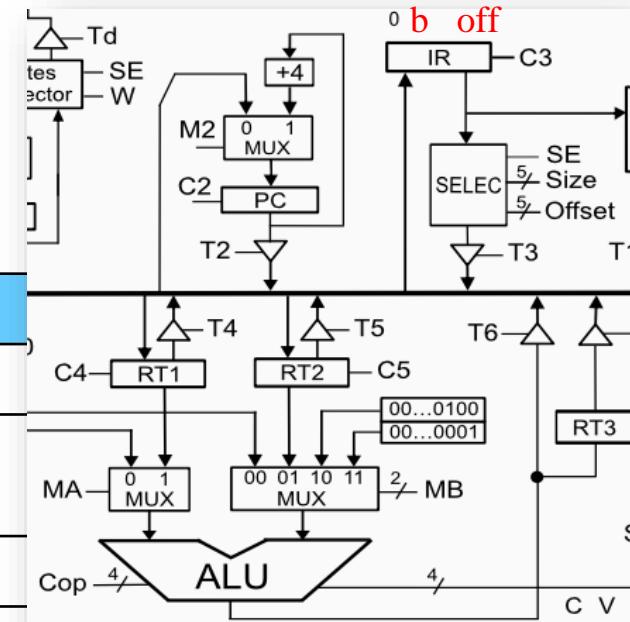


Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, MI Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4	Decoding	A0, B=0, C=0

Execution of b offset




Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, MI Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4	Decoding	A0, B=0, C=0
C5	$\text{RT1} \leftarrow \text{RI}(\text{off})$	Size=10000 (16), Offset=0, SE=1, T3, C4

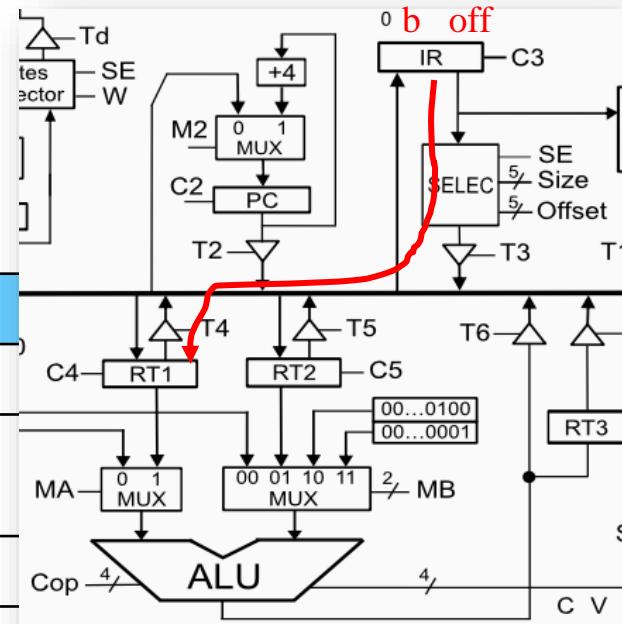


Execution of b offset



Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, MI Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4	Decoding	A0, B=0, C=0
C5	$\text{RT1} \leftarrow \text{RI}(\text{off})$	Size=10000 (16), Offset=0, SE=1, T3, C4
C6	$\text{RT2} \leftarrow \text{PC}$	T2, C5

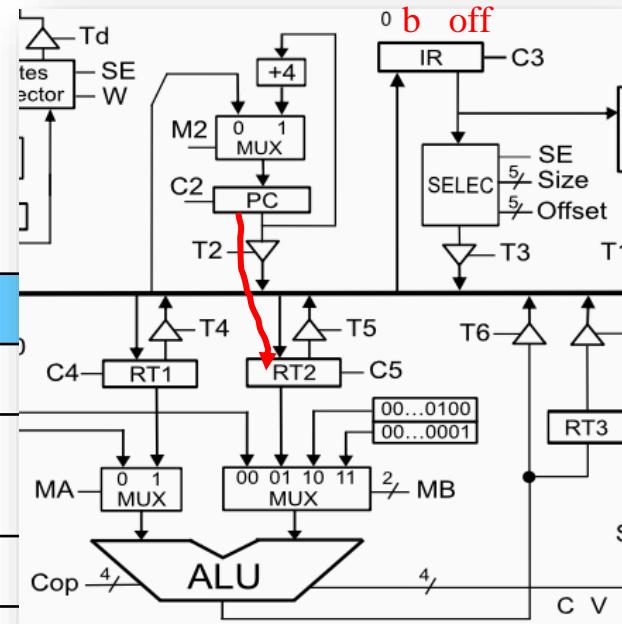


Execution of b offset

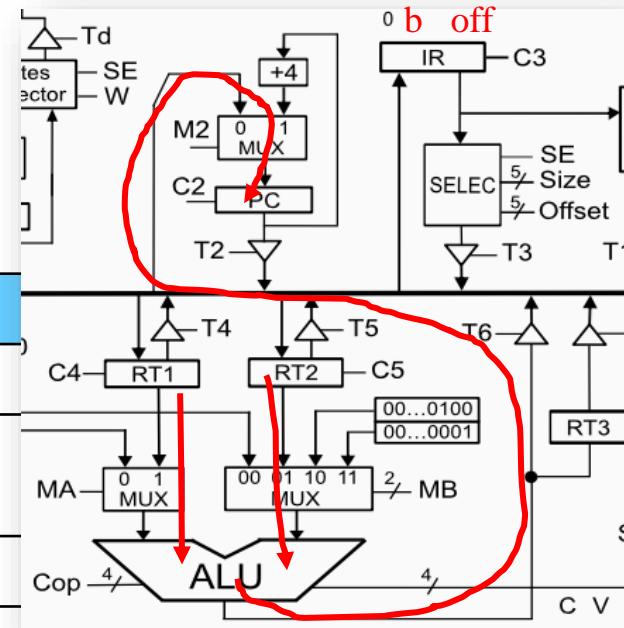


Cycle	Elem. Op.	Control Signals
C1	MAR \leftarrow PC	T2, C0
C2	PC \leftarrow PC + 4, MBR \leftarrow MP	C2, MI Ta, R, CI, MI, BW=11
C3	IR \leftarrow MBR	T1, C3
C4	Decoding	A0, B=0, C=0
C5	RT1 \leftarrow RI(off)	Size=10000 (16), Offset=0, SE=1, T3, C4
C6	RT2 \leftarrow PC	T2, C5
C7	PC \leftarrow RT1 + RT2	MA=1, MB=1, MC=1, SELCOP=+, T6, M2=0, C2
C6	Salto a fetch	A0, B=1, C=0

Elemental Processor: SR

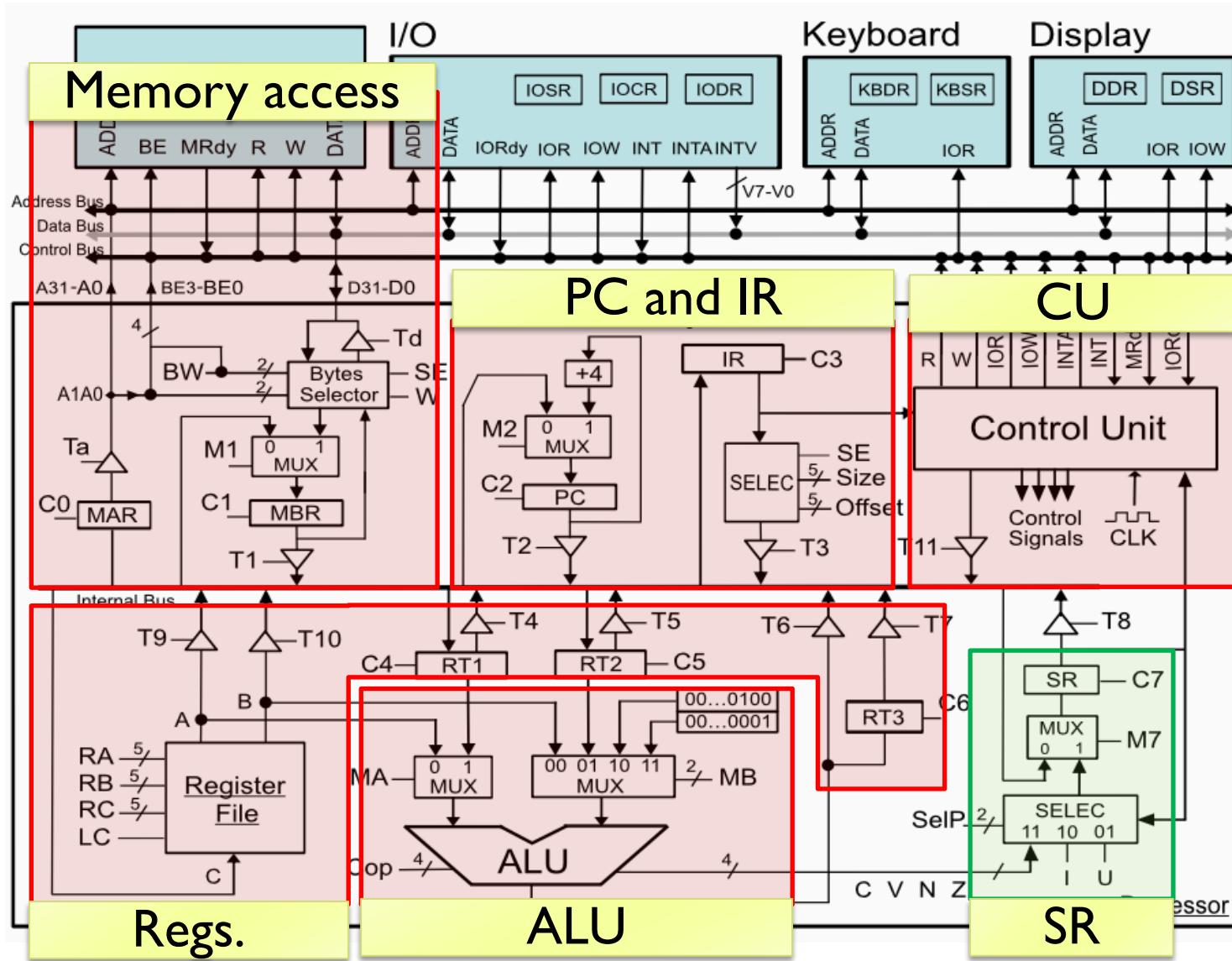


SR: Status Register

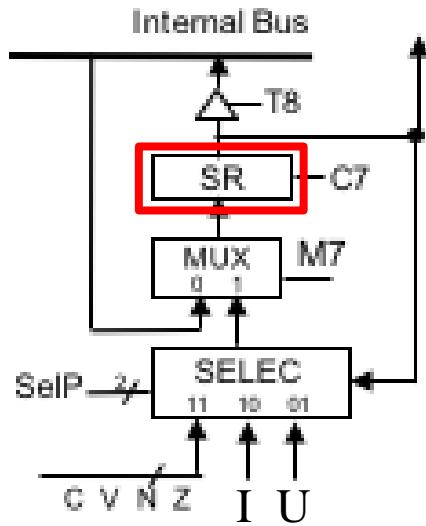

- ▶ Stores information (status bits) about the **status of the program being executed on the processor.**
- ▶ Typical status bits:
 - ▶ C, V, N, Z:
Result from **last operation in ALU**
 - ▶ U:
CPU running in **kernel or user mode**
 - ▶ I:
Interruptions are enabled or not


SR: Status Register

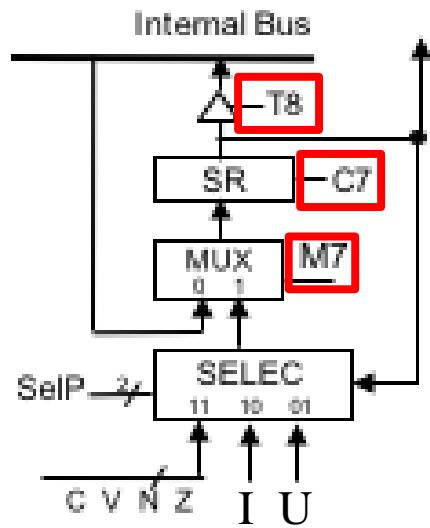

▶ SR

- ▶ T8 – from SR to internal data bus
- ▶ C7 – from internal data bus to SR
- ▶ M7 – flags from IDB or SELEC

SR: Status Register

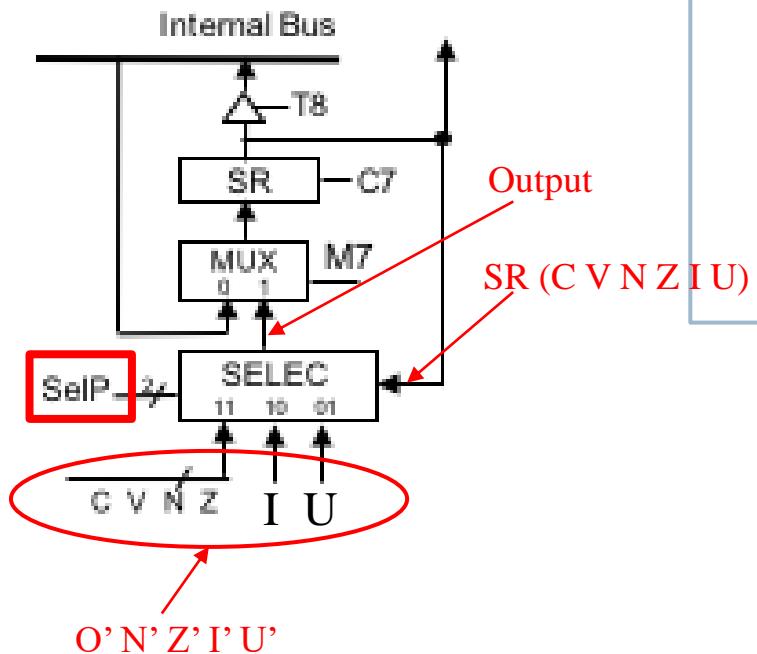


▶ SR

- ▶ T8 – from SR to internal data bus
- ▶ C7 – from internal data bus to SR
- ▶ M7 – flags from IDB or SELEC
- ▶ SelP – update flags: ALU / I / U

```
if (SelP == 11)
    Output = C' V' N' Z' I U
if (SelP == 10)
    Output = C V N Z I' U
if (SelP == 01)
    Output = C V N Z I U'
```

SR: Save/Restore + Update from ALU

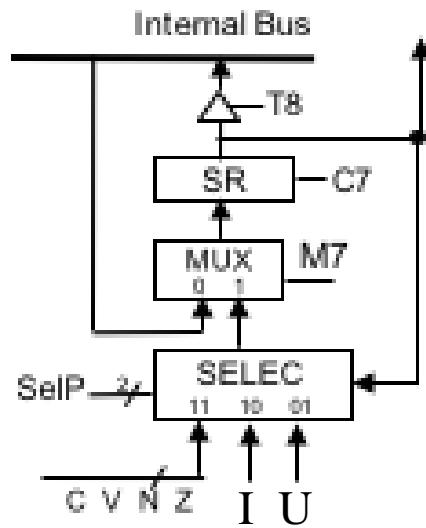


▶ SR

- ▶ T8 – from SR to internal data bus
- ▶ C7 – from internal data bus to SR
- ▶ M7 – flags from IDB or SELEC
- ▶ SelP – update flags:ALU / I / U

- ▶ T8, C4
 - ▶ RTI \leftarrow SR
- ▶ T4, M7=0, C7
 - ▶ SR \leftarrow RTI
- ▶ SelP=II, M7, C7
 - ▶ SR \leftarrow <ALU flags>

SR: check some flag...

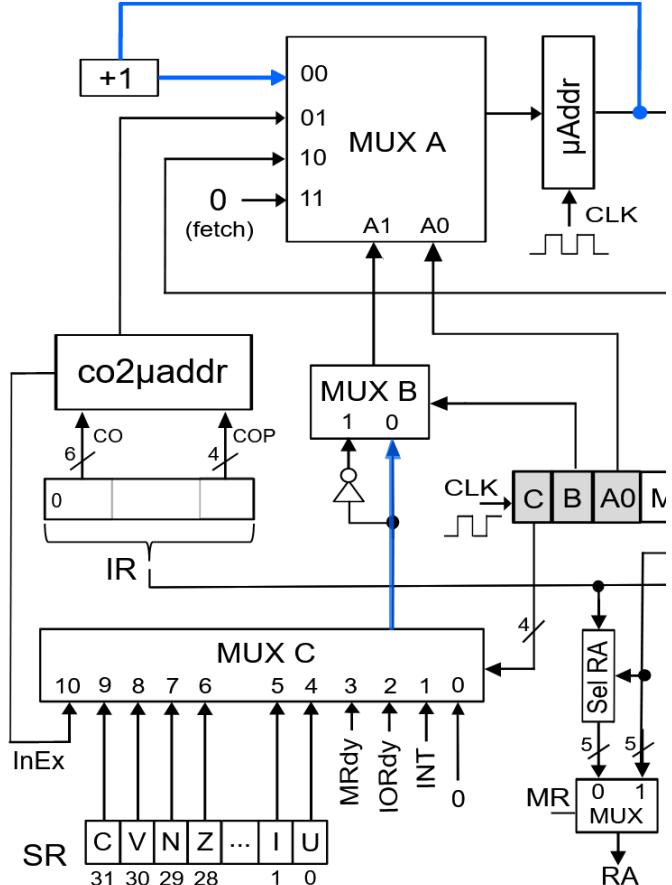

▶ SR

- ▶ C – condition to select
- ▶ B – condition or not condition
- ▶ $A0$ – $I:fetch/co2maddr$
0: from $maddr/maddr+I$

▶ $C=[4\dots 9], B=0, A0=0$

- ▶ If C $maddr \leftarrow MADDR$
else $maddr \leftarrow maddr + I$

▶ $C=0, B=1, A0=0$

- ▶ $maddr \leftarrow MADDR$

beq r1, r2, offset

Cycle	Elem. Op.
C1	MAR \leftarrow PC
C2	PC \leftarrow PC + 4, MBR \leftarrow MP
C3	IR \leftarrow MBR
C4	Decode
C12	Jump to fetch

Si $\$r1 == \$r2$
 $PC \leftarrow PC + offset$

beq r1, r2, offset

Cycle	Elem. Op.
C1	MAR \leftarrow PC
C2	PC \leftarrow PC + 4, MBR \leftarrow MP
C3	IR \leftarrow MBR
C4	Decode
C5	MBR \leftarrow SR
C6	\$r1 - \$r2
C7	Si SR.Z != 0 jump to C11
C11	SR \leftarrow MBR
C12	Jump to fetch

Si \$r1 == \$r2
PC \leftarrow PC + offset

beq r1, r2, offset

Cycle	Elem. Op.
C1	MAR \leftarrow PC
C2	PC \leftarrow PC + 4, MBR \leftarrow MP
C3	IR \leftarrow MBR
C4	Decode
C5	MBR \leftarrow SR
C6	\$r1 - \$r2
C7	Si SR.Z != 0 jump to C11
C8	RT1 \leftarrow PC
C9	RT2 \leftarrow IR(offset)
C10	PC \leftarrow RT1 + RT2
C11	SR \leftarrow MBR
C12	Jump to fetch

Si \$r1 == \$r2
PC \leftarrow PC + offset


beq r1, r2, offset

Cycle	Elem. Op.	Control Signals
C1	MAR \leftarrow PC	T2, C0
C2	PC \leftarrow PC + 4, MBR \leftarrow MP	C2, M1, Ta, R, CI, MI, BW=11
C3	IR \leftarrow MBR	T1, C3
C4	Decode	A0, B=0, C=0
C5	MBR \leftarrow SR	T8, CI
C6	\$r1 - \$r2	SELA=10101, SELB=10000, MC=1, SELCOP=1011, SELP=11, M7, C7
C7	Si SR.Z != 0 jump to C11	A0=0, B=1, C=110, MADDR=beq11
C8	RT1 \leftarrow PC	T2, C4
C9	RT2 \leftarrow IR(offset)	Size=10000, Offset=0, SE=1, T3, C5
C10	PC \leftarrow RT1 + RT2	MA=1, MB=1, MC=1, SELCOP=+, T6, C2
C11	SR \leftarrow MBR	T1, M7=0, C7
C12	Jump to fetch	A0, B=1, C=0

Structure of an elementary computer


CU

Control Unit (C.U.)

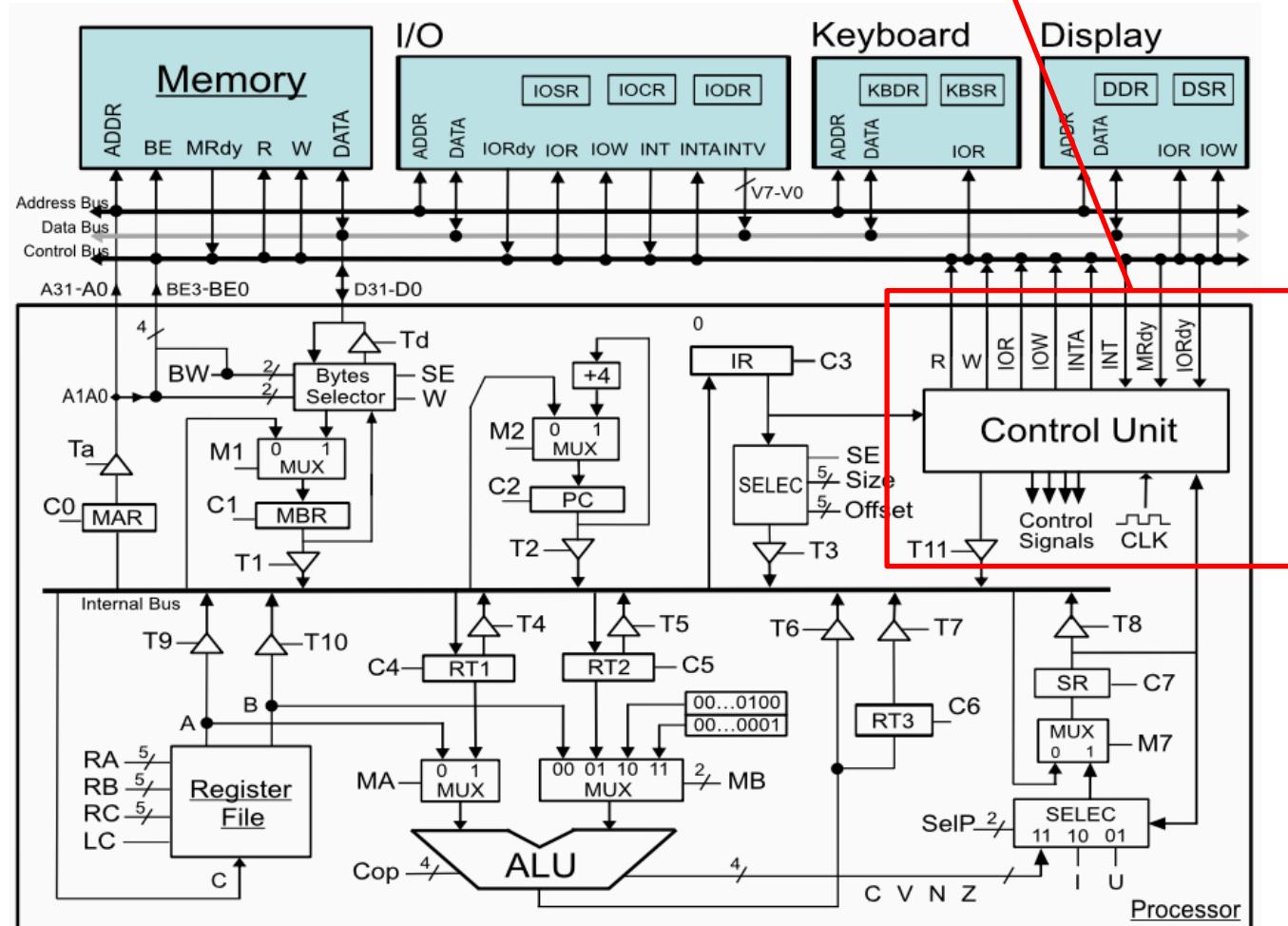


Control unit:

Phases of execution of an instruction

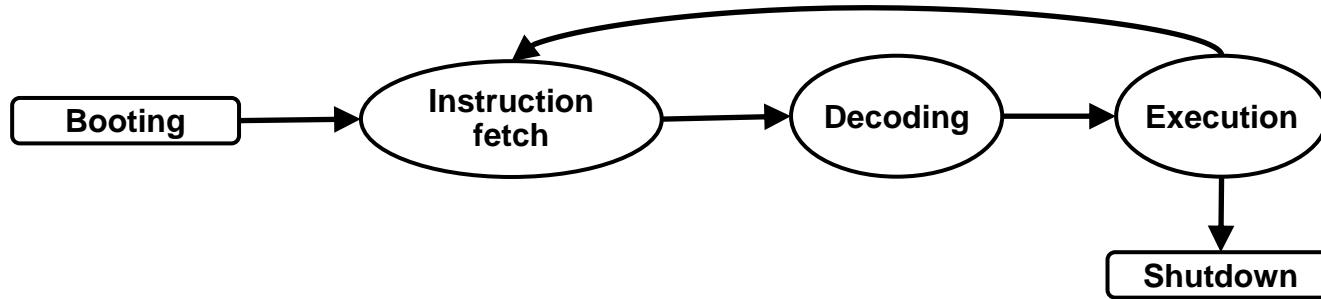

- ▶ **Instruction Reading or fetch**
 - ▶ Read the instruction stored in the memory address indicated by PC and take it to IR.
 - ▶ PC is updated to point to the next instruction
- ▶ **Decoding**
 - ▶ Analysis of the instruction in IR to determine:
 - ▶ The operation to be performed.
 - ▶ Control signals to be activated
- ▶ **Execution**
 - ▶ Generation of the control signals in each clock cycle.


Clock

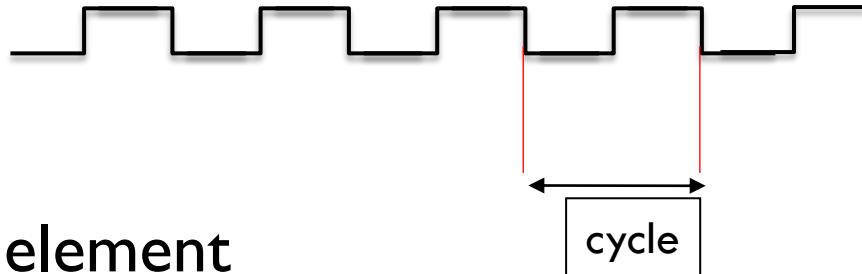


- ▶ A computer is a **synchronous element**
 - ▶ Clock controls the operation
- ▶ The clock regulates the operations in a given time:
 - ▶ In a clock cycle one or more elementary operations are executed as long as there is no conflict
 - ▶ In the same cycle you can perform
 - $\text{MAR} \leftarrow \text{PC}$ and $\text{RT3} \leftarrow \text{RT2} + \text{RTI}$
 - ▶ In the same cycle it **is not possible** to perform
 - $\text{MAR} \leftarrow \text{PC}$ and $\text{RI} \leftarrow \text{RT3}$ **why?**
 - ▶ The necessary control signals are kept active during the cycle

Description of the Control Unit activity

Instruction

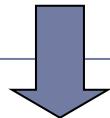


Sequence of
elementary
operations

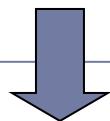

Sequence of **control**
signals for each
elementary operation

mv R0 R1

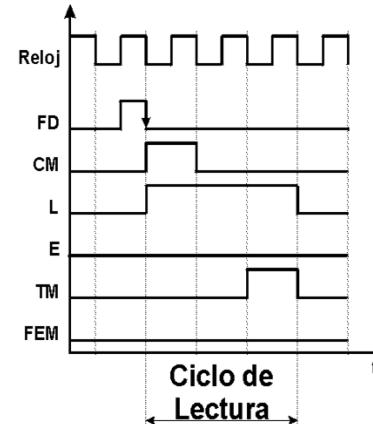
- RI \leftarrow [PC]
- PC++
- decoding
- $R0 \leftarrow R1$




+ level of
hw. details

Description of the Control Unit activity

Instruction

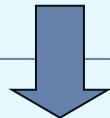


Sequence of
elementary
operations

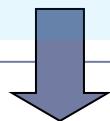

Sequence of **control**
signals for each
elementary operation

mv R0 R1

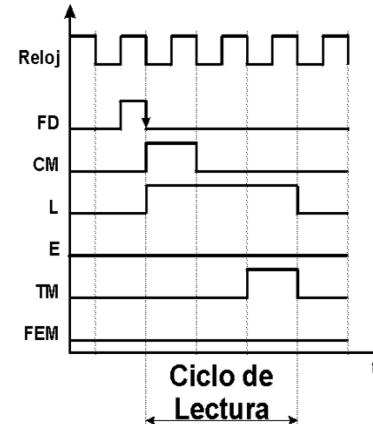- RI \leftarrow [PC]
- PC++
- decoding
- $R0 \leftarrow R1$



+ level of
hw. details

Fetch (Elemental Operations)

- RI \leftarrow [PC]
- PC++
- decoding

Cycle	Elem. Op.
C1	MAR \leftarrow PC
C2	PC \leftarrow PC + 4
C3	MBR \leftarrow MP
C4	IR \leftarrow MBR
C5	Decode




Cycle	Elem. Op.
C1	MAR \leftarrow PC
C2	PC \leftarrow PC + 4, MBR \leftarrow MP
C3	IR \leftarrow MBR
C4	Decode


Possibility of simultaneous operations

Description of the Control Unit activity

Instruction

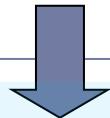


Sequence of
elementary
operations

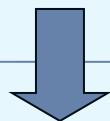

Sequence of **control**
signals for each
elementary operation

mv R0 R1

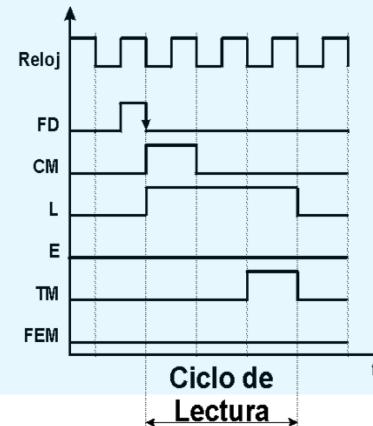- RI \leftarrow [PC]
- PC++
- decoding
- $R0 \leftarrow R1$



+ level of
hw. details

Fetch (Control Signals)


- RI <- [PC]
- PC++
- decoding

- ▶ Specification of the active control signals in each clock cycle
 - ▶ Can be generated from the RT level.

Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, M2 Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3

Example


▶ lw \$reg, dir

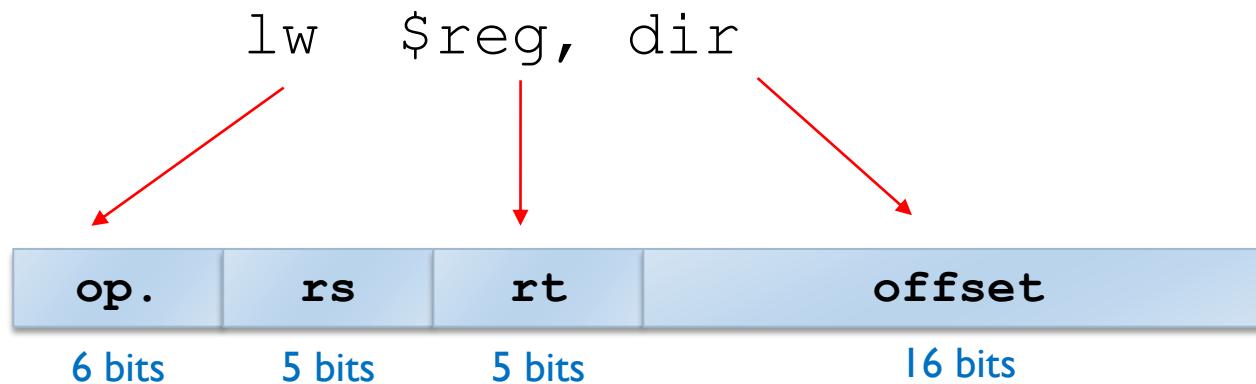

Execution of lw \$reg, dir




Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, M2 Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4		
C5		
C6		
C7		

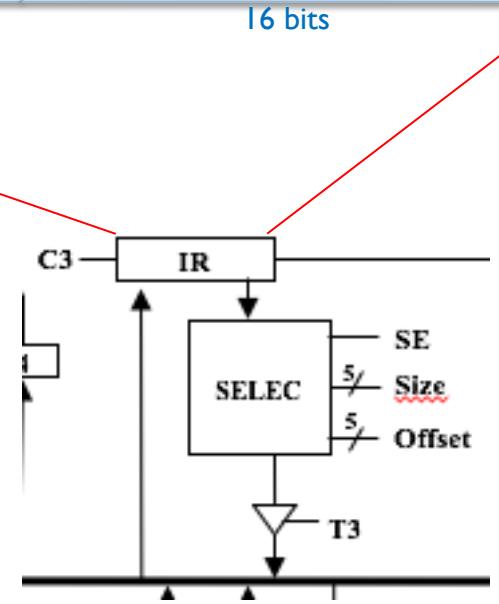

Execution of lw \$reg, dir




Cycle	Elem. Op.	Control Signals
C1	MAR \leftarrow PC	T2, C0
C2	PC \leftarrow PC + 4, MBR \leftarrow MP	C2, M2 Ta, R, CI, MI, BW=11
C3	IR \leftarrow MBR	T1, C3
C4	Decoding	A0, B=0, C=0
C5		
C6		
C7		

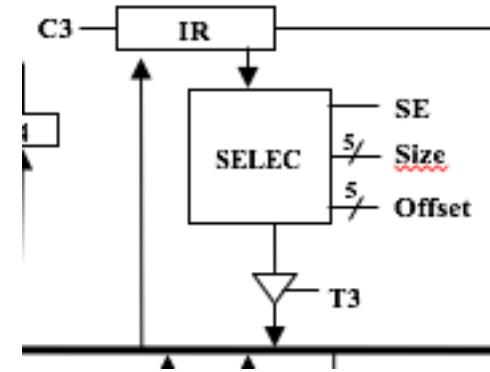

Execution of lw \$reg, dir




Cycle	Elem. Op.	Control Signals
C1	MAR \leftarrow PC	T2, C0
C2	PC \leftarrow PC + 4, MBR \leftarrow MP	C2, M2 Ta, R, CI, MI, BW=11
C3	IR \leftarrow MBR	T1, C3
C4	Decoding	A0, B=0, C=0
C5	MAR \leftarrow RI(dir)	C0, T3, Size = 10000 Offset = 00000
C6		
C7		

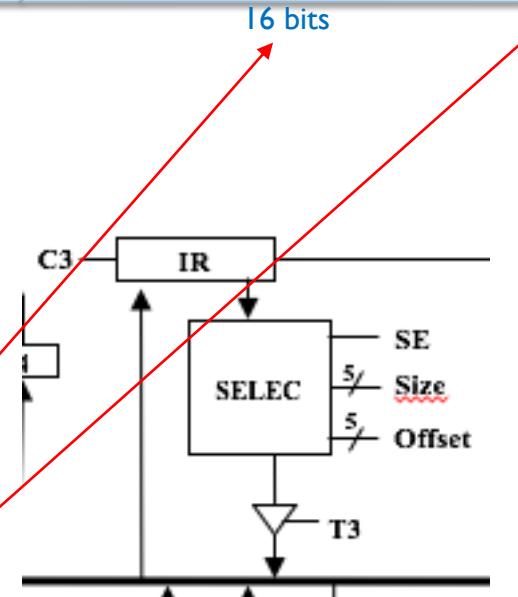

Execution of lw \$reg, dir




Cycle	Elem. Op.	Control Signals
C1	MAR \leftarrow PC	T2, C0
C2	PC \leftarrow PC + 4, MBR \leftarrow MP	C2, M2 Ta, R, CI, MI, BW=11
C3	IR \leftarrow MBR	T1, C3
C4	Decoding	A0, B=0, C=0
C5	MAR \leftarrow RI(dir)	C0, T3, Size = 10000 Offset = 00000
C6	MBR \leftarrow MP	Ta, R, CI, MI, BW=11
C7		

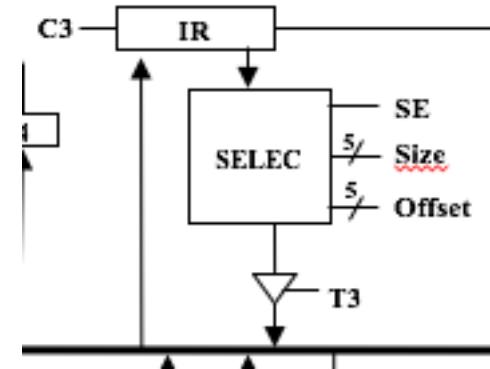

Execution of lw \$reg, dir




Cycle	Elem. Op.	Control Signals
C1	$\text{MAR} \leftarrow \text{PC}$	T2, C0
C2	$\text{PC} \leftarrow \text{PC} + 4$, $\text{MBR} \leftarrow \text{MP}$	C2, M2 Ta, R, CI, MI, BW=11
C3	$\text{IR} \leftarrow \text{MBR}$	T1, C3
C4	Decoding	A0, B=0, C=0
C5	$\text{MAR} \leftarrow \text{RI}(\text{dir})$	C0, T3, Size = 10000 Offset = 00000
C6	$\text{MBR} \leftarrow \text{MP}$	Ta, R, CI, MI, BW=11
C7	$\$reg \leftarrow \text{MBR}$	T1, RC=id \$reg, LC

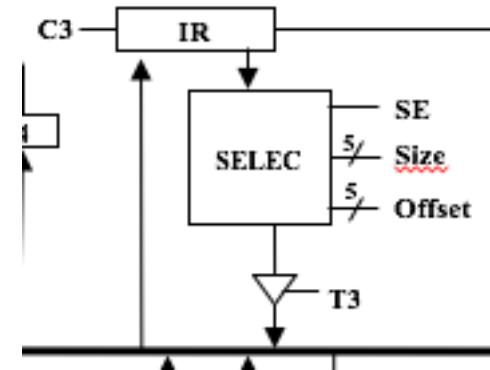

Instructions that take up several words

Example: addm R1, addr R1 \leftarrow R1 + MP [addr]

Format:

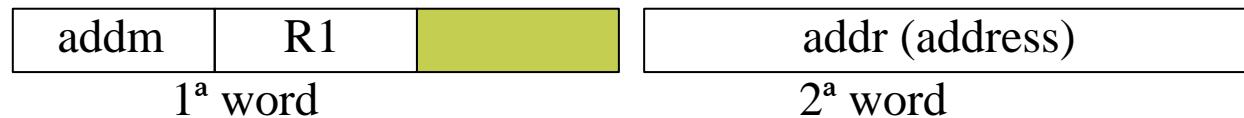

Cycle	Elem. Op.
C1	MAR \leftarrow PC
C2	PC \leftarrow PC + 4, MBR \leftarrow MP
C3	IR \leftarrow MBR
C4	Decoding
C5	MAR \leftarrow PC

Cycle	Elem. Op.
C6	MBR \leftarrow MP, PC \leftarrow PC + 4
C7	MAR \leftarrow MBR
C8	MBR \leftarrow MP
C9	RTI \leftarrow MBR
C10	RI \leftarrow RI + RTI

Simple tips (1/2): general phases in an instruction...

- A. Fetch + Decod.
- B. Fetch operands.
- C. Execution
- D. Store results

Example

ADD (R₂) R₃ (R₄)

A. Fetch + Decod.

- 1.- MAR \leftarrow PC
- 2.- RI \leftarrow Memory(MAR)
- 3.- PC \leftarrow PC + "4"
- 4.- Decoding

B. Fetch operands.

- 5.- MAR \leftarrow R₄
- 6.- MBR \leftarrow Memory(MAR)
- 7.- RTI \leftarrow MBR

C. Execution

- 8.- MBR \leftarrow R₃ + RTI

D. Store results

- 9.- MAR \leftarrow R₂
- 10.- Memory(MAR) \leftarrow MBR

Simple tips (2/2): remember don'ts, everything else is yes...

1. **It is not possible to go through a register in the clock cycle**
2. **It is not possible to take two or more values to a bus at the same time**
3. **It is not possible to set a datapath if the circuitry does not enable it.**

ARCOS Group

uc3m | Universidad **Carlos III** de Madrid

Lesson 4 (I)

The processor

Computer Structure
Bachelor in Computer Science and Engineering

